

EE3124 — Electric Machines & Drives   Comprehensive Exam Question Bank (65 Questions + Formula Sheet)																				
SECTION A — CONCEPTUAL & SHORT-ANSWER QUESTIONS (Q1-type in exam)																				
L1 Overview	<p>Q1. Compare a <b>turbogenerator</b> (thermal/nuclear) with a <b>hydroelectric generator</b>. Address: speed, number of poles, rotor type, physical shape, and reason for each difference.</p>	<p>A1.</p> <table><thead><tr><th></th><th>Turbogenerator</th><th>Hydro Generator</th></tr></thead><tbody><tr><td>Speed</td><td>High — 3000 rpm (2-pole, 50 Hz)</td><td>Low — 150–300 rpm (many poles)</td></tr><tr><td>Poles</td><td>2 or 4</td><td>20, 40+</td></tr><tr><td>Rotor type</td><td>Non-salient (round/cylindrical)</td><td>Salient (projects outward)</td></tr><tr><td>Shape</td><td>Long shaft, small diameter</td><td>Short shaft, large diameter</td></tr><tr><td>Reason</td><td>High speed → round rotor avoids centrifugal stress; few poles sufficient</td><td>Slow turbine → needs many poles; large diameter accommodates them</td></tr></tbody></table> <p>Relation: <math>n_s = \frac{120f}{P}</math>. At 50 Hz, 40 poles → 150 rpm. At 50 Hz, 2 poles → 3000 rpm.</p>		Turbogenerator	Hydro Generator	Speed	High — 3000 rpm (2-pole, 50 Hz)	Low — 150–300 rpm (many poles)	Poles	2 or 4	20, 40+	Rotor type	Non-salient (round/cylindrical)	Salient (projects outward)	Shape	Long shaft, small diameter	Short shaft, large diameter	Reason	High speed → round rotor avoids centrifugal stress; few poles sufficient	Slow turbine → needs many poles; large diameter accommodates them
	Turbogenerator	Hydro Generator																		
Speed	High — 3000 rpm (2-pole, 50 Hz)	Low — 150–300 rpm (many poles)																		
Poles	2 or 4	20, 40+																		
Rotor type	Non-salient (round/cylindrical)	Salient (projects outward)																		
Shape	Long shaft, small diameter	Short shaft, large diameter																		
Reason	High speed → round rotor avoids centrifugal stress; few poles sufficient	Slow turbine → needs many poles; large diameter accommodates them																		
L5 Sync	<p>Q2. (a) Define <b>armature reaction</b> in a synchronous generator. (b) State its effect on terminal voltage <math>V_T</math> for lagging, unity, and leading power factor loads. (c) How is it modelled in the equivalent circuit?</p>	<p>A2.</p> <p>(a) <b>Armature reaction</b> = distortion of the air-gap magnetic field caused by the stator current when a load is connected. The stator currents create a magnetic field <math>B_S</math> that vectorially adds to the rotor field <math>B_R</math>, changing the net field.</p> <p>(b) Effect on <math>V_T</math>:</p> <ul style="list-style-type: none"><li>• <b>Lagging PF:</b> <math>B_S</math> opposes <math>B_R</math> → demagnetising → <math>V_T</math> drops significantly</li><li>• <b>Unity PF:</b> <math>B_S</math> is 90° to <math>B_R</math> → slight distortion only → small <math>V_T</math> drop</li><li>• <b>Leading PF:</b> <math>B_S</math> aids <math>B_R</math> → magnetising → <math>V_T</math> rises (can exceed <math>E_A</math>)</li></ul> <p>(c) Modelled as the synchronous reactance <math>X_S</math> in the per-phase equivalent circuit: <math>E_A = V_\phi + I_A(R_A + jX_S)</math></p>																		
L1/L3-L5	<p>Q3. Explain the function of the <b>commutator and brushes</b> in a DC machine. Why do AC machines not need a commutator?</p>	<p>A3.</p> <p><b>Commutator function:</b> The armature winding of a DC machine generates alternating current as the coils rotate through the magnetic field. The commutator (segmented copper cylinder) acts as a mechanical rectifier — it switches the external connection of each coil at the moment its current reverses, so the <b>external current is always unidirectional (DC)</b>. Carbon brushes ride on the commutator segments to provide the stationary electrical connection.</p> <p><b>Why AC machines don't need it:</b> In AC machines (synchronous and induction), the armature winding is on the <b>stator</b> (stationary). The stator windings are directly connected to the AC supply — no switching is needed. The field is on the rotor (supplied via slip rings for synchronous machines, or induced for induction machines). Since there's no need to convert AC to DC at the output, no commutator is required.</p> <p><i>The commutator is the main source of maintenance issues in DC machines (brush wear, sparking).</i></p>																		

L1/L3-L5

**Q4.** Distinguish between **salient-pole** and **non-salient (round) pole** rotors in synchronous machines. When is each used and why?

**A4.**

	Salient Pole	Non-salient (Round) Pole
Construction	Poles project outward from rotor hub	Poles flush with rotor surface
Air-gap	Non-uniform (smaller under pole, larger between)	Uniform all around
Typical poles	4+ poles (up to 40+)	2–4 poles
Speed	Low speed (<1000 rpm)	High speed (1500–3600 rpm)
Application	Hydroelectric generators, diesel generators	Steam/gas turbine generators (turbogenerators)
Reason	Low speed → can fit large salient poles on big-diameter rotor	High speed → centrifugal forces demand solid, round rotor to avoid stress

L5 Sync

**Q5.** Explain why a synchronous motor **cannot start direct-on-line (DOL)**. Then describe **three starting methods**.

**A5.**

**Cannot start DOL:** At standstill, the rotor is stationary while the stator field rotates at  $n_s$ . The stator field "laps" the rotor twice per electrical cycle, inducing a torque that alternates direction (first +, then −). The net average starting torque is **zero**. Attempting DOL causes large inrush current with no useful acceleration.

**Three starting methods:**

- Variable Frequency Drive (VFD):** Supply frequency starts at ~0 Hz and ramps up to rated frequency, allowing the rotor to always remain in synchronism. Most modern method.
- Amortisseur (damper) windings:** Short-circuited bars embedded in rotor slots — acts like a squirrel-cage rotor. Motor starts as induction motor (~95%  $n_s$ ), then "pulls in" to synchronous speed. Most common for direct DOL-style starting.
- External prime mover:** Spin rotor to synchronous speed using a separate motor, synchronize to grid as a generator, then disconnect prime mover — machine operates as motor.

L5 Sync

**Q6.** Explain the **V-curves** of a synchronous motor. Define underexcited and overexcited. Why would a plant install an overexcited synchronous motor even when no mechanical load is needed?

**A6.**

A V-curve plots  $|I_A|$  vs  $I_F$  (field current) at **constant shaft load power**. It is V-shaped because:

- As  $I_F$  increases from zero:  $|I_A|$  first decreases then increases → minimum at unity PF
- Underexcited** (left of minimum):  $I_A$  lags  $V_\phi$  → motor absorbs reactive power  $Q$  (acts inductively)
- Overexcited** (right of minimum):  $I_A$  leads  $V_\phi$  → motor supplies reactive power  $Q$  to the grid (acts capacitively)

**Synchronous condenser application:** Other loads on a factory bus (motors, transformers) are inductive — they draw lagging current and consume  $Q$ , degrading the plant power factor and incurring utility penalty charges. An overexcited synchronous motor — even with no shaft load — supplies leading current, compensating the lagging loads and improving the overall bus power factor. This is cheaper than banks of capacitors for large installations and the reactive output is controllable by adjusting  $I_F$ .

L3 DC	<p><b>Q7.</b> A series DC motor is accidentally <b>disconnected from its load</b> while running. Explain what happens and why this is dangerous. How does a <b>cumulatively compounded motor</b> avoid this problem?</p>	<p><b>A7.</b></p> <p><b>Series motor at no-load:</b> Field winding is in series with armature <math>\rightarrow \Phi \propto I_a</math>. Speed equation:</p> $\omega_m = \frac{V_a}{K_e K_f I_a}$ <p>As load <math>\rightarrow 0</math>, <math>I_a \rightarrow 0</math> (denominator approaches 0), so <math>\omega_m \rightarrow \infty</math>. The motor <b>over-speeds and can fly apart mechanically</b>, destroying bearings, windings, and potentially injuring personnel.</p> <p><b>Rule:</b> Never run a series DC motor without a coupled load. Never use belt drives (belt can slip off <math>\rightarrow</math> no-load condition).</p> <p><b>Cumulatively compounded motor:</b> Has both a shunt field (constant, provides minimum <math>\Phi</math> even at no-load) and a series field. At no-load: <math>\Phi = \Phi_{\text{shunt}} \neq 0 \rightarrow</math> speed is limited (like a shunt motor). Under heavy load: series field adds flux, giving high torque (like a series motor). Result: safe at no-load + high starting torque.</p>																								
L6 IM	<p><b>Q8.</b> Compare <b>cage rotor</b> and <b>wound rotor</b> induction motors in terms of construction, ability to modify performance, and applications. Why have wound-rotor motors become less common?</p>	<p><b>A8.</b></p> <table> <tr> <th>Feature</th><th>Cage Rotor</th><th>Wound Rotor</th></tr> <tr> <td>Construction</td><td>Bars shorted at both ends by rings</td><td>Full 3-phase winding, slip rings on shaft</td></tr> <tr> <td>Rotor circuit access</td><td>Not accessible</td><td>External resistance insertable via slip rings</td></tr> <tr> <td>Starting</td><td>High inrush current (<math>\sim 6 \times I_{\text{rated}}</math>), moderate <math>\tau_{\text{start}}</math></td><td>Can achieve maximum <math>\tau</math> at start by setting <math>R_2 + R_{\text{ext}} = X_{\text{eq}}</math></td></tr> <tr> <td>Speed control</td><td>Only via VFD</td><td>External R changes torque-speed curve (wasteful)</td></tr> <tr> <td>Maintenance</td><td>Very low (no brushes)</td><td>Brushes + slip rings require regular maintenance</td></tr> <tr> <td>Cost</td><td>Lower</td><td>Higher</td></tr> <tr> <td>Applications</td><td>Pumps, fans, compressors, general purpose</td><td>Large cranes, mills, hoists (historically)</td></tr> </table> <p><b>Why wound rotor less common:</b> Modern variable frequency drives (VFDs) give cage motors the same speed/torque flexibility without the maintenance penalty of slip rings and brushes. A cage motor + VFD is the preferred modern solution.</p>	Feature	Cage Rotor	Wound Rotor	Construction	Bars shorted at both ends by rings	Full 3-phase winding, slip rings on shaft	Rotor circuit access	Not accessible	External resistance insertable via slip rings	Starting	High inrush current ( $\sim 6 \times I_{\text{rated}}$ ), moderate $\tau_{\text{start}}$	Can achieve maximum $\tau$ at start by setting $R_2 + R_{\text{ext}} = X_{\text{eq}}$	Speed control	Only via VFD	External R changes torque-speed curve (wasteful)	Maintenance	Very low (no brushes)	Brushes + slip rings require regular maintenance	Cost	Lower	Higher	Applications	Pumps, fans, compressors, general purpose	Large cranes, mills, hoists (historically)
Feature	Cage Rotor	Wound Rotor																								
Construction	Bars shorted at both ends by rings	Full 3-phase winding, slip rings on shaft																								
Rotor circuit access	Not accessible	External resistance insertable via slip rings																								
Starting	High inrush current ( $\sim 6 \times I_{\text{rated}}$ ), moderate $\tau_{\text{start}}$	Can achieve maximum $\tau$ at start by setting $R_2 + R_{\text{ext}} = X_{\text{eq}}$																								
Speed control	Only via VFD	External R changes torque-speed curve (wasteful)																								
Maintenance	Very low (no brushes)	Brushes + slip rings require regular maintenance																								
Cost	Lower	Higher																								
Applications	Pumps, fans, compressors, general purpose	Large cranes, mills, hoists (historically)																								
L6 IM	<p><b>Q9.</b> Explain why an induction motor <b>can never reach synchronous speed</b>. What is <b>slip</b> and what is the typical operating slip range at full load?</p>	<p><b>A9.</b></p> <p>Induction motor torque requires <b>relative motion</b> between the rotating stator field (at <math>n_s</math>) and the rotor. As <math>n_m \rightarrow n_s</math>:</p> <ul style="list-style-type: none"> <li><math>\rightarrow</math> Slip <math>s = (n_s - n_m)/n_s \rightarrow 0</math></li> <li><math>\rightarrow</math> Rotor induced voltage <math>E_R = s \cdot E_{R0} \rightarrow 0</math></li> <li><math>\rightarrow</math> Rotor current <math>I_2 \rightarrow 0</math> (no EMF to drive it)</li> <li><math>\rightarrow</math> Induced torque <math>\tau_{\text{ind}} \rightarrow 0</math> (no rotor field)</li> <li><math>\rightarrow</math> Friction losses decelerate rotor <math>\rightarrow n_m</math> falls below <math>n_s</math> again</li> </ul> <p>The rotor reaches a stable equilibrium where <math>\tau_{\text{ind}} = \tau_{\text{load}}</math> at some finite slip. <b>Typical full-load slip: 1–5%</b> for small/medium motors. The motor runs just below synchronous speed.</p> <p><b>Slip</b> <math>s = \frac{n_s - n_m}{n_s}</math> (dimensionless). <math>s=0</math>: synchronous (zero torque). <math>s=1</math>: standstill. Normal operation: <math>0 &lt; s &lt; 0.05</math>.</p>																								

L5 Sync	<p><b>Q10.</b> State the <b>four conditions</b> for synchronising a generator to an infinite bus. Why must the incoming generator's frequency be <i>slightly higher</i>—and not equal to—the grid frequency?</p>	<p><b>A10.</b></p> <p><b>Four conditions (all must be met simultaneously):</b></p> <ol style="list-style-type: none"> <li>1. RMS terminal voltage of incoming generator = grid RMS voltage</li> <li>2. Phase sequence of incoming generator = grid phase sequence</li> <li>3. Phase angle of incoming = grid phase angle (checked with synchroscope — pointer rotating slowly clockwise)</li> <li>4. Frequency of incoming generator slightly <b>higher</b> than grid frequency</li> </ol> <p><b>Why slightly higher, not equal:</b> If exactly equal, the machines might lock in with <math>\delta = 0 \rightarrow</math> no power transfer. With slightly higher frequency, after closing the breaker the torque angle <math>\delta</math> naturally increases from 0, the generator begins delivering real power to the grid (positive <math>\delta</math> = generator mode). If the frequency were lower, <math>\delta</math> would go negative and the machine would immediately absorb power as a motor, undesirably drawing current from the grid on first connection.</p> <p><i>A synchroscope only checks one phase — phase sequence must be verified separately with a phase sequence meter.</i></p>																								
L7 Special	<p><b>11.</b> Compare <b>BLDC (Brushless DC)</b> and <b>sinusoidal synchronous AC motors</b>. Both have PM rotors and 3-phase stators — what are their key operational differences? What are BLDC's advantages over conventional PM DC motors?</p>	<p><b>A11.</b></p> <table border="1"> <thead> <tr> <th>Feature</th><th>BLDC</th><th>Sinusoidal Sync AC Motor</th></tr> </thead> <tbody> <tr> <td>Stator winding</td><td>Concentrated (trapezoidal layout)</td><td>Distributed (sinusoidal layout)</td></tr> <tr> <td>Back-EMF</td><td>Trapezoidal</td><td>Sinusoidal</td></tr> <tr> <td>Drive current</td><td>Quasi-square (2 phases on at a time)</td><td>3-phase sinusoidal</td></tr> <tr> <td>Converted power</td><td><math>P_{conv} = 2EI = \text{constant}</math> (ripple-free)</td><td>Constant (3-phase balance)</td></tr> <tr> <td>Torque ripple</td><td>Higher</td><td>Lower</td></tr> <tr> <td>Noise</td><td>More</td><td>Quieter</td></tr> <tr> <td>Motor equations</td><td>DC: <math>E_a = k\omega</math>, <math>\tau = kl</math></td><td>AC phasor equations</td></tr> </tbody> </table> <p><b>BLDC advantages over conventional PM DC motor:</b> no brushes/commutator <math>\rightarrow</math> no sparking, no maintenance, no RF noise; higher efficiency (no brush drop <math>\approx 2V</math>); longer life; higher speeds possible (<math>&gt;50,000</math> rpm); power winding on stator <math>\rightarrow</math> better heat dissipation.</p>	Feature	BLDC	Sinusoidal Sync AC Motor	Stator winding	Concentrated (trapezoidal layout)	Distributed (sinusoidal layout)	Back-EMF	Trapezoidal	Sinusoidal	Drive current	Quasi-square (2 phases on at a time)	3-phase sinusoidal	Converted power	$P_{conv} = 2EI = \text{constant}$ (ripple-free)	Constant (3-phase balance)	Torque ripple	Higher	Lower	Noise	More	Quieter	Motor equations	DC: $E_a = k\omega$ , $\tau = kl$	AC phasor equations
Feature	BLDC	Sinusoidal Sync AC Motor																								
Stator winding	Concentrated (trapezoidal layout)	Distributed (sinusoidal layout)																								
Back-EMF	Trapezoidal	Sinusoidal																								
Drive current	Quasi-square (2 phases on at a time)	3-phase sinusoidal																								
Converted power	$P_{conv} = 2EI = \text{constant}$ (ripple-free)	Constant (3-phase balance)																								
Torque ripple	Higher	Lower																								
Noise	More	Quieter																								
Motor equations	DC: $E_a = k\omega$ , $\tau = kl$	AC phasor equations																								
L3 DC	<p><b>Q12.</b> Explain the <b>two methods of controlling the speed</b> of a separately excited DC motor. State the speed region each applies to, the torque capability in each region, and why they cannot be combined at the same speed.</p>	<p><b>A12.</b></p> <p><b>Speed equation:</b> <math>\omega_m = \frac{V_a}{K_e \Phi} - \frac{R_a}{(K_e \Phi)^2} \cdot \tau</math></p> <p><b>Method 1 — Armature Voltage Control (below base speed <math>\omega_{base}</math>):</b></p> <ul style="list-style-type: none"> <li>• Reduce <math>V_a \rightarrow</math> lower <math>\omega_m</math>; field <math>\Phi = \text{constant}</math> at rated</li> <li>• <math>T</math>–<math>\omega</math> slope unchanged; <math>\tau_{max} = \text{constant}</math> (rated) <math>\rightarrow</math> <b>constant torque region</b></li> <li>• Limit: increasing <math>V_a</math> above rated to go above <math>\omega_{base}</math> would insulate the armature</li> </ul> <p><b>Method 2 — Field Weakening (above base speed <math>\omega_{base}</math>):</b></p> <ul style="list-style-type: none"> <li>• Reduce <math>I_f \rightarrow</math> lower <math>\Phi \rightarrow</math> higher <math>\omega_m</math>; <math>V_a = \text{rated}</math></li> <li>• <math>\tau_{max}</math> decreases (<math>\tau = K_e \Phi I_a</math>, <math>\Phi \downarrow</math> while <math>I_a</math> limited) <math>\rightarrow</math> <b>constant power region</b></li> <li>• Limit: too much field weakening <math>\rightarrow</math> cannot maintain torque for heavy loads</li> </ul> <p><b>Combined range:</b> Armature voltage below <math>\omega_{base}</math> + field weakening above <math>\omega_{base} \rightarrow</math> total speed range up to 40:1.</p>																								

L6 IM	<p><b>Q13.</b> What is <b>VVVF (Variable Voltage Variable Frequency)</b> control for an induction motor? Explain the three operating regions and why constant V/f is used below base speed.</p>	<p><b>A13.</b></p> <p>VVVF (also called V/f control) uses an inverter to vary both voltage and frequency applied to the motor, controlling its speed by changing <math>n_s = 120f/P</math>.</p> <p><b>Three operating regions:</b></p> <ol style="list-style-type: none"> <li><b>1. Low frequency / Voltage boost region (<math>f &lt; \sim 5 \text{ Hz}</math>):</b> Stator resistance drop becomes significant relative to induced EMF (<math>E \approx V - IR</math>). Extra voltage boost applied to maintain adequate flux and prevent torque collapse.</li> <li><b>2. Constant torque region (<math>5 \text{ Hz} \leq f \leq f_{\text{base}}</math>):</b> Maintain <math>V/f = \text{constant}</math>. This keeps the air-gap flux <math>\Phi = \text{constant}</math> (since <math>E \approx 4.44k\Phi f</math>, constant <math>V/f \rightarrow \text{constant } \Phi</math>). Constant flux <math>\rightarrow</math> constant <math>\tau_{\text{max}}</math>. Motor can deliver rated torque at all speeds.</li> <li><b>3. Constant power / field-weakening region (<math>f &gt; f_{\text{base}}</math>):</b> Voltage held at rated maximum; frequency continues to increase. Flux decreases (<math>\Phi \propto V/f \rightarrow \text{decreases}</math>). Torque capability falls (<math>\propto 1/f^2</math>); power <math>\approx \text{constant}</math>. Equivalent to DC field weakening.</li> </ol> <p><b>Why constant V/f:</b> Core flux <math>\Phi \propto E/f \approx V/f</math>. Keeping <math>V/f</math> constant maintains rated flux <math>\rightarrow</math> rated torque capability. Reducing V with f prevents core saturation at low speeds; increasing V with f prevents core saturation at high speeds.</p>
L5 Sync	<p><b>Q14.</b> What is <b>hunting</b> in a synchronous motor? What causes it and how is it suppressed?</p>	<p><b>A14.</b></p> <p><b>Hunting:</b> An oscillation of the rotor around its synchronous (steady-state) position. It occurs when a sudden load change or disturbance causes the torque angle <math>\delta</math> to overshoot and then oscillate about the new equilibrium value. The rotor "swings" back and forth around <math>n_s</math>.</p> <p><b>Cause:</b> The synchronous motor is effectively a second-order underdamped system. When <math>\delta</math> is displaced, the restoring torque <math>\propto \sin\delta</math> acts, but with low damping the system oscillates rather than settling directly. If undamped, oscillations can grow and the motor can pull out of synchronism.</p> <p><b>Suppression — Amortisseur (damper) windings:</b> Short-circuited bars in rotor slots. During steady-state operation they carry no current (no relative motion). When the rotor oscillates, there IS relative motion between rotor and the rotating stator field <math>\rightarrow</math> currents induced in damper bars <math>\rightarrow</math> these currents create a braking torque proportional to oscillation speed <math>\rightarrow</math> damping effect <math>\rightarrow</math> oscillations die out quickly. This is the same principle as eddy current braking.</p>
L6 IM	<p><b>Q15.</b> Why does an induction motor always operate at <b>lagging power factor</b>? Can it ever supply reactive power to the grid?</p>	<p><b>A15.</b></p> <p><b>Why lagging PF:</b> An induction motor requires magnetising current to establish flux in the air gap. This magnetising current <math>I_M</math> flows through the magnetising branch <math>X_M</math> and is <b>purely lagging</b> (<math>90^\circ</math> behind V). The total stator current = active component (in phase with V, transfers real power) + magnetising component (lags <math>90^\circ</math>). The resulting total <math>I_1</math> always lags <math>V_\phi</math>.</p> <p>Unlike a synchronous motor, the induction motor has no DC field excitation — it must get ALL its magnetising flux from the stator supply, which always requires lagging reactive current. The power factor is typically 0.8–0.9 lagging at full load, and can fall to 0.1–0.3 lagging at no load.</p> <p><b>Can it supply reactive power?</b> A standard induction motor on a standard supply: <b>No</b> — it always absorbs Q. However, a <b>self-excited induction generator</b> (with capacitors providing the magnetising Q) can deliver both P and Q to isolated loads. On a grid, an induction <b>generator</b> (run above <math>n_s</math>) consumes Q from the grid for magnetisation but supplies P to the grid.</p>

L7 Special	<p><b>Q16.</b> Describe the <b>Switched Reluctance Machine (SRM)</b>: structure, operating principle, and why it has high torque ripple. State two advantages and two disadvantages vs induction motor.</p>	<p><b>A16.</b></p> <p><b>Structure:</b> Doubly-salient — both stator and rotor have projecting poles (salient poles). No permanent magnets. No rotor windings. Stator has coils wound around each salient pole. Rotor has no windings at all (just iron teeth).</p> <p><b>Operating principle:</b> When a stator coil is energised, the rotor tries to minimise its reluctance by rotating toward alignment with the stator poles. Torque:</p> $\tau = \frac{1}{2} \cdot i^2 \cdot \frac{dL}{d\theta}$ <p>Coils must be switched off before full alignment (otherwise negative torque on return stroke). Electronic commutation switches coils in sequence to maintain unidirectional rotation.</p> <p><b>High torque ripple cause:</b> Torque is produced in discrete pulses (one per coil firing). Between pulses, output torque dips. The non-sinusoidal nature of <math>L(\theta)</math> means torque cannot be perfectly constant. Ripple ratio can be 20–100% depending on number of poles.</p> <p><b>Advantages:</b> No PMs (low cost, no magnet demagnetisation risk); simple rugged rotor → high-speed and high-temperature capable.</p> <p><b>Disadvantages:</b> High torque ripple → vibration and acoustic noise; requires complex power converter and position sensing.</p>																								
L5 Sync	<p><b>Q17.</b> What is <b>voltage regulation</b> of a synchronous generator? Write the formula. For a generator supplying a lagging PF load, will VR be positive or negative? What about a leading PF load?</p>	<p><b>A17.</b></p> <p><b>Voltage regulation:</b></p> $VR\% = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$ <p>where <math>V_{NL}</math> = no-load terminal voltage (= <math> E_A </math> per phase for Y-connection, with field current unchanged) and <math>V_{FL}</math> = full-load rated terminal voltage.</p> <p><b>Lagging PF load:</b> Armature reaction demagnetises → terminal voltage drops under load → <math>V_{NL} &gt; V_{FL}</math> → <b>VR &gt; 0 (positive)</b>. A larger field current is needed to restore rated <math>V_T</math> under lagging load.</p> <p><b>Leading PF load:</b> Armature reaction magnetises → terminal voltage rises under load → <math>V_{NL} &lt; V_{FL}</math> → <b>VR &lt; 0 (negative)</b>. Less field current (or no excitation) is needed; the machine can be self-exciting with leading loads.</p> <p><i>A well-regulated generator has VR close to zero. Synchronous generators typically have VR of 10–30% for lagging loads.</i></p>																								
L3+L6	<p><b>Q18.</b> Compare a <b>DC series motor</b> and a <b>three-phase induction motor</b> for use as a traction motor (e.g. in a train). What are the tradeoffs? Which is used in modern high-speed trains and why?</p>	<p><b>A18.</b></p> <table border="1"> <thead> <tr> <th>Feature</th><th>DC Series Motor</th><th>3-phase Induction Motor</th></tr> </thead> <tbody> <tr> <td>Starting torque</td><td>Very high (<math>\tau \propto I^2</math>)</td><td>Moderate (can be increased with VFD)</td></tr> <tr> <td>Speed control</td><td>Simple (vary <math>V_a</math>)</td><td>Excellent with VFD (V/f control)</td></tr> <tr> <td>Maintenance</td><td>High (commutator, brushes)</td><td>Very low (cage rotor)</td></tr> <tr> <td>Weight/power density</td><td>Lower</td><td>Higher (especially with IGBT VFD)</td></tr> <tr> <td>Regenerative braking</td><td>Possible but complex</td><td>Easy with VFD (4-quadrant operation)</td></tr> <tr> <td>Operating environment</td><td>Sparking issues in dusty/flammable areas</td><td>Totally enclosed, safe anywhere</td></tr> <tr> <td>Speed range</td><td>Wide (flux control + voltage)</td><td>Very wide with modern VFDs</td></tr> </tbody> </table> <p><b>Modern high-speed trains (MTR, high-speed rail) use induction motors with VFDs</b> because: no brush/commutator maintenance (critical in tunnels), higher reliability, smooth speed control, easy regenerative braking (energy recovery into grid), better performance density.</p>	Feature	DC Series Motor	3-phase Induction Motor	Starting torque	Very high ( $\tau \propto I^2$ )	Moderate (can be increased with VFD)	Speed control	Simple (vary $V_a$ )	Excellent with VFD (V/f control)	Maintenance	High (commutator, brushes)	Very low (cage rotor)	Weight/power density	Lower	Higher (especially with IGBT VFD)	Regenerative braking	Possible but complex	Easy with VFD (4-quadrant operation)	Operating environment	Sparking issues in dusty/flammable areas	Totally enclosed, safe anywhere	Speed range	Wide (flux control + voltage)	Very wide with modern VFDs
Feature	DC Series Motor	3-phase Induction Motor																								
Starting torque	Very high ( $\tau \propto I^2$ )	Moderate (can be increased with VFD)																								
Speed control	Simple (vary $V_a$ )	Excellent with VFD (V/f control)																								
Maintenance	High (commutator, brushes)	Very low (cage rotor)																								
Weight/power density	Lower	Higher (especially with IGBT VFD)																								
Regenerative braking	Possible but complex	Easy with VFD (4-quadrant operation)																								
Operating environment	Sparking issues in dusty/flammable areas	Totally enclosed, safe anywhere																								
Speed range	Wide (flux control + voltage)	Very wide with modern VFDs																								

9. A magnetic core with air gap:  $A_c=A_g=3.8\text{ cm}^2$ ,  $l_c=30\text{ cm}$ ,  $g=1.5\text{ mm}$ ,  $N=80\text{ turns}$ ,  $\mu_r=3000$ ,  $i=1.8\text{ A}$ . Find: (a)  $\mathfrak{R}_c$  and  $\mathfrak{R}_g$ , (b) flux  $\Phi$ , (c) flux linkage  $\lambda$ , (d) inductance  $L$ .

A19.

$$\begin{aligned} \text{(a) } \mathfrak{R}_c &= \frac{l_c}{\mu_0 \mu_r A_c} = \frac{0.30}{4\pi \times 10^{-7} \times 3000 \times 3.8 \times 10^{-4}} = \boxed{0.211 \times 10^6 \text{ A}\cdot\text{t/Wb}} \\ \mathfrak{R}_g &= \frac{g}{\mu_0 A_g} = \frac{1.5 \times 10^{-3}}{4\pi \times 10^{-7} \times 3.8 \times 10^{-4}} = \boxed{3.141 \times 10^6 \text{ A}\cdot\text{t/Wb}} \\ \text{(b) } \Phi &= \frac{N \cdot i}{\mathfrak{R}_c + \mathfrak{R}_g} = \frac{80 \times 1.8}{3.352 \times 10^6} = \boxed{4.30 \times 10^{-5} \text{ Wb}} \\ \text{(c) } \lambda &= N \cdot \Phi = 80 \times 4.30 \times 10^{-5} = \boxed{3.44 \times 10^{-3} \text{ Wb}\cdot\text{turn}} \\ \text{(d) } L &= \frac{\lambda}{i} = \frac{3.44 \times 10^{-3}}{1.8} = \boxed{1.91 \text{ mH}} \end{aligned}$$

$\mathfrak{R}_g/\mathfrak{R}_c \approx 15:1 \rightarrow$  air gap dominates. Fringing neglected ( $A_g=A_c$ ).

10. A **three-leg core** has  $N=300$  turns on the centre leg. Left and right outer legs:  $\mathfrak{R}_L=\mathfrak{R}_R=8 \times 10^6 \text{ A}\cdot\text{t/Wb}$  each. Centre leg:  $\mathfrak{R}_C=2 \times 10^6 \text{ A}\cdot\text{t/Wb}$ . Find current  $i$  for  $\Phi_C=1.0 \times 10^{-4} \text{ Wb}$  and flux in each outer leg.

A20.

$$\begin{aligned} \mathfrak{R}_L \parallel \mathfrak{R}_R &= \frac{\mathfrak{R}_L}{2} = 4 \times 10^6 \text{ A}\cdot\text{t/Wb} \quad \mathfrak{R}_{\text{total}} = 2 \times 10^6 + 4 \times 10^6 = 6 \times 10^6 \\ \text{mmf} &= \Phi_C \times \mathfrak{R}_{\text{total}} = 1.0 \times 10^{-4} \times 6 \times 10^6 = 600 \text{ A}\cdot\text{t} \\ i &= \frac{600}{300} = \boxed{2.0 \text{ A}} \\ \Phi_L = \Phi_R &= \frac{\Phi_C}{2} = \boxed{0.5 \times 10^{-4} \text{ Wb}} \quad (\text{symmetry}) \end{aligned}$$

11. A **linear machine (moving bar)**:  $B=0.5\text{ T}$  into page,  $l=1\text{ m}$ ,  $R=0.25\text{ }\Omega$ ,  $V_B=100\text{ V}$  (battery).

- (a) Initial current and force on bar when switch first closed (bar stationary)
- (b) No-load steady-state speed
- (c) With a  $25\text{ N}$  opposing force, find steady-state speed and machine efficiency

A21.

(a) At start:  $e=0$ , bar stationary:

$$I_{\text{init}} = \frac{V_B}{R} = \frac{100}{0.25} = 400\text{ A} \quad F_{\text{init}} = BIl = 0.5 \times 400 \times 1 = \boxed{200\text{ N}}$$

(b) No-load steady state:  $I \rightarrow 0$  (frictionless, no load), so  $e = V_B$ :

$$e = BLv \rightarrow v_{\text{NL}} = \frac{V_B}{BL} = \frac{100}{0.5 \times 1} = \boxed{200\text{ m/s}}$$

(c) Steady state with  $F=25\text{ N}$  opposing:

$$\begin{aligned} BIl &= 25\text{ N} \rightarrow I = \frac{25}{0.5 \times 1} = 50\text{ A} \\ e &= V_B - IR = 100 - 50 \times 0.25 = 87.5\text{ V} \quad v = \frac{87.5}{0.5 \times 1} = \boxed{175\text{ m/s}} \\ P_{\text{in}} &= V_B \times I = 100 \times 50 = 5000\text{ W} \quad P_{\text{out}} = F \times v = 25 \times 175 = 4375\text{ W} \\ \eta &= \frac{4375}{5000} = \boxed{87.5\%} \end{aligned}$$

L2 Magnetics	<p><b>2.</b> A coil of L=100 mH carries current i=5 A. (a) Find the energy stored. (b) If the core has <math>\mathfrak{R}=10^5</math> A·t/Wb, verify using the alternate energy formula. (c) If the air gap is doubled (<math>\mathfrak{R}</math> doubles), how does stored energy change for the same current?</p>	<p><b>A22.</b></p> <p>(a) <math>W = \frac{1}{2} Li^2 = \frac{1}{2} \times 0.1 \times 25 = \boxed{1.25 \text{ J}}</math></p> <p>(b) <math>L = N^2 / \mathfrak{R} \rightarrow N^2 = L \times \mathfrak{R} = 0.1 \times 10^5 = 10^4 \rightarrow N = 100</math> turns. <math>\Phi = Ni / \mathfrak{R} = 100 \times 5 / 10^5 = 5 \times 10^{-3}</math> Wb:</p> $W = \frac{\Phi^2 \cdot \mathfrak{R}}{2} = \frac{(5 \times 10^{-3})^2 \times 10^5}{2} = \frac{25 \times 10^{-6} \times 10^5}{2} = 1.25 \text{ J} \checkmark$ <p>(c) If <math>\mathfrak{R}</math> doubles: <math>L = N^2 / \mathfrak{R}</math> halves <math>\rightarrow L' = 50</math> mH. Same current i=5A:</p> $W' = \frac{1}{2} \times 0.05 \times 25 = 0.625 \text{ J} = \boxed{\text{halved}}$ <p><i>Air gap stores most of the magnetic energy — but increasing the gap reduces L and thus reduces stored energy at same current. The field energy density in the gap (<math>B^2/2\mu_0</math>) determines the force between pole faces.</i></p>
L2 Magnetics	<p><b>3.</b> A toroid: N=200 turns, mean radius r=10 cm, cross-section A=4 cm², <math>\mu_r=2000</math>. Find the current i required to establish B=1 T in the core. If the core saturates (<math>\mu_r</math> drops to 100 at B=1.5 T), find new i for B=1.5 T and explain the implication.</p>	<p><b>A23.</b></p> $B = \mu_0 \mu_r \cdot \frac{Ni}{2\pi r} \rightarrow i = \frac{B \cdot 2\pi r}{\mu_0 \mu_r N}$ $i = \frac{1.0 \times 2\pi \times 0.1}{4\pi \times 10^{-7} \times 2000 \times 200} = \frac{0.6283}{0.5027} = \boxed{1.25 \text{ A}}$ <p>At saturation (B=1.5 T, <math>\mu_r=100</math>):</p> $i = \frac{1.5 \times 2\pi \times 0.1}{4\pi \times 10^{-7} \times 100 \times 200} = \frac{0.9425}{2.513 \times 10^{-3}} = \boxed{37.5 \text{ A}}$ <p><b>Implication:</b> To increase B by only 50% (from 1.0 to 1.5 T), the required current increases 30× (from 1.25 to 37.5 A). Once saturated, the core is nearly as hard to magnetise as air. This is why operating machines above rated flux is very inefficient — huge current with little flux gain. Also, reluctance <math>\mathfrak{R} = l/(\mu_0 \mu_r A)</math> becomes much larger when saturated.</p>
SECTION C — DC MACHINE CALCULATIONS		
L3 DC	<p><b>Q24.</b> A DC series motor draws 35 A at 220 V at 1000 rpm. <math>R_a=0.25 \Omega</math>, <math>R_f=0.15 \Omega</math>, <math>P_{rot}=600</math> W. Find: (a) <math>E_a</math>, (b) developed torque <math>\tau_d</math>, (c) output power <math>P_{out}</math>.</p>	<p><b>A24.</b></p> <p>(a) <math>E_a = V_T - I_a(R_a + R_f) = 220 - 35 \times 0.4 = \boxed{206 \text{ V}}</math></p> <p>(b) <math>\omega_m = 2\pi \times 1000 / 60 = 104.7</math> rad/s <math>\tau_d = \frac{E_a I_a}{\omega_m} = \frac{206 \times 35}{104.7} = \boxed{68.9 \text{ N}\cdot\text{m}}</math></p> <p>(c) <math>P_{out} = 220 \times 35 - 35^2 \times 0.4 - 600 = 7700 - 490 - 600 = \boxed{6610 \text{ W}}</math></p>
L3 DC	<p><b>Q25.</b> A 25 kW, 125 V separately excited DC machine, <math>E_a=127</math> V, <math>R_a=0.03 \Omega</math>, n=3000 rpm constant. Determine mode (motor/generator), <math>I_a</math>, terminal power, and electromagnetic torque for:</p> <p>(a) <math>V_T=130</math> V   (b) <math>V_T=124</math> V</p>	<p><b>A25.</b></p> <p>(a) <math>V_T=130 &gt; E_a=127 \rightarrow</math> <b>Motor.</b> External supply drives current in.</p> $I_a = \frac{130 - 127}{0.03} = \boxed{100 \text{ A}} \quad P_{term} = 130 \times 100 = 13 \text{ kW (input)} \quad P_{conv} = 127 \times 100 = 12.7 \text{ kW}$ $\tau = \frac{12700}{100\pi} = \boxed{40.4 \text{ N}\cdot\text{m}}$ <p>(b) <math>V_T=124 &lt; E_a=127 \rightarrow</math> <b>Generator.</b> Machine pushes current out.</p> $I_a = \frac{127 - 124}{0.03} = \boxed{100 \text{ A}} \quad P_{term} = 124 \times 100 = 12.4 \text{ kW (output)} \quad \tau = \boxed{40.4 \text{ N}\cdot\text{m}}$ <p><i>Same torque magnitude — what changed is the direction of power flow, not the magnitude of electromagnetic interaction.</i></p>



L3 DC

**Q26. A DC shunt generator:**  $V_T=240$  V,  $R_a=0.08$   $\Omega$ ,  $R_f=120$   $\Omega$ ,  $n=1500$  rpm, load current  $I_L=100$  A. Find: (a) field current  $I_f$ , (b) armature current  $I_a$ , (c) generated  $E_a$ , (d) input torque  $\tau_{in}$ , (e) efficiency  $\eta$ .

**A26.**

$$(a) I_f = \frac{V_T}{R_f} = \frac{240}{120} = \boxed{2 \text{ A}}$$

$$(b) I_a = I_L + I_f = 100 + 2 = \boxed{102 \text{ A}} \quad (\text{generator: } I_a \text{ flows out})$$

$$(c) \text{Generator KVL: } E_a = V_T + I_a R_a = 240 + 102 \times 0.08 = \boxed{248.2 \text{ V}}$$

$$(d) \omega_m = 2\pi \times 1500 / 60 = 50\pi \text{ rad/s} \quad \tau_{in} = \frac{E_a I_a}{\omega_m} = \frac{248.2 \times 102}{50\pi} = \boxed{161.4 \text{ N}\cdot\text{m}}$$

$$(e) P_{out} = V_T \times I_L = 240 \times 100 = 24000 \text{ W} \quad P_{in} = E_a \times I_a = 248.2 \times 102 = 25316 \text{ W}$$

$$\eta = \frac{24000}{25316} = \boxed{94.8\%}$$

L3 DC

**Q27. A DC motor:**  $V_T=220$  V,  $R_a=0.4$   $\Omega$ , rated  $I_a=50$  A. To limit starting current to **twice rated**, an external resistance  $R_{ext}$  is inserted in series with the armature at start.

(a) Find the required  $R_{ext}$

(b) As the motor accelerates and  $E_a$  rises to 100 V, what is the new armature current with  $R_{ext}$  still in circuit?

(c) At what  $E_a$  should  $R_{ext}$  be removed?

**A27.**

(a) Max allowed  $I_a = 2 \times 50 = 100$  A. At start,  $E_a = 0$ :

$$I_{max} = \frac{V_T}{R_a + R_{ext}} = 100 \text{ A} \rightarrow R_{ext} = \frac{220}{100} - 0.4 = \boxed{1.8 \Omega}$$

(b) When  $E_a = 100$  V ( $R_{ext}$  still in):

$$I_a = \frac{V_T - E_a}{R_a + R_{ext}} = \frac{220 - 100}{0.4 + 1.8} = \frac{120}{2.2} = \boxed{54.5 \text{ A}}$$

(c) Remove  $R_{ext}$  when  $I_a$  without  $R_{ext}$  would not exceed 100 A:

$$I_a = \frac{V_T - E_a}{R_a} \leq 100 \text{ A} \rightarrow V_T - E_a \leq 40 \text{ V} \rightarrow E_a \geq \boxed{180 \text{ V}}$$

L3 DC

**Q28. A DC shunt motor:**  $K_e \Phi = 1$  V·s/rad,  $R_a = 0.25$   $\Omega$ ,  $V_a = 250$  V, currently  $E_a = 245$  V. (a) Find no-load speed. (b) Field flux decreases by 10% ( $K_e \Phi = 0.9$ ). Find new no-load speed and explain the cause-effect chain.

**A28.**

$$(a) \omega_0 = \frac{E_a}{K_e \Phi} = \frac{245}{1.0} = \boxed{245 \text{ rad/s}}$$

$$(b) \omega_{0,new} = \frac{V_a}{K_e \Phi_{new}} = \frac{250}{0.9} = \boxed{277.8 \text{ rad/s (13.4\% faster)}}$$

Cause-effect:  $\downarrow I_f \rightarrow \downarrow \Phi \rightarrow \downarrow E_a = K_e \Phi \omega \rightarrow \uparrow I_a = (V_a - E_a) / R_a \rightarrow \uparrow \tau_{ind} = K_e \Phi I_a$  (net increase since  $I_a$  rises more than  $\Phi$  falls)  
 $\rightarrow$  rotor accelerates  $\rightarrow \uparrow E_a \rightarrow \downarrow I_a \rightarrow$  new equilibrium at higher  $\omega$ .

L3 DC

**Q29.** A DC series motor supplies a fan where torque  $T \propto n^2$ . At  $V_T=220\text{ V}$ ,  $I_a=25\text{ A}$ ,  $n=300\text{ rpm}$ .  $R_a=0.6\text{ }\Omega$ ,  $R_f=0.4\text{ }\Omega$ . Fan speed to be reduced to 200 rpm by inserting external resistance  $R_{ext}$ :

(a) Find developed torque  $T_1$  and new torque  $T_2$

(b) Find new armature current  $I_{a2}$  and  $R_{ext}$

(c) Find new output power

**A29.**

(a)  $E_{a1}=220-25\times1=195\text{ V}$      $\omega_1=2\pi\times300/60=10\pi=31.4\text{ rad/s}$

$$T_1=\frac{E_{a1}I_{a1}}{\omega_1}=\frac{195\times25}{10\pi}=\boxed{155.2\text{ N}\cdot\text{m}}$$
$$T_2=T_1\times(200/300)^2=155.2\times0.444=\boxed{68.9\text{ N}\cdot\text{m}}$$

(b) Series motor:  $T\propto I_a^2 \rightarrow T_2/T_1=(I_{a2}/I_{a1})^2$ :

$$I_{a2}=25\times\sqrt{(68.9/155.2)}=25\times\sqrt{0.444}=25\times0.667=\boxed{16.67\text{ A}}$$
$$E_{a2}=E_{a1}\times\frac{I_{a2}\times n_2}{I_{a1}\times n_1}=195\times\frac{16.67\times200}{25\times300}=195\times0.444=86.6\text{ V}$$
$$R_{ext}=\frac{V_T-E_{a2}}{I_{a2}}-(R_a+R_f)=\frac{220-86.6}{16.67}-1.0=8.0-1.0=\boxed{7.0\text{ }\Omega}$$

(c)  $P_{out,2}\approx E_{a2}\times I_{a2}=86.6\times16.67=\boxed{1443\text{ W}}$

L3 DC

**Q30.** Compare **armature voltage control** vs **armature resistance control** for speed reduction of a DC motor. Why is resistance control considered inefficient? Calculate power loss in  $R_{ext}=2\text{ }\Omega$  with  $I_a=40\text{ A}$  and compare to useful output if  $E_a=100\text{ V}$  at that operating point.

**A30.**

Feature	Armature Voltage Control	Armature Resistance Control
Method	Reduce $V_a$ via converter	Insert $R_{ext}$ in series with armature
Efficiency	High ( $\approx 95\%$ + for modern converters)	Low (energy wasted in $R_{ext}$ )
Speed range	Wide, precise	Limited by heat dissipation
Heat generated	Minimal	Large (proportional to $I^2R_{ext}$ )
Speed regulation	Good ( $T-\omega$ slope unchanged)	Poor ( $T-\omega$ slope steepens)
Initial cost	Higher (needs converter)	Cheaper (just a resistor)

**Efficiency calculation:**

$$P_{wasted\text{ in }R_{ext}} = I_a^2 \times R_{ext} = 40^2 \times 2 = 3200\text{ W}$$
$$P_{useful} = E_a \times I_a = 100 \times 40 = 4000\text{ W}$$

Resistor wastes  $\boxed{3200/7200 = 44\%}$  of total input — clearly inefficient.

SECTION D — AC MACHINE FUNDAMENTALS

L4 AC Fund.

**11.** A 2-pole, 3-phase generator:  $B_M=0.2\text{ T}$ ,  $n=3600\text{ rpm}$ , stator diameter=0.5 m,  $l=0.3\text{ m}$ ,  $N_C=15\text{ turns/coil}$ , Y-connected. Find: (a) three phase voltages, (b)  $V_{\phi,rms}$ , (c)  $V_{T,rms}$

**A31.**

$$\omega_m=120\pi\text{ rad/s} \quad \Phi_M=2\times0.25\times0.3\times0.2=0.03\text{ Wb} \quad \hat{e}=15\times120\pi\times0.03=54\pi=\boxed{169.6\text{ V}}$$

(a)  $v_a=169.6\sin(120\pi t)\text{ V}$ ,  $v_b=169.6\sin(120\pi t-120^\circ)\text{ V}$ ,  $v_c=169.6\sin(120\pi t-240^\circ)\text{ V}$

(b)  $V_\phi=169.6/\sqrt{2}=\boxed{119.9\text{ V}\approx120\text{ V}}$     (c)  $V_T=\sqrt{3}\times120=\boxed{207.8\text{ V}\approx208\text{ V}}$

L4 AC Fund.

**12.** (a) A synchronous machine must produce 50 Hz power at exactly 375 rpm. How many poles P must it have? (b) A 6-pole machine in a 60 Hz system — what is its synchronous speed? (c) A machine has  $n_s=600\text{ rpm}$  on a 50 Hz system — how many poles? Is this physically realizable?

**A32.**

(a)  $P = \frac{120 \times f}{n_s} = \frac{120 \times 50}{375} = 16\text{ poles}$      $\boxed{P = 16\text{ (8 pole pairs)}}$  ✓ (integer, even)

(b)  $n_s = \frac{120 \times 60}{6} = \boxed{1200\text{ rpm}}$

(c)  $P = \frac{120 \times 50}{600} = 10\text{ poles}$      $\boxed{P=10\text{ (5 pole pairs) — physically realizable}}$

Key check: P must be a positive even integer. Odd-pole machines cannot be built (poles must come in N-S pairs).

L4 AC Fund.

**Q33.** A four-pole stator winding has an electrical angle  $\theta_e=180^\circ$ . (a) What is the mechanical angle  $\theta_m$ ? (b) If the supply frequency is 50 Hz, what is the mechanical speed  $n_s$ ? (c) A fractional-pitch coil spans  $160^\circ$  electrical instead of  $180^\circ$ . Qualitatively, what is the benefit and the cost?

**A33.**

(a)  $\theta_m = \frac{\theta_e}{P/2} = \frac{180^\circ}{2} = \mathbf{90^\circ \text{ mechanical}}$

(b)  $n_s = 120 \times 50 / 4 = \mathbf{1500 \text{ rpm}}$

(c) **Benefit of fractional pitch (160° vs 180°):** The pitch factor  $k_p = \sin(\text{pitch}/2) = \sin(80^\circ) = 0.985$ . The coil's fundamental voltage is slightly reduced (by 1.5%) but harmonic voltages (3rd, 5th, etc.) are much more reduced — e.g. 3rd harmonic has pitch factor  $\sin(3 \times 80^\circ) / \sin(3 \times 90^\circ) = \sin(240^\circ) / 1 \approx 0.866 / 1$  — significantly attenuated. Result: cleaner, more sinusoidal output voltage.

**Cost:** Fundamental voltage is slightly reduced (by factor  $k_p < 1$ ), and end turns are slightly longer. But the reduction in harmonic distortion usually outweighs this.

SECTION E — SYNCHRONOUS GENERATOR

L5 Sync

**Q34.** A 200 kVA, 480 V, 50 Hz, Y-connected synchronous generator. At rated  $I_F=5$  A:  $V_{T,OC}=540$  V,  $I_{L,SC}=300$  A. DC test:  $V_{DC}=10$  V,  $I_{DC}=25$  A. Find  $R_A$ ,  $E_A$ , and  $X_S$ .

**A34.**

$R_A = \frac{V_{DC}}{2I_{DC}} = \frac{10}{50} = \mathbf{0.20 \, \Omega}$       $E_A = \frac{540}{\sqrt{3}} = \mathbf{311.8 \text{ V}}$

$Z_S = \frac{311.8}{300} = 1.039 \, \Omega$       $X_S = \sqrt{1.039^2 - 0.20^2} = \mathbf{1.020 \, \Omega}$

L5 Sync

**Q35.** A 6 kV, 3-phase, Y-connected generator,  $X_S=0.6 \, \Omega$ ,  $R_A \approx 0$ , supplying 30 MVA at 0.9 PF lagging. Find: (a)  $V_\phi$ ,  $I_A$ , (b)  $E_A$  and  $\delta$ , (c) voltage regulation VR%.

**A35.**

(a)  $V_\phi = 6000 / \sqrt{3} = 3464 \text{ V}$       $I_A = 30 \times 10^6 / (\sqrt{3} \times 6000) = 2887 \text{ A} \angle -25.84^\circ$

(b)  $E_A = 3464 + j0.6 \times 2887 \angle -25.84^\circ = 3464 + j1732 \angle 64.16^\circ = 4217 + j1559$

$|E_A| = \mathbf{4498 \text{ V}}$       $\delta = \tan^{-1}(1559 / 4217) = \mathbf{20.3^\circ}$

(c)  $VR\% = \frac{|E_A| - V_\phi}{V_\phi} \times 100 = \frac{4498 - 3464}{3464} \times 100 = \mathbf{29.9\%}$

*High VR for lagging load — field current must increase significantly to maintain rated  $V_T$  under load.*

L5 Sync

**Q36.** Same generator as Q35, but now supplies 30 MVA at 0.9 PF **leading**. Find  $E_A$  and VR%. Compare with Q35 result and explain physically.

**A36.**

$I_A = 2887 \angle +25.84^\circ = 2598 + j1259 \text{ A (leading)}$

$E_A = 3464 + j0.6 \times (2598 + j1259) = 3464 + j1559 + j^2 \times 755 = 3464 - 755 + j1559 = 2709 + j1559$

$|E_A| = \sqrt{2709^2 + 1559^2} = \mathbf{3125 \text{ V}}$

$VR\% = \frac{3125 - 3464}{3464} \times 100 = \mathbf{-9.8\% \text{ (negative!)}}$

**Physical explanation:** Leading current means the stator magnetic field **aids** the rotor field (magnetising armature reaction). The terminal voltage **RISES** when this load is connected. If the load disconnects,  $V_T$  would **fall** to  $V_{NL} = |E_A| = 3125 \text{ V} < 3464 \text{ V}$ . Capacitive loads can be dangerous — generators may overvoltage on load rejection if they were pre-compensating for the leading power factor.

L5 Sync	<p><b>Q37.</b> A 100 MVA, 14.4 kV, 0.8 PF lagging, 2-pole, 50 Hz, Y-connected generator: <math>X_S=2.281\ \Omega</math>, <math>R_A=0.0228\ \Omega</math>. Find: (a) <math> E_A </math> and <math>\delta</math>, (b) shaft input torque (ignore losses), (c) what is the maximum power this generator can deliver if <math>E_A</math> stays at this value?</p>	<p><b>A37.</b></p> $V_\phi = 14400/\sqrt{3} = 8314\text{ V} \quad I_A = 100 \times 10^6 / (\sqrt{3} \times 14400) = 4009\text{ A} \angle -36.87^\circ$ <p>(a) <math>E_A = 8314 + (3207 - j2405)(0.0228 + j2.281) = 13873 + j7261</math> <math> E_A  = \boxed{15,658\text{ V}}</math> <math>\delta = \boxed{27.6^\circ}</math></p> <p>(b) <math>P_{out} = 100 \times 10^6 \times 0.8 = 80\text{ MW}</math> <math>\omega_m = 2\pi \times 50 = 100\pi\text{ rad/s}</math> (2-pole)</p> $\tau_{in} = P/\omega = 80 \times 10^6 / 100\pi = \boxed{254.6\text{ kN}\cdot\text{m}}$ <p>(c) <math>P_{max} = \frac{3V_\phi E_A}{X_S} = \frac{3 \times 8314 \times 15658}{2.281} = \boxed{171.6\text{ MW}}</math> (at <math>\delta = 90^\circ</math>)</p> <p><i>Operating power (80 MW) is 46.6% of <math>P_{max}</math> <math>\rightarrow</math> stable operating point with good margin.</i></p>
L5 Sync	<p><b>Q38.</b> A <math>\Delta</math>-connected, 60 Hz, 4-pole synchronous generator: <math>V_T=480\text{ V}</math>, <math>X_S=0.1\ \Omega</math>, <math>R_A=0.015\ \Omega</math>. Full load: <math>I_L=1200\text{ A}</math> at 0.8 PF lagging. Friction/windage=40 kW, core losses=30 kW, field losses negligible.</p> <p>(a) Find shaft rotation speed (b) Find full-load <math>E_A</math> (c) Find overall efficiency</p>	<p><b>A38.</b></p> <p>(a) <math>n_s = 120 \times 60 / 4 = \boxed{1800\text{ rpm}}</math></p> <p><math>\Delta</math>-connected: <math>V_\phi = V_T = 480\text{ V}</math>. <math>I_A = I_L / \sqrt{3} = 1200 / \sqrt{3} = 692.8\text{ A} \angle -36.87^\circ</math></p> <p>(b) <math>E_A = 480 + (554.2 - j415.7)(0.015 + j0.1)</math>  <math>= 480 + (554.2 \times 0.015 + 554.2 \times j0.1 + (-j415.7) \times 0.015 + (-j415.7)(j0.1))</math>  <math>= 480 + (8.31 + j55.42 - j6.24 + 41.57) = 480 + 49.88 + j49.18 = 529.9 + j49.18</math>  <math> E_A  = \sqrt{529.9^2 + 49.18^2} = \boxed{532.2\text{ V}}</math></p> <p>(c) <math>P_{out} = \sqrt{3} \times 480 \times 1200 \times 0.8 = 798.6\text{ kW}</math> <math>P_{in} = P_{out} + P_{Cu} + P_{core} + P_{fw}</math>  <math>P_{Cu} = 3 \times 692.8^2 \times 0.015 = 21.6\text{ kW}</math> <math>P_{in} = 798.6 + 21.6 + 30 + 40 = 890.2\text{ kW}</math>  <math>\eta = \frac{798.6}{890.2} = \boxed{89.7\%}</math></p>
SECTION F — SYNCHRONOUS MOTOR		
L5 Sync	<p><b>Q39.</b> A 208 V, 45 kVA, <math>\Delta</math>-connected, 60 Hz synchronous motor: <math>X_S=2.5\ \Omega</math>, <math>R_A=0</math>. Losses: <math>P_{fw}=1.5\text{ kW}</math>, <math>P_{core}=1.0\text{ kW}</math>. Shaft load=15 hp at PF=0.80 leading.</p> <p>Find <math>I_A</math>, <math>I_{Line}</math>, <math>E_A</math>.</p>	<p><b>A39.</b></p> $P_{in} = 15 \times 746 + 1500 + 1000 = 13690\text{ W} \quad V_\phi = 208\text{ V} (\Delta)$ $I_A = \frac{13690}{3 \times 208 \times 0.80} = 27.4\text{ A} \text{ leading} \rightarrow I_A = 27.4 \angle +36.87^\circ$ $I_{Line} = \sqrt{3} \times 27.4 = \boxed{47.5\text{ A}}$ $E_A = 208 - j2.5 \times 27.4 \angle 36.87^\circ = 208 - 68.5 \angle 126.87^\circ = 208 + 41.1 - j54.8 = 249.1 - j54.8$ $ E_A  = \sqrt{249.1^2 + 54.8^2} = \boxed{255.1\text{ V}} \quad (>V_\phi \rightarrow \text{consistent with leading/overexcited})$
L5 Sync	<p><b>Q40.</b> Using Q39 motor (<math> E_A =255.1\text{ V}</math> fixed). Shaft load increases to <b>30 hp</b>. Find new <math>\delta</math>, <math>I_A</math>, <math>I_{Line}</math>, and power factor.</p>	<p><b>A40.</b></p> $P_{new} = 30 \times 746 + 2500 = 24880\text{ W} \quad \sin\delta_{new} = \frac{P_{new} \times X_S}{3V_\phi  E_A } = \frac{24880 \times 2.5}{3 \times 208 \times 255.1} = 0.391 \rightarrow \delta = \boxed{23.0^\circ}$ $E_{A,new} = 255.1 \angle -23.0^\circ = 234.8 - j99.7$ $I_{A,new} = \frac{208 - (234.8 - j99.7)}{j2.5} = \frac{-26.8 + j99.7}{j2.5} = 39.9 + j10.7$ $ I_{A,new}  = \boxed{41.3\text{ A}} \quad I_{Line} = \boxed{71.5\text{ A}} \quad \text{PF} = \cos(\arctan(10.7/39.9)) = \boxed{0.966\text{ leading}}$

L5 Sync	<p><b>Q41.</b> A 208 V, 45 kVA, Δ-connected motor (<math>X_S=2.5\ \Omega</math>). Shaft=15 hp, PF=0.85 lagging initially. Field current then <b>increased by 25%</b> (<math>E_A</math> increases 25%). Find new <math>I_A</math> and PF after field increase.</p>	<p><b>A41.</b></p> <p><math>P_{in}=13690\text{ W}</math>, <math>I_{A,old}=13690/(3\times 208\times 0.85)=25.8\text{ A}\angle -31.79^\circ</math></p> <p><math>E_{A,old}=208-j2.5\times 25.8\angle -31.79^\circ=174.0-j54.8\rightarrow  E_{A,old} =182.4\text{ V}</math></p> <p><math>E_{A,new}=1.25\times 182.4=228.0\text{ V}</math>. P const <math>\rightarrow E_A\sin\delta=54.8</math> const</p> <p><math>\sin\delta_{new}=54.8/228.0=0.2404\rightarrow \delta_{new}=13.9^\circ\rightarrow E_{A,new}=228.0\angle -13.9^\circ=221.3-j54.8</math></p> <p><math>I_{A,new}=\frac{208-(221.3-j54.8)}{j2.5}=21.9+j5.3\rightarrow  I_{A,new} =\mathbf{22.5\text{ A}}</math> PF=<math>\mathbf{0.972\text{ leading}}</math></p> <p><i>PF shifted from 0.85 lagging <math>\rightarrow</math> 0.972 leading by increasing field current 25%. Motor now supplies Q to grid.</i></p>
L5 Sync	<p><b>Q42.</b> A 380 V, 60 Hz, 4-pole, Y-connected synchronous motor draws 30 A at unity PF (lossless).</p> <p>(a) Find output torque</p> <p>(b) To change PF to 0.8 leading — increase or decrease <math>I_F</math>? Explain with phasor reasoning.</p> <p>(c) Find new <math>I_L</math> at 0.8 leading PF.</p>	<p><b>A42.</b></p> <p>(a) <math>P=\sqrt{3}\times 380\times 30\times 1.0=19752\text{ W}</math> <math>\omega_m=2\pi\times 1800/60=60\pi\text{ rad/s}</math> <math>\tau=19752/(60\pi)=\mathbf{104.8\text{ N}\cdot\text{m}}</math></p> <p>(b) <b>Increase <math>I_F</math>.</b> At unity PF, <math>I_A</math> is in phase with <math>V_\phi</math> and <math>E_A\sin\delta</math> is fixed by load power. Increasing <math>I_F\rightarrow</math> increases <math> E_A </math> while <math>E_A\sin\delta=\text{constant}\rightarrow\delta</math> decreases. From motor KVL <math>E_A=V_\phi-jX_S I_A</math>: larger <math> E_A </math> with smaller <math>\delta</math> forces <math>I_A</math> to rotate toward leading. The machine becomes overexcited.</p> <p>(c) <math>I_{L,new}=\frac{P}{\sqrt{3}\times V_L\times \text{PF}}=\frac{19752}{\sqrt{3}\times 380\times 0.8}=\mathbf{37.5\text{ A}}</math></p>
L5 Sync	<p><b>Q43.</b> A 3.3 kV, Y-connected synchronous motor: <math>X_S=5\ \Omega</math>, <math>R_A\approx 0</math>. At rated load, <math>\delta=30^\circ</math>, <math> E_A =2400\text{ V}</math>.</p> <p>(a) Find the real power P developed per phase</p> <p>(b) Find the pull-out torque (<math>n_s=1000\text{ rpm}</math>, 6-pole, 50 Hz)</p> <p>(c) How much safety margin does the current operating point have before pull-out?</p>	<p><b>A43.</b></p> <p><math>V_\phi=3300/\sqrt{3}=1905\text{ V}</math> <math>\omega_m=2\pi\times 1000/60=104.7\text{ rad/s}</math></p> <p>(a) <math>P_{\text{phase}}=\frac{V_\phi E_A \sin\delta}{X_S}=\frac{1905\times 2400\times \sin 30^\circ}{5}=\frac{1905\times 2400\times 0.5}{5}=\mathbf{457.2\text{ kW/phase}}</math></p> <p>Total <math>P=3\times 457.2=1371.6\text{ kW}</math></p> <p>(b) <math>\tau_{\text{max}}=\frac{3V_\phi E_A}{X_S \omega_m}=\frac{3\times 1905\times 2400}{5\times 104.7}=\mathbf{26.19\text{ kN}\cdot\text{m}}</math></p> <p>(c) Current torque <math>\tau=P_{\text{total}}/\omega_m=1371600/104.7=13.1\text{ kN}\cdot\text{m}</math></p> <p>Safety margin=<math>\tau_{\text{max}}/\tau=26.19/13.1=\mathbf{2.0\times (100\%\text{ margin — very safe})}</math></p>
SECTION G — INDUCTION MACHINE CALCULATIONS		
L6 IM	<p><b>Q44.</b> A 208 V, 10 hp, 4-pole, 60 Hz, Y-connected induction motor, full-load slip=5%. Find: (a) <math>n_s</math>, (b) <math>n_m</math>, (c) <math>f_r</math>, (d) shaft torque <math>\tau_{\text{shaft}}</math></p>	<p><b>A44.</b></p> <p>(a) <math>n_s=120\times 60/4=\mathbf{1800\text{ rpm}}</math> (b) <math>n_m=(1-0.05)\times 1800=\mathbf{1710\text{ rpm}}</math></p> <p>(c) <math>f_r=0.05\times 60=\mathbf{3\text{ Hz}}</math> (d) <math>\omega_m=2\pi\times 1710/60=179.1\text{ rad/s}</math> <math>\tau=7460/179.1=\mathbf{41.7\text{ N}\cdot\text{m}}</math></p>
L6 IM	<p><b>Q45.</b> A 380 V, 4-pole, 50 Hz, Y-connected, 80 hp induction motor: <math>R_1=0.10\ \Omega</math>, <math>R_2=0.07\ \Omega</math>, <math>X_M=10\ \Omega</math>, <math>X_1=X_2=0.21\ \Omega</math>, <math>P_{\text{mech}}=1.5\text{ kW}</math>, <math>P_{\text{core}}=1.0\text{ kW}</math>. Slip <math>s=0.10</math>. Find <math>I_L</math>, PF, <math>P_{AG}</math>, <math>\tau_{\text{ind}}</math>, <math>P_{\text{conv}}</math>, <math>P_{\text{out}}</math>, <math>\tau_{\text{load}}</math>, <math>\eta</math>, and rotor speed.</p>	<p><b>A45.</b></p> <p><math>n_s=1500\text{ rpm}</math>, <math>\omega_s=50\pi\text{ rad/s}</math>, <math>n_m=1350\text{ rpm}</math>, <math>\omega_m=45\pi\text{ rad/s}</math>, <math>V_\phi=220\text{ V}</math></p> <p><math>Z_F=j10\parallel(0.7+j0.21)=0.668+j0.252</math> <math>Z_{\text{total}}=0.768+j0.462</math> <math> Z_{\text{total}} =0.896\ \Omega</math></p> <p><math>I_L=220/0.896=\mathbf{245\text{ A}}</math> PF=<math>\cos(\arctan(0.462/0.768))=\mathbf{0.857\text{ lag}}</math></p> <p><math>P_{in}=3\times 220\times 245\times 0.857=139\text{ kW}</math> <math>P_{\text{SCL}}=3\times 245^2\times 0.10=18.0\text{ kW}</math></p> <p><math>P_{AG}=139-18=\mathbf{120\text{ kW}}</math> <math>\tau_{\text{ind}}=120000/(50\pi)=\mathbf{764\text{ N}\cdot\text{m}}</math></p> <p><math>P_{\text{conv}}=0.9\times 120=\mathbf{108\text{ kW}}</math> <math>P_{\text{out}}=108-1.5=\mathbf{106.5\text{ kW}}</math> <math>\tau_{\text{load}}=106500/(45\pi)=\mathbf{753\text{ N}\cdot\text{m}}</math></p> <p><math>\eta=106.5/139=\mathbf{76.6\%}</math></p>

L6 IM	<p><b>Q46.</b> A 480 V, 60 Hz, 50 hp induction motor draws 60 A at 0.85 PF lagging. Known losses: <math>P_{SCL}=2</math> kW, <math>P_{RCL}=700</math> W, <math>P_{fw}=600</math> W, <math>P_{core}=1800</math> W. Find: (a) <math>P_{AG}</math>, (b) slip s, (c) <math>P_{conv}</math>, (d) <math>P_{out}</math>, (e) <math>\eta</math>.</p>	<p><b>A46.</b></p> $P_{in} = \sqrt{3} \times 480 \times 60 \times 0.85 = 42,416 \text{ W}$ <p>(a) <math>P_{AG} = 42416 - 2000 - 1800 = \boxed{38,616 \text{ W}}</math></p> <p>(b) <math>s = P_{RCL} / P_{AG} = 700 / 38616 = \boxed{1.81\%}</math></p> <p>(c) <math>P_{conv} = (1 - 0.0181) \times 38616 = \boxed{37,916 \text{ W}}</math></p> <p>(d) <math>P_{out} = 37916 - 600 = \boxed{37,316 \text{ W} \approx 50.0 \text{ hp} \checkmark}</math></p> <p>(e) <math>\eta = 37316 / 42416 = \boxed{88.0\%}</math></p>
L6 IM	<p><b>Q47.</b> A 460 V, 25 hp, 60 Hz, 4-pole, Y-connected wound-rotor IM: <math>R_1=0.641 \Omega</math>, <math>R_2=0.332 \Omega</math>, <math>X_1=1.106 \Omega</math>, <math>X_2=0.464 \Omega</math>, <math>X_M=26.3 \Omega</math>, <math>P_{rot}=1100</math> W. Find: (a) <math>s_{max}</math> and speed at max torque, (b) <math>\tau_{max}</math>, (c) starting torque at <math>s=1</math>.</p>	<p><b>A47.</b></p> $V_\phi = 265.6 \text{ V}, \omega_s = 60\pi = 188.5 \text{ rad/s}, V_{TH} = 265.6 \times 26.3 / 27.406 = 254.9 \text{ V}, R_{TH} = 0.591 \Omega, X_{TH} = 1.106 \Omega$ <p>(a) <math>s_{max} = \frac{0.332}{\sqrt{0.591^2 + 1.570^2}} = \frac{0.332}{1.677} = \boxed{0.198}</math> <math>n_{max} = (1 - 0.198) \times 1800 = \boxed{1444 \text{ rpm}}</math></p> <p>(b) <math>\tau_{max} = \frac{3 \times 254.9^2}{2 \times 188.5 \times (0.591 + 1.677)} = \frac{194960}{855.5} = \boxed{228 \text{ N}\cdot\text{m}}</math></p> <p>(c) <math>\tau_{start} = \frac{3 \times 254.9^2 \times 0.332}{188.5 \times [(0.591 + 0.332)^2 + 1.570^2]} = \frac{64732}{625} = \boxed{104 \text{ N}\cdot\text{m}}</math></p>
L6 IM	<p><b>Q48.</b> For the motor in Q47: rotor resistance doubled (<math>R_2=0.664 \Omega</math>, external resistance inserted via slip rings). (a) New <math>s_{max}</math> and speed? (b) New <math>\tau_{max}</math>? (c) New starting torque? (d) State the general rules for <math>R_2</math>'s effect on induction motor performance.</p>	<p><b>A48.</b></p> <p>(a) <math>s_{max} \propto R_2 \rightarrow s_{max,new} = 2 \times 0.198 = \boxed{0.396}</math> <math>n = (1 - 0.396) \times 1800 = \boxed{1087 \text{ rpm}}</math></p> <p>(b) <math>\tau_{max}</math> independent of <math>R_2 \rightarrow \boxed{228 \text{ N}\cdot\text{m (unchanged)}}</math></p> <p>(c) <math>\tau_{start,new} = \frac{3 \times 254.9^2 \times 0.664}{188.5 \times [(0.591 + 0.664)^2 + 1.570^2]} = \frac{129461}{761} = \boxed{170 \text{ N}\cdot\text{m} \uparrow}</math></p> <p>(d) Rules:</p> <ul style="list-style-type: none"> <li><math>s_{max} = \frac{R_2}{\sqrt{R_{TH}^2 + (X_{TH} + X_2)^2}}</math> — directly proportional to <math>R_2</math></li> <li><math>\tau_{max}</math> — completely independent of <math>R_2</math></li> <li><math>\tau_{start}</math> increases as <math>R_2</math> increases, reaching maximum when <math>s_{max}=1</math> (i.e. <math>R_2 = \sqrt{R_{TH}^2 + (X_{TH} + X_2)^2}</math>)</li> <li>Higher <math>R_2 \rightarrow</math> lower efficiency (more rotor copper loss at same slip)</li> </ul>
L6 IM	<p><b>Q49.</b> A 7.5 hp, 4-pole, 208 V, 60 Hz, Y-connected induction motor (rated 28 A) is tested:  DC: <math>V_{DC}=13.6</math> V, <math>I_{DC}=28</math> A  No-load: <math>V_T=208</math> V, <math>I_A=8.17</math> A, <math>P_{NL}=420</math> W  LR test: <math>V_T=25</math> V, <math>I_A=28</math> A, <math>P_{LR}=920</math> W, <math>f_{test}=15</math> Hz  Find <math>R_1</math>, <math>R_2</math>, <math>X_1</math>, <math>X_2</math>, <math>X_M</math> and compute <math>\tau_{max}</math>.</p>	<p><b>A49.</b></p> $R_1 = 13.6 / (2 \times 28) = \boxed{0.243 \Omega}$ $X_1 + X_M \approx 120.1 / 8.17 = 14.7 \Omega \rightarrow \boxed{X_M \approx 14.7 \Omega}$ $R_{LR} = 920 / (3 \times 28^2) = 0.391 \Omega \quad Z_{LR} = (25 / \sqrt{3}) / 28 = 0.516 \Omega \quad X_{LR,15\text{Hz}} = \sqrt{0.516^2 - 0.391^2} = 0.334 \Omega$ $X_{LR,60\text{Hz}} = 0.334 \times (60 / 15) = 1.336 \Omega \rightarrow X_1 = X_2 = \boxed{0.668 \Omega} \text{ (Design A, equal split)}$ $R_2 = 0.391 - 0.243 = \boxed{0.148 \Omega}$ $V_{TH} = 114.8 \text{ V}, R_{TH} = 0.203 \Omega, s_{max} = 0.148 / 1.367 = 0.108$ $\tau_{max} = 3 \times 114.8^2 / [2 \times (60\pi)(0.203 + 1.367)] = \boxed{66.8 \text{ N}\cdot\text{m}}$

L6 IM

**Q50.** A 415 V, 50 Hz, 4-pole, 3-phase induction motor runs at full load. Supply voltage suddenly drops to **0.9×415 V** (10% voltage sag).

(a) What happens to the maximum torque capability?

(b) If the load demands rated torque, what happens to the motor?

(c) Quantify the change in  $\tau_{\max}$  and explain using the formula.

L6 IM

**Q51.** Motor classes for design induction motors: briefly describe Classes **A, B, C, D** in terms of starting torque, starting current, and slip. Give one application for each.

L6 IM

**Q52.** A wound-rotor induction motor has the Thevenin circuit equivalent:  $V_{TH}$ =200 V,  $R_{TH}$ =0.3  $\Omega$ ,  $X_{TH}$ =1.0  $\Omega$ ,  $X_2$ =0.5  $\Omega$ ,  $R_2$ =0.2  $\Omega$ ,  $\omega_s$ =188.5 rad/s.

(a) Find  $R_{ext}$  needed for **maximum starting torque** ( $s_{\max}$ =1)

(b) Verify by computing starting torque with and without  $R_{ext}$

**A50.**

(a) From  $\tau_{\max}$  formula:  $\tau_{\max} \propto V_{TH}^2 \propto V_1^2$ :

$$\tau_{\max, new} = \tau_{\max, old} \times (0.9)^2 = 0.81 \times \tau_{\max, old}$$

→ **19% reduction in  $\tau_{\max}$**

(b) If load still requires rated torque  $T_{rated}$ , and  $\tau_{\max}$  dropped to  $0.81 \times \tau_{\max, old}$ : as long as  $\tau_{rated} < \tau_{\max, new}$ , the motor continues running but at **higher slip** (operating point moves down-left on torque-speed curve toward the peak). If  $\tau_{rated} > \tau_{\max, new}$ , the motor cannot produce enough torque → it **stalls (pulls out)**.

(c) The formula shows  $\tau_{\max} = 3V_{TH}^2/[2\omega_s(R_{TH} + \dots)]$  — numerator has  $V_{TH}^2 \propto V_{supply}^2$ . Doubling voltage would quadruple  $\tau_{\max}$ ; reducing by 10% reduces by 19%.

*This is why voltage sags during motor starting of large motors can stall neighbouring motors on the same bus. Also why voltage support (capacitor banks, synchronous condensers) is critical in industrial plants.*

**A51.**

Class	Starting Torque	Starting Current	Full-load Slip	Application
A	Normal (100–150%)	High (6–7× $I_{rated}$ )	Low (<5%)	Fans, centrifugal pumps, compressors — low inertia, quick start
B	Normal (≥150%)	Lower (≤5× $I_{rated}$ )	Normal (≤5%)	Machine tools, large fans, conveyor drives — where starting current matters
C	High (≥200%)	Low (≤5× $I_{rated}$ )	Normal	Crushers, reciprocating compressors, refrigeration — heavy starting loads
D	Very high (≥275%)	Low	High (5–20%)	Punch presses, bulldozers, shearing machines — shock loads; high-slip for energy storage in flywheel

*Class A/B:  $R_2$  low →  $s_{\max}$  near 0 → efficient, runs near sync speed. Class D:  $R_2$  high →  $s_{\max}$  near 1 → high starting torque, runs at high slip (low speed, less efficient).*

**A52.**

(a) For  $s_{\max}$ =1:  $R_2 + R_{ext} = \sqrt{R_{TH}^2 + (X_{TH} + X_2)^2}$ :

$$\sqrt{0.3^2 + (1.0 + 0.5)^2} = \sqrt{0.09 + 2.25} = \sqrt{2.34} = 1.530 \Omega$$
$$R_{ext} = 1.530 - R_2 = 1.530 - 0.200 = \textbf{1.330 \Omega per phase}$$

(b) Without  $R_{ext}$  ( $R_2$ =0.2,  $s$ =1):

$$\tau_{start} = \frac{3 \times 200^2 \times 0.2}{188.5 \times [(0.3 + 0.2)^2 + 1.5^2]} = \frac{24000}{188.5 \times 2.5} = \textbf{50.8 N \cdot m}$$

With  $R_{ext}$  (total  $R$ =1.530  $\Omega$ ,  $s$ =1):

$$\tau_{start, ext} = \frac{3 \times 200^2 \times 1.530}{188.5 \times [(0.3 + 1.530)^2 + 1.5^2]} = \frac{183600}{188.5 \times (3.348 + 2.25)} = \frac{183600}{1055.0} = \textbf{174 N \cdot m \uparrow 3.4\times}$$

L7 Special

53. A universal motor (series DC motor on AC):  $V_s=200\text{ V}_{\text{rms}}$ , 50 Hz,  $R_a=0.4\text{ }\Omega$ ,  $L_a=3\text{ mH}$ ,  $R_f=0.8\text{ }\Omega$ ,  $L_f=6\text{ mH}$ . Full load:  $I_a=10\text{ A}$ ,  $n=1000\text{ rpm}$ . At half torque: find new  $I_a$  and speed.

A53.

$X_{\text{total}}=2\pi\times50\times9\times10^{-3}=2.827\text{ }\Omega$     $R_{\text{total}}=1.2\text{ }\Omega$     $\omega_m=104.7\text{ rad/s}$

$200^2=(E_a+10\times1.2)^2+(10\times2.827)^2 \rightarrow E_a=\boxed{186\text{ V}}$     $K_eK_f=186/(10\times104.7)=0.1776$

Half torque:  $\tau\propto I_a^2 \rightarrow I_{a,\text{new}}=10/\sqrt{2}=\boxed{7.07\text{ A}}$

$200^2=(E_{a,\text{new}}+8.48)^2+399.6 \rightarrow E_{a,\text{new}}=190.5\text{ V}$

$\omega_{\text{new}}=190.5/(0.1776\times7.07)=\boxed{151.8\text{ rad/s} \rightarrow 1449\text{ rpm}}$

L7 Special

54. Describe the **120° conduction pattern** of a BLDC motor with a 3-phase inverter. Which upper and lower switches conduct in each of the 6 commutation intervals? Why is this called "brushless DC"?

A54.

The 3-phase inverter has 3 upper switches (S1, S3, S5) and 3 lower switches (S2, S4, S6). Hall sensors detect rotor position in 60° steps → 6 commutation intervals per electrical cycle. In each interval, exactly **one upper + one lower switch** conducts (always one from different phases):

Interval	Upper	Lower	Phases conducting
I (0–60°)	S1 (A)	S6 (B)	A → B (C open)
II (60–120°)	S1 (A)	S2 (C)	A → C (B open)
III (120–180°)	S3 (B)	S2 (C)	B → C (A open)
IV (180–240°)	S3 (B)	S4 (A)	B → A (C open)
V (240–300°)	S5 (C)	S4 (A)	C → A (B open)
VI (300–360°)	S5 (C)	S6 (B)	C → B (A open)

Each device conducts for 120° per cycle. **Called "brushless DC"** because: the DC source delivers a constant DC current to the two active phases at any moment (like a DC motor); from the battery's perspective, DC current is drawn and commutation is electronic (not mechanical). DC motor equations ( $E_a=k\omega$ ,  $\tau=kl$ ) apply at any instant.

L7 Special

55. Explain why a **single-phase induction motor** produces no starting torque. Then explain how **capacitor-start** and **shaded-pole** methods solve this problem.

A55.

**No starting torque — double revolving field theory:** A single-phase alternating current creates an alternating (pulsating) magnetic field, not a rotating one. This pulsating field can be mathematically decomposed into two equal counter-rotating fields of half magnitude. One rotates at  $+\omega_s$ , the other at  $-\omega_s$ . At standstill, both fields create equal and opposite torques that cancel exactly → net starting torque = 0. Once rotating, the field in the direction of rotation becomes dominant and the motor accelerates.

**Capacitor-start method:** An auxiliary winding is placed 90° (in space) from the main winding. A series capacitor shifts the auxiliary winding current  $\approx 90^\circ$  in time from the main winding current. Two currents 90° apart in space AND time → approximate rotating magnetic field → starting torque. A centrifugal switch disconnects the auxiliary winding at  $\sim 75\%$  rated speed.

**Shaded-pole method:** A copper short-circuit ring is placed over part of each salient stator pole. The ring acts as a shorted secondary — it carries an induced current that opposes the changing flux in its portion of the pole, causing that part's flux to lag behind the unshaded portion's flux. This creates a "sweeping" field from unshaded to shaded region → weak rotating field → small starting torque. Simplest and cheapest; efficiency is low; used for very small motors (fans, clocks).



L7 Special

Mixed

L5 Sync

<p><b>56.</b> Describe the <b>SRM (Switched Reluctance Machine)</b> energy conversion cycle using the inductance <math>L(\theta)</math> curve. Why must the phase current be switched off before full alignment? What is the consequence of late switching?</p>	<p><b>A56.</b></p> <p><b>Energy conversion using <math>L(\theta)</math>:</b> The inductance of one stator phase varies with rotor position — minimum when poles are unaligned, maximum when fully aligned. The torque is:</p> $\tau = \frac{1}{2} \cdot I^2 \cdot \frac{dL}{d\theta}$ <p>When the phase is energised at an unaligned position and <math>dL/d\theta &gt; 0</math> (inductance increasing), torque is positive (motoring). When <math>dL/d\theta &lt; 0</math> (inductance decreasing — rotor past aligned position), torque would be negative (braking/ generating).</p> <p><b>Must switch off before full alignment:</b> If current remains on past the aligned position, <math>dL/d\theta</math> becomes negative → torque reverses direction → the motor fights itself, wasting energy and causing torque ripple and backward impulses.</p> <p><b>Consequence of late switching:</b> The rotor continues past alignment with current still flowing → negative (braking) torque pulse. This increases torque ripple and reduces average torque and efficiency. In worst case, motor can fail to rotate or reverse. The commutation advance angle must be optimised for each speed (firing angle control).</p>
SECTION I — ANALYSIS, DERIVATION & TRUE/FALSE	
<p><b>Q57.</b> State whether each of the following is TRUE or FALSE and justify briefly:</p> <p>(a) A DC series motor can be safely operated with no mechanical load.</p> <p>(b) Increasing <math>R_2</math> in an induction motor increases its maximum torque.</p> <p>(c) An overexcited synchronous motor supplies reactive power to the grid.</p> <p>(d) The air-gap power <math>P_{AG} = \tau_{ind} \cdot \omega_s</math>.</p> <p>(e) A synchronous motor can start direct-on-line.</p> <p>(f) Swapping any two supply phases of a 3-phase induction motor reverses its direction.</p> <p>(g) The back-EMF in a BLDC motor is sinusoidal.</p> <p>(h) Fractional-pitch windings reduce both fundamental voltage and harmonic voltages.</p>	<p><b>A57.</b></p> <p>(a) <b>FALSE</b> — <math>\Phi \propto I_a</math>: no load → <math>I_a \rightarrow 0 \rightarrow \Phi \rightarrow 0 \rightarrow \text{speed} \rightarrow \infty</math>. Mechanically catastrophic.</p> <p>(b) <b>FALSE</b> — <math>\tau_{max}</math> is independent of <math>R_2</math>. Only <math>s_{max}</math> shifts proportionally to <math>R_2</math>.</p> <p>(c) <b>TRUE</b> — Overexcited: <math>I_A</math> leads <math>V_\phi \rightarrow</math> motor acts as capacitive load → supplies Q (reactive power) to grid. Used as synchronous condenser for power factor correction.</p> <p>(d) <b>TRUE</b> — By definition: <math>P_{AG}</math> is the power transferred across air gap = <math>\tau_{ind} \cdot \omega_s</math>. Note <math>P_{conv} = \tau_{ind} \cdot \omega_m \neq P_{AG}</math>.</p> <p>(e) <b>FALSE</b> — Cannot start DOL. Average starting torque = 0 because the stator field reverses torque direction twice per cycle at standstill.</p> <p>(f) <b>TRUE</b> — Swapping 2 phases reverses the rotation direction of the stator's rotating magnetic field, reversing the motor.</p> <p>(g) <b>FALSE</b> — BLDC has trapezoidal back-EMF (concentrated windings). Sinusoidal back-EMF is characteristic of distributed-winding synchronous AC motors.</p> <p>(h) <b>PARTIALLY TRUE</b> — Fractional pitch reduces fundamental by factor <math>k_p &lt; 1</math>, but reduces harmonic voltages much more (harmonic pitch factors are much smaller). Net effect is improved waveform quality.</p>
<p><b>Q58.</b> A synchronous machine: <math>X_S=1\ \Omega</math>, <math>R_A=0</math>, <math>V_\phi=240\text{ V}\angle 0^\circ</math>, <math> E_A =280\text{ V}</math>, <math>\delta=30^\circ</math>.</p> <p>(a) Motor or generator? Why?</p> <p>(b) Find P and Q per phase</p> <p>(c) Over- or underexcited? Justify.</p>	<p><b>A58.</b></p> <p>(a) <math>\delta=30^\circ</math> with <math>E_A</math> defined as <math>E_A\angle\delta</math>: if <math>E_A</math> leads <math>V_\phi \rightarrow</math> <b>generator</b> (<math>E_A</math> ahead → pushes current out). If <math>E_A</math> lags <math>V_\phi \rightarrow</math> motor. At <math>\delta=+30^\circ</math> (<math>E_A</math> leads) → <b>Generator</b>.</p> <p>(b) <math>P_{\text{phase}} = \frac{V_\phi E_A \sin\delta}{X_S} = \frac{240 \times 280 \times 0.5}{1} = \boxed{33,600\text{ W/phase}}</math>    <math>P_{3\phi} = 100.8\text{ kW}</math></p> $I_A = \frac{E_A\angle 30^\circ - V_\phi\angle 0^\circ}{jX_S} = \frac{280(\cos 30^\circ + j\sin 30^\circ) - 240}{j} = \frac{242.5 + j140 - 240}{j} = \frac{2.5 + j140}{j} = 140 - j2.5\text{ A}$ <p><math>Q_{\text{phase}} = V_\phi I_A \sin\theta = 240 \times 2.5 = \boxed{600\text{ VAR/phase (positive, supplies Q)}}</math></p> <p>(c) <math> E_A  \cos \delta = 280 \times \cos 30^\circ = 242.5\text{ V} &gt; V_\phi = 240\text{ V} \rightarrow</math> <b>Overexcited generator</b> (supplies reactive power to grid).</p>

L3 DC

L6 IM

L6 IM

<p><b>Q59. Derive</b> the torque-speed equation for a series DC motor from first principles, showing that torque <math>\propto (1/\text{speed})^2</math> for constant supply voltage.</p>	<p><b>A59.</b></p> <p>For series motor: <math>I_f=I_a=I</math>, and <math>\Phi=K_f I</math>. Starting from:</p> $V_T = E_a + I(R_a + R_f) = K_e K_f I \omega_m + I \cdot R_s$ $\tau = K_e \Phi I = K_e K_f I^2 \rightarrow I = \sqrt{\frac{\tau}{K_e K_f}}$ <p>Substitute into KVL:</p> $V_T = K_e K_f \sqrt{\frac{\tau}{K_e K_f}} \cdot \omega_m + R_s \cdot \sqrt{\frac{\tau}{K_e K_f}}$ $\omega_m = \frac{V_T}{\sqrt{K_e K_f \tau}} - \frac{R_s}{K_e K_f}$ <p>So for large <math>\tau</math> (ignoring <math>R_s</math> term): <math>\omega_m \propto 1/\tau \rightarrow \tau \propto 1/\omega_m^2</math>. This is the hyperbolic torque-speed characteristic of series motor — huge torque at low speed, very high speed at low torque.</p> <p><i>This means <math>\tau \propto I_a^2</math> (best starting torque per amp) but <math>\omega \rightarrow \infty</math> as <math>\tau \rightarrow 0</math>. Applications: traction drives, cranes — loads that always have torque when running.</i></p>
<p><b>Q60.</b> What happens if a running induction motor is <b>plugged</b> (two supply phases are swapped while motor runs at rated speed)?</p> <p>(a) Explain what happens to slip and the direction of torque immediately after plugging.</p> <p>(b) Why is plugging used in practice despite being stressful on the motor?</p> <p>(c) Compare braking current during plugging vs normal starting.</p>	<p><b>A60.</b></p> <p>(a) Before plugging: motor runs at <math>n_m \approx (1-0.03)n_s = 0.97n_s</math> in the forward direction. After phase swap, the stator field now rotates at <math>-n_s</math> (reverse direction). Relative speed of rotor to stator field = <math>n_m - (-n_s) = n_m + n_s \approx 1.97n_s</math>. New effective slip:</p> $s_{\text{plug}} = \frac{n_s - n_m}{n_s} = \frac{-n_s - (+n_m)}{-n_s} = \frac{n_s + n_m}{n_s} \approx 2 - s_{\text{rated}} \approx \boxed{1.97}$ <p>The induced torque is now <b>in the reverse direction</b> — opposing the forward motion. The motor decelerates rapidly. A relay or controller must disconnect the motor once it reaches zero speed (otherwise it will restart in reverse).</p> <p>(b) <b>Plugging</b> gives the fastest stopping time — deceleration torque is 1.5–2× the accelerating torque. Used in machine tools, hoists, and positioning systems where rapid stop is required. Much faster than coasting or DC injection braking for high-inertia loads.</p> <p>(c) Plugging current <math>\approx 2\times</math> starting current (since effective voltage across circuit is <math>\approx 2V_T</math> at <math>s=2</math>). Very high thermal stress — plugging is only used intermittently and motor must be rated for it. Starting current <math>\approx 6\times I_{\text{rated}}</math>, plugging current <math>\approx 10\text{--}12\times I_{\text{rated}}</math>.</p>
<p><b>Q61.</b> A 3-phase, 4-pole, 50 Hz induction motor measured at steady state:</p> <p><math>P_{\text{in}}=40\text{ kW}</math>, <math>P_{\text{SCL}}=1.5\text{ kW}</math>, <math>P_{\text{core}}=0.5\text{ kW}</math>, <math>P_{\text{RCL}}=1.9\text{ kW}</math>, <math>P_{\text{fw}}=0.6\text{ kW}</math>.</p> <p>Find: (a) slip, (b) <math>n_m</math>, (c) <math>P_{\text{out}}</math>, (d) <math>\eta</math>, (e) <math>\tau_{\text{ind}}</math>, (f) <math>\tau_{\text{load}}</math>.</p>	<p><b>A61.</b></p> <p>(a) <math>P_{\text{AG}}=40-1.5-0.5=38\text{ kW}</math> <math>s=P_{\text{RCL}}/P_{\text{AG}}=1.9/38=\boxed{5.0\%}</math></p> <p>(b) <math>n_s=1500\text{ rpm}</math> <math>n_m=(1-0.05)\times 1500=\boxed{1425\text{ rpm}}</math></p> <p>(c) <math>P_{\text{conv}}=(1-0.05)\times 38=36.1\text{ kW}</math> <math>P_{\text{out}}=36.1-0.6=\boxed{35.5\text{ kW (47.6 hp)}}</math></p> <p>(d) <math>\eta=35.5/40=\boxed{88.75\%}</math></p> <p>(e) <math>\omega_s=50\pi\text{ rad/s}</math> <math>\tau_{\text{ind}}=38000/(50\pi)=\boxed{241.7\text{ N}\cdot\text{m}}</math></p> <p>(f) <math>\omega_m=2\pi\times 1425/60=149.2\text{ rad/s}</math> <math>\tau_{\text{load}}=35500/149.2=\boxed{238.0\text{ N}\cdot\text{m}}</math></p>

L5 Sync	<p><b>Q62.</b> Explain the concept of the <b>brushless exciter</b> used in large synchronous generators. Why is it preferred over slip rings and brushes for large machines? Draw a block diagram description.</p>	<p><b>A62.</b></p> <p><b>Brushless exciter system block description:</b></p> <ol style="list-style-type: none"> <li><b>Pilot exciter</b> (small AC generator with PM rotor, on same shaft) → produces AC output regardless of external power.</li> <li><b>Main exciter</b> (AC generator: field on stator, armature on rotor shaft) → stator field current controlled by pilot exciter or AVR. Rotor armature produces AC at shaft rotation frequency.</li> <li><b>Rotating rectifier</b> (diode bridge, also on shaft) → rectifies main exciter AC output to DC.</li> <li><b>DC field current</b> → delivered directly to main synchronous generator field winding (also on shaft) — no slip rings or brushes needed anywhere.</li> </ol> <p><b>Why preferred for large machines:</b></p> <ul style="list-style-type: none"> <li>• Eliminates brush wear — no maintenance interruption for large machines in remote locations</li> <li>• No brush voltage drop (significant loss for large field currents, e.g. 1000 A × 2V brush drop = 2 kW)</li> <li>• No sparking in hazardous environments</li> <li>• More reliable — brushes can fail and short-circuit or open-circuit the field</li> <li>• Scalability — field current can be hundreds of amps without brush contact issues</li> </ul> <p><i>Slip rings are still used for small/medium synchronous machines where simplicity and cost matter more than maintenance reduction.</i></p>
L5 Sync	<p><b>Q63.</b> A 6-pole, 50 Hz, 3.3 kV, Y-connected synchronous motor drives a compressor at rated load. <math>X_S=8\ \Omega</math>, <math>R_A=0</math>. <math>P_{in}=2</math> MW at PF=0.9 lagging. (a) Find <math>I_A</math>, <math>E_A</math>, <math>\delta</math>. (b) The load is suddenly removed (<math>P \rightarrow 0</math>) but field maintained. What is the new armature current and PF?</p>	<p><b>A63.</b></p> <p><math>V_\phi = 3300/\sqrt{3} = 1905\text{ V}</math></p> <p>(a) <math>I_A = \frac{2 \times 10^6}{3 \times 1905 \times 0.9} = 389.9\text{ A} \angle -25.84^\circ</math> (lagging → motor underexcited)</p> <p><math>E_A = 1905 - j8 \times 389.9 \angle -25.84^\circ = 1905 - 3119 \angle 64.16^\circ = 1905 - (1357 + j2806) = 548 - j2806</math></p> <p><math> E_A  = \sqrt{548^2 + 2806^2} = \boxed{2859\text{ V}}</math>    <math>\delta = \tan^{-1}(2806/548) = \boxed{79.0^\circ \text{ (lagging } E_A \text{ : motor mode } \checkmark)}</math></p> <p>(b) Load removed → <math>P=0 \rightarrow E_A \sin \delta = 0 \rightarrow \delta = 0</math> (<math>E_A</math> aligns with <math>V_\phi</math>). <math> E_A =2859\text{ V}</math> maintained:</p> $I_{A,NL} = \frac{V_\phi - E_A \angle 0^\circ}{jX_S} = \frac{1905 - 2859}{j8} = \frac{-954}{j8} = j119.3\text{ A}$ <p><math> I_{A,NL}  = \boxed{119.3\text{ A}}</math>    Purely imaginary (j) → <b>PF=0 leading</b> (purely reactive, supplying Q to grid)</p> <p><i>With no real load, overexcited motor draws 119 A of purely leading reactive current — acting as a synchronous condenser. The 26% of rated current maintains a large reactive power supply to the grid.</i></p>
L6 IM	<p><b>Q64. Efficiency limit from slip:</b> Show that for an induction motor, the maximum possible efficiency is bounded by <math>\eta_{max} \leq (1-s) \times (P_{conv}/P_{AG})</math>. If slip=4%, friction/windage losses=2% of <math>P_{conv}</math>, and stator losses=8% of <math>P_{in}</math>, estimate overall efficiency.</p>	<p><b>A64.</b></p> <p><b>Derivation:</b></p> $P_{conv} = (1-s) \cdot P_{AG}$ $P_{out} = P_{conv} - P_{rot} \leq P_{conv} = (1-s)P_{AG} \leq (1-s)P_{in}$ $\eta = \frac{P_{out}}{P_{in}} \leq (1-s) \quad (\text{upper bound when all other losses} \rightarrow 0)$ <p><b>Numerical estimate:</b> <math>s=0.04 \rightarrow P_{conv}=0.96P_{AG}</math>. Let <math>P_{in}=100</math> units.</p> <p><math>P_{SCL}=8</math> units (stator)    <math>P_{core}=2</math> units (estimate)</p> <p><math>P_{AG}=100-8-2=90</math> units</p> <p><math>P_{RCL}=0.04 \times 90=3.6</math> units    <math>P_{conv}=0.96 \times 90=86.4</math> units</p> <p><math>P_{rot}=0.02 \times 86.4=1.73</math> units    <math>P_{out}=86.4-1.73=84.67</math> units</p> <p><math>\eta = 84.67/100 = \boxed{84.7\%}</math>    (bound from slip alone: <math>1-s=96\%</math>)</p> <p><i>Actual <math>\eta &lt; (1-s)</math> because stator losses, core losses, and rotational losses all further reduce output. The slip-based bound is tight only for small machines with dominant rotor losses.</i></p>

**Q65. Design question:** A factory has a 1 MW, 0.75 PF lagging induction motor load on a 11 kV bus. The utility charges a penalty for PF below 0.90 lagging. The factory wants to install a **synchronous motor** (rated 200 kW,  $X_S=2\ \Omega$  per phase, Y-connected, 11 kV) running overexcited to supply the needed reactive power. Find the required  $|E_A|$  of the synchronous motor.

**A65.**

**Step 1 — Find current reactive power absorbed by induction motors:**

$$P_{load}=1\text{ MW}\quad PF_{old}=0.75\text{ lag}\quad \theta_{old}=\cos^{-1}(0.75)=41.41^\circ$$
$$Q_{load}=P\tan\theta_{old}=1\times10^6\times\tan41.41^\circ=0.882\text{ MVAR (absorbed, lagging)}$$

**Step 2 — Required reactive power after PF correction to 0.90:**

$$\theta_{new}=\cos^{-1}(0.90)=25.84^\circ\quad Q_{required}=1\times10^6\times\tan25.84^\circ=0.484\text{ MVAR}$$

$$Q_{sync\text{ motor must supply}}=Q_{load}-Q_{required}=0.882-0.484=$$
 **0.398 MVAR leading**

**Step 3 — Find  $I_A$  of sync motor (200 kW real power + 398 kVAR leading):**

$$V_\phi=11000/\sqrt{3}=6351\text{ V}\quad I_A=\frac{P+jQ_{supply}}{3V_\phi}=\frac{200000+j398000}{3\times6351}=10.5+j20.9\text{ A}$$

(Leading current has positive imaginary part:  $I_A=10.5+j20.9\text{ A}$ ,  $|I_A|=23.4\text{ A}$ )

**Step 4 — Find  $E_A$ :**

$$E_A=V_\phi-jX_S\cdot I_A=6351-j2\times(10.5+j20.9)=6351-j21+41.8=6392.8-j21$$

$$|E_A|=\sqrt{6392.8^2+21^2}=$$
 **6392.8 V  $\approx$  6.39 kV per phase**  $\rightarrow$  Line:  $6.39\times\sqrt{3}=11.07\text{ kV}$

## 1. FUNDAMENTAL CONSTANTS & CONVERSIONS

$\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$  (permeability of free space)  
 $1 \text{ hp} = 746 \text{ W}$   
 $\omega \text{ [rad/s]} = 2\pi n \text{ [rpm]} / 60$   
 $n \text{ [rpm]} = 60\omega / (2\pi)$   
 $P = \tau \cdot \omega \text{ [W]}; \quad \tau = P / \omega \text{ [N}\cdot\text{m]}$   
 $\sqrt{2} \approx 1.4142; \quad \sqrt{3} \approx 1.7321; \quad \pi \approx 3.14159$

## 2. MAGNETIC CIRCUIT

**Ampere's Law:**  $\oint \mathbf{H} \cdot d\mathbf{l} = \sum i \rightarrow \mathbf{H} \cdot \mathbf{l}_c = N \cdot i$   
**B–H relation:**  $\mathbf{B} = \mu_0 \mu_r \cdot \mathbf{H} \text{ [T]}$   
**Flux:**  $\Phi = \mathbf{B} \cdot \mathbf{A} \text{ [Wb]}$   
**mmf:**  $\mathcal{F} = N \cdot i \text{ [A}\cdot\text{turns]}$   
**Reluctance:**  $\mathfrak{R} = l / (\mu_0 \mu_r \mathbf{A}) \text{ [A}\cdot\text{t/Wb]}$   
**Air gap:**  $\mathfrak{R}_g = g / (\mu_0 \mathbf{A}_g)$   
**Ohm's law:**  $\Phi = \mathcal{F} / \mathfrak{R} = N \cdot i / \mathfrak{R}$   
**Series:**  $\mathfrak{R}_{\text{total}} = \mathfrak{R}_1 + \mathfrak{R}_2 + \dots$  Parallel:  $1/\mathfrak{R}_{\text{total}} = \sum (1/\mathfrak{R}_k)$   
**Flux linkage:**  $\lambda = N \cdot \Phi \text{ [Wb}\cdot\text{turn}]$   
**Inductance:**  $L = \lambda / i = N^2 / \mathfrak{R} \text{ [H]}$   
**Faraday:**  $e = -N \cdot d\Phi / dt = L \cdot di / dt \text{ [V]}$   
**Moving bar:**  $e = \mathbf{B} \cdot \mathbf{L} \cdot \mathbf{v} \text{ [V]}; \quad \mathbf{F} = \mathbf{B} \cdot \mathbf{I} \cdot \mathbf{l} \text{ [N]}$   
**Energy:**  $W = \frac{1}{2} L i^2 = \frac{1}{2} \Phi^2 \mathfrak{R} = \frac{1}{2} B H (\text{Vol}) \text{ [J]}$   
**Hysteresis loss:**  $P_H = K_H \cdot f \cdot B_{\text{max}}^n$  ( $n \approx 1.6 - 2$ )  
**Eddy current loss:**  $P_E = K_E \cdot f^2 \cdot B_{\text{max}}^2$   
**Toroid:**  $B = \mu_0 \mu_r \cdot NI / (2\pi r)$   
**KCL analogue:**  $\sum \Phi = 0$  at any node  
**KVL analogue:**  $\sum (Ni) = \sum (\Phi \cdot \mathfrak{R})$  around loop

## 3. THREE-PHASE POWER & CONNECTIONS

**Y-connection:**  $V_L = \sqrt{3} \cdot V_\phi; \quad I_L = I_\phi$   
 **$\Delta$ -connection:**  $V_L = V_\phi; \quad I_L = \sqrt{3} \cdot I_\phi$   
**Real power:**  $P = \sqrt{3} \cdot V_L \cdot I_L \cdot \cos\theta = 3 \cdot V_\phi \cdot I_\phi \cdot \cos\theta \text{ [W]}$   
**Apparent power:**  $S = \sqrt{3} \cdot V_L \cdot I_L \text{ [VA]}$   
**Reactive power:**  $Q = S \cdot \sin\theta = P \cdot \tan\theta \text{ [VAR]}$   
**Power factor:**  $\text{PF} = \cos\theta = P / S$   
**Complex power:**  $\tilde{S} = P + jQ = \tilde{V} \cdot \tilde{I}^*$   
 Lagging PF: I lags V (inductive,  $Q > 0$  absorbed)  
 Leading PF: I leads V (capacitive,  $Q < 0$  or Q supplied)

## 4. SYNCHRONOUS SPEED

**Sync speed:**  $n_s = 120 \cdot f / P \text{ [rpm]}$  ( $P$  = number of poles)  
**Angular:**  $\omega_s = 4\pi f / P \text{ [rad/s]}$   
**Elec–mech angle:**  $\theta_e = (P/2) \cdot \theta_m$   
**Elec–mech freq:**  $f_e = (P/2) \cdot n / 60$   
**50 Hz table:**  $2P \rightarrow 3000, 4P \rightarrow 1500, 6P \rightarrow 1000, 8P \rightarrow 750, 20P \rightarrow 300 \text{ rpm}$   
**60 Hz table:**  $2P \rightarrow 3600, 4P \rightarrow 1800, 6P \rightarrow 1200, 8P \rightarrow 900 \text{ rpm}$

## 5. DC MACHINES

**Back-EMF:**  $E_a = K_e \cdot \Phi \cdot \omega_m \text{ [V]}$   
**Torque:**  $\tau = K_e \cdot \Phi \cdot I_a \text{ [N}\cdot\text{m]}$  (same  $K_e$ !)  
**Flux (linear):**  $\Phi = K_f \cdot I_f$   
**Motor KVL:**  $V_a = E_a + I_a \cdot R_a$   
**Generator KVL:**  $V_a = E_a - I_a \cdot R_a$   
**Developed power:**  $P_d = E_a \cdot I_a = \tau \cdot \omega_m$   
**Shunt:**  $I_L = I_a + I_f; \quad I_f = V_T / R_f; \quad V_a = V_T$   
**Series:**  $I_L = I_a = I_f; \quad V_T = E_a + I_a (R_a + R_f)$   
**T– $\omega$  (shunt/sep):**  $\omega = V_a / (K_e \Phi) - [R_a / (K_e \Phi)^2] \cdot \tau$   
**Series  $\tau$ – $\omega$ :**  $\omega = V_T / (K_e K_f \tau) - R_s / (K_e K_f)$   
**Series E ratio:**  $E_2 / E_1 = (I_{a2} \cdot \omega_2) / (I_{a1} \cdot \omega_1)$   
**Losses:**  $P_{Cu} = I_a^2 R_a; \quad P_{\text{brush}} = V_{BD} \cdot I_a; \quad P_f = I_f^2 R_f$   
**Efficiency:**  $\eta = P_{\text{out}} / P_{\text{in}}; \quad P_{\text{in}} = V_T \cdot I_L$   
 **$P_{\text{out}}$  (motor):**  $= P_d - P_{\text{rot}} - P_{\text{core}}$

## 6. AC MACHINE FUNDAMENTALS

**3-phase currents:**  $i_a = I_M \sin(\omega t); \quad i_b = I_M \sin(\omega t - 120^\circ); \quad i_c = I_M \sin(\omega t - 240^\circ)$   
**Net field magnitude:**  $|B_{\text{net}}| = 1.5 \cdot B_M$  (rotates at  $\omega_e$ )  
**Peak coil voltage:**  $\hat{e} = N_C \cdot \omega_m \cdot \Phi_M \text{ [V]}$   
**RMS phase voltage:**  $V_{\phi, \text{rms}} = \hat{e} / \sqrt{2}$   
**Winding factor:**  $k_w = k_p \cdot k_d \leq 1$   
**Pitch factor:**  $k_p = \sin(\text{pitch\_angle} / 2)$

## 7. SYNCHRONOUS MACHINES

**Internal voltage:**  $E_A = K \cdot \Phi \cdot \omega \text{ [V rms]}$   
**Generator KVL:**  $E_A = V_\phi + I_A (R_A + jX_S)$   
**Motor KVL:**  $V_\phi = E_A + I_A (R_A + jX_S)$   
**Power (gen&motor):**  $P = 3 \cdot V_\phi \cdot E_A \cdot \sin\delta / X_S$   
**Max power ( $\delta = 90^\circ$ ):**  $P_{\text{max}} = 3 \cdot V_\phi \cdot E_A / X_S$   
**Reactive power:**  $Q = 3 \cdot V_\phi \cdot I_A \cdot \sin\theta$   
**Max torque (motor):**  $\tau_{\text{max}} = 3 \cdot V_\phi \cdot E_A / (X_S \cdot \omega_m)$   
**Torque general:**  $\tau_{\text{ind}} = k \cdot B_R \cdot B_{\text{net}} \cdot \sin\delta$   
**DC test (Y):**  $R_A = V_{DC} / (2 \cdot I_{DC})$   
**OC test (Y):**  $E_A = V_{T,OC} / \sqrt{3}$   
**SC test:**  $Z_S = E_A / I_{A,SC}; \quad X_S = \sqrt{(Z_S^2 - R_A^2)}$   
**Voltage regulation:**  $\text{VR}\% = (V_{NL} - V_{FL}) / V_{FL} \times 100\%$   
 **$V_{NL}$  (Y-conn):**  $= |E_A|$  (field current unchanged)  
**Phasor (Gen,  $V_\phi = \text{ref } 0^\circ$ ):**  
 Lagging load:  $I_A \angle -\theta \rightarrow |E_A| > V_\phi \rightarrow \text{VR} > 0$   
 Leading load:  $I_A \angle +\theta \rightarrow |E_A| < V_\phi \rightarrow \text{VR} < 0$

10. KEY INEQUALITIES AND CONDITIONS

<b>Sync generator mode:</b> $E_A$ leads $V_\phi$ ( $\delta > 0$ )
<b>Sync motor mode:</b> $E_A$ lags $V_\phi$ ( $\delta < 0$ )
<b>Overexcited (gen or motor):</b> $ E_A  \cos \delta > V_\phi \rightarrow$ supplies Q (leading $I_A$ )
<b>Underexcited (gen or motor):</b> $ E_A  \cos \delta < V_\phi \rightarrow$ absorbs Q (lagging $I_A$ )
<b>DC motor vs generator:</b> $V_T > E_a \rightarrow$ motor; $E_a > V_T \rightarrow$ generator
<b>Induction motor stability:</b> operates at $s < s_{\max}$ (rising torque region)
<b>Grid sync (all 4):</b> equal V, equal seq, equal angle, $f_{\text{inc}} > f_{\text{grid}}$
<b>Series motor:</b> NEVER run at no-load (speed $\rightarrow \infty$ )
<b>Sync motor:</b> CANNOT start DOL (zero average starting torque)
<b>Max IM starting torque:</b> when $R_2 = \sqrt{(R_{TH})^2 + (X_{TH} + X_2)^2}$

11. POWER FACTOR CORRECTION (SYNC CONDENSER)

<b>Reactive power demand:</b> $Q_{\text{load}} = P \cdot \tan(\cos^{-1}(\text{PF}_{\text{old}}))$
<b>After correction:</b> $Q_{\text{required}} = P \cdot \tan(\cos^{-1}(\text{PF}_{\text{new}}))$
<b>Q to supply:</b> $Q_{\text{supply}} = Q_{\text{load}} - Q_{\text{required}}$
<b>Sync motor current:</b> $S_{SM} = P_{SM} + jQ_{\text{supply}}$
<b><math>I_A</math> of sync motor:</b> $I_A = S_{SM} / (3V_\phi)$
<b><math>E_A</math> needed:</b> $E_A = V_\phi - I_A \cdot jX_S$ (motor sign)
<b>Induction motor PF:</b> Always lagging (absorbs Q); cannot supply Q

12. MACHINE PARAMETER TEST SUMMARY

<b>Sync Gen (3 tests):</b>
DC: $R_A = V_{DC} / (2I_{DC})$ [Y-conn, 2 series windings]
OC: $E_A = V_{T,OC} / \sqrt{3}$ [Y]; $Z_S = E_A / I_{SC}$ ; $X_S = \sqrt{Z_S^2 - R_A^2}$
<b>Induction Motor (3 tests):</b>
DC: $R_1 = V_{DC} / (2I_{DC})$ [Y-conn]
NL: $X_M = V_{\phi,NL} / I_{NL}$ ; $P_{\text{rot}} + P_{\text{core}} = P_{NL} - 3I_{NL}^2 R_1$
LR: $R_{LR} = P_{LR} / (3I^2)$ ; $Z_{LR} = V_\phi / I$ ; scale X by $f_{\text{rated}} / f_{\text{test}}$

8. INDUCTION MACHINES

<b>Slip:</b> $s = (\eta_s - \eta_m) / \eta_s$ ; $\eta_m = (1-s) \cdot \eta_s$ ; $\omega_m = (1-s) \omega_s$
<b>Rotor frequency:</b> $f_r = s \cdot f_e$
<b>Rotor quantities:</b> $E_R = s \cdot E_{R0}$ ; $X_R = s \cdot X_{R0}$
<b>Rotor current (referred):</b> $I_2 = E_1 / (R_2/s + jX_2)$
<b>Power flow chain:</b>
$P_{AG} = P_{in} - P_{SCL} - P_{core} = 3I_2^2 R_2 / s = \tau_{ind} \cdot \omega_s$
$P_{RCL} = s \cdot P_{AG} = 3I_2^2 R_2$
$P_{conv} = (1-s) \cdot P_{AG} = \tau_{ind} \cdot \omega_m$
$P_{out} = P_{conv} - P_{rot}$ ; $\tau_{load} = P_{out} / \omega_m$
<b>Key ratios:</b> $P_{RCL} / P_{AG} = s$ ; $P_{conv} / P_{AG} = 1-s$
<b>Thevenin:</b> $V_{TH} \approx V_1 \cdot X_M' / (X_1 + X_M')$
$R_{TH} = R_1 \cdot (X_M' / (X_1 + X_M'))^2$ ; $X_{TH} \approx X_1$
<b>Induced torque:</b> $\tau_{ind} = 3V_{TH}^2 (R_2/s) / [\omega_s \{ (R_{TH} + R_2/s)^2 + (X_{TH} + X_2)^2 \}]$
<b>Max torque slip:</b> $s_{\max} = R_2 / \sqrt{(R_{TH})^2 + (X_{TH} + X_2)^2}$
<b>Max torque:</b> $\tau_{\max} = 3V_{TH}^2 / [2\omega_s (R_{TH} + \sqrt{(R_{TH})^2 + (X_{TH} + X_2)^2})]$
$\tau_{\max}$ is INDEPENDENT of $R_2$ ; $s_{\max} \propto R_2$
<b>Torque <math>\propto V_1^2</math></b> (proportional to square of supply voltage)
<b>DC test (Y):</b> $R_1 = V_{DC} / (2 \cdot I_{DC})$
<b>LR test:</b> $R_{LR} = P / (3I^2)$ ; $Z_{LR} = V_\phi / I$ ; $X_{LR} = \sqrt{Z^2 - R^2} \cdot (f_r / f_l)$
$R_2 = R_{LR} - R_1$ ; Design A/D: $X_1 = X_2 = X_{LR} / 2$
<b>Plugging:</b> $s_{\text{plug}} \approx 2 - s_{\text{rated}} \approx 2$ (immediately after phase reversal)

9. SPECIAL MACHINES

<b>Universal motor voltage:</b> $ V_s ^2 = (E_a + I_a R_{\text{total}})^2 + (I_a X_{\text{total}})^2$
$X_{\text{total}} = 2\pi f (L_a + L_\ell)$ ; $R_{\text{total}} = R_a + R_\ell$
$\tau \propto I_a^2$ (series) $\rightarrow$ half torque: $I_{a,\text{new}} = I_{\text{old}} / \sqrt{2}$
<b>BLDC:</b> $V_s = E_a + 2I \cdot R_{ph}$ ; $P_{conv} = 2 \cdot E \cdot I$
$E_a = k \cdot \omega$ ; $\tau = k \cdot I$ (DC equations apply)
<b>SRM torque:</b> $\tau = \frac{1}{2} \cdot I^2 \cdot dL / d\theta$
Switch off current BEFORE full alignment ( $dL / d\theta$ changes sign)