



# EE3123 Introduction to Electric Power Systems

## Three-phase power circuit analysis

Prof. CQ Jiang

Many thanks to Prof. Michael Tse


# Three-phase voltages

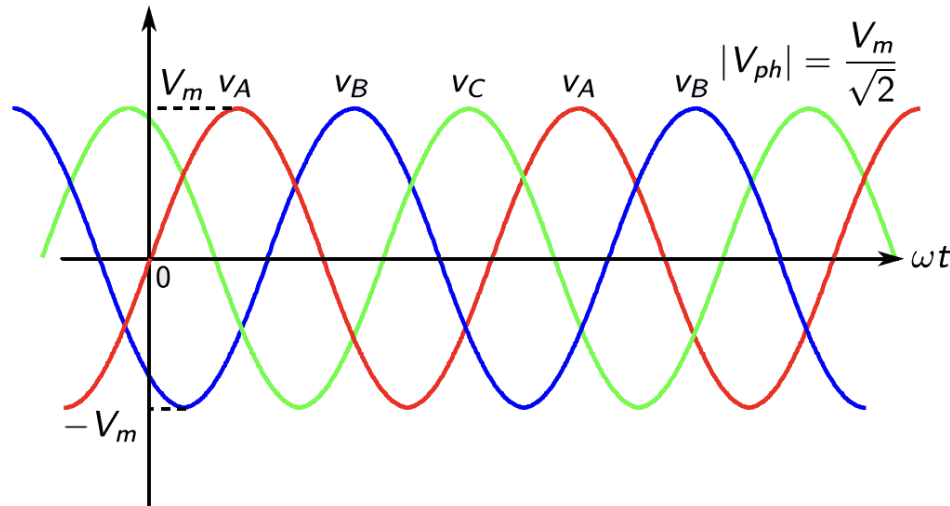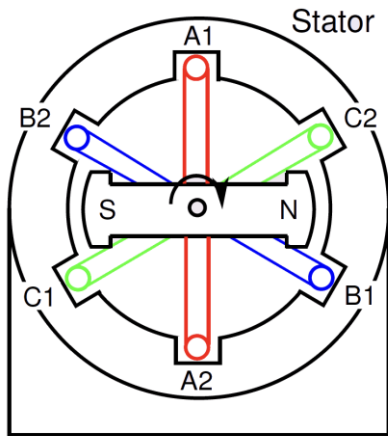

$$v_A = V_m \sin \omega t \Rightarrow V_A = |V_{ph}| \angle 0^\circ$$


$$v_B = V_m \sin(\omega t - 120^\circ) \Rightarrow V_B = |V_{ph}| \angle -120^\circ$$

$$v_C = V_m \sin(\omega t - 240^\circ) \Rightarrow V_C = |V_{ph}| \angle -240^\circ$$

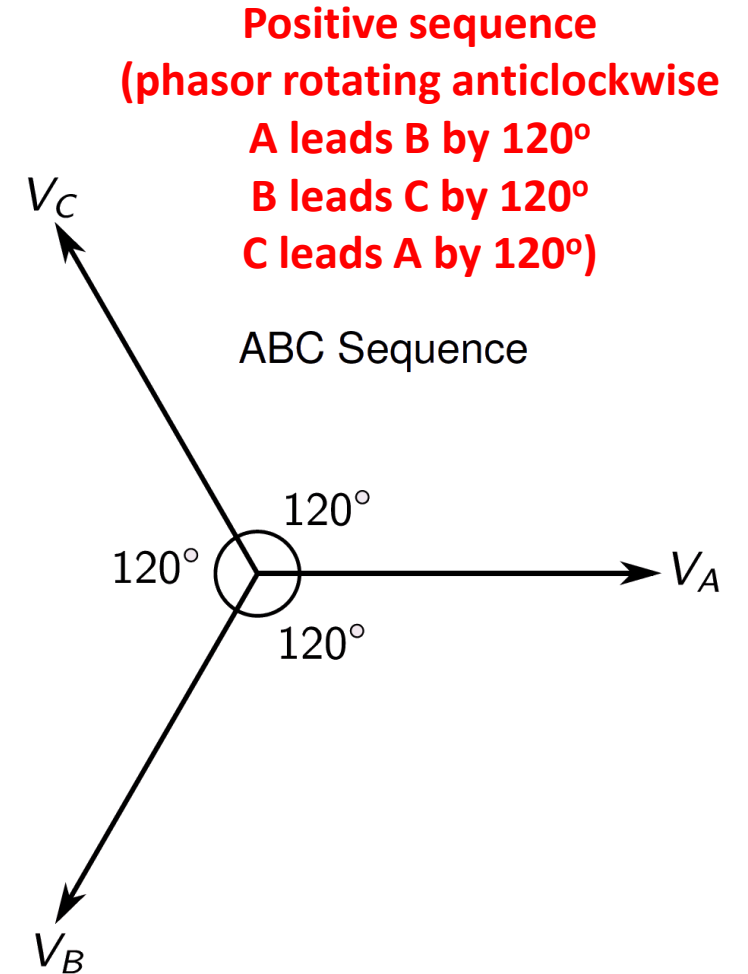


If  $|V_A| = |V_B| = |V_C| = |V_{ph}|$  and all phase differences are equal, the three-phase voltages are BALANCED.


# POSITIVE SEQUENCE or ABC SEQUENCE

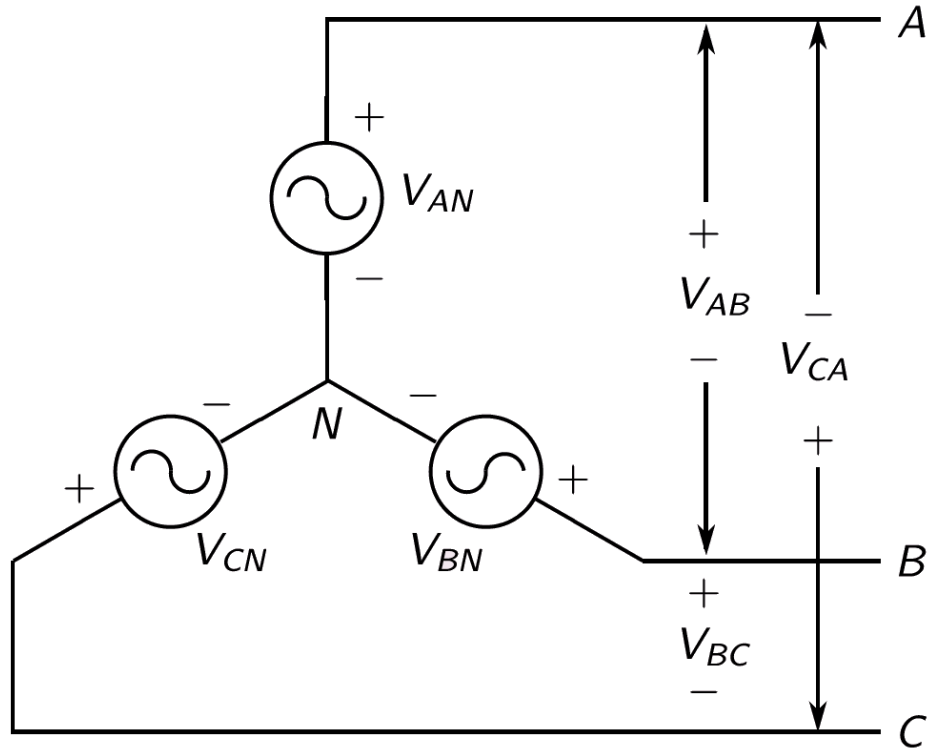
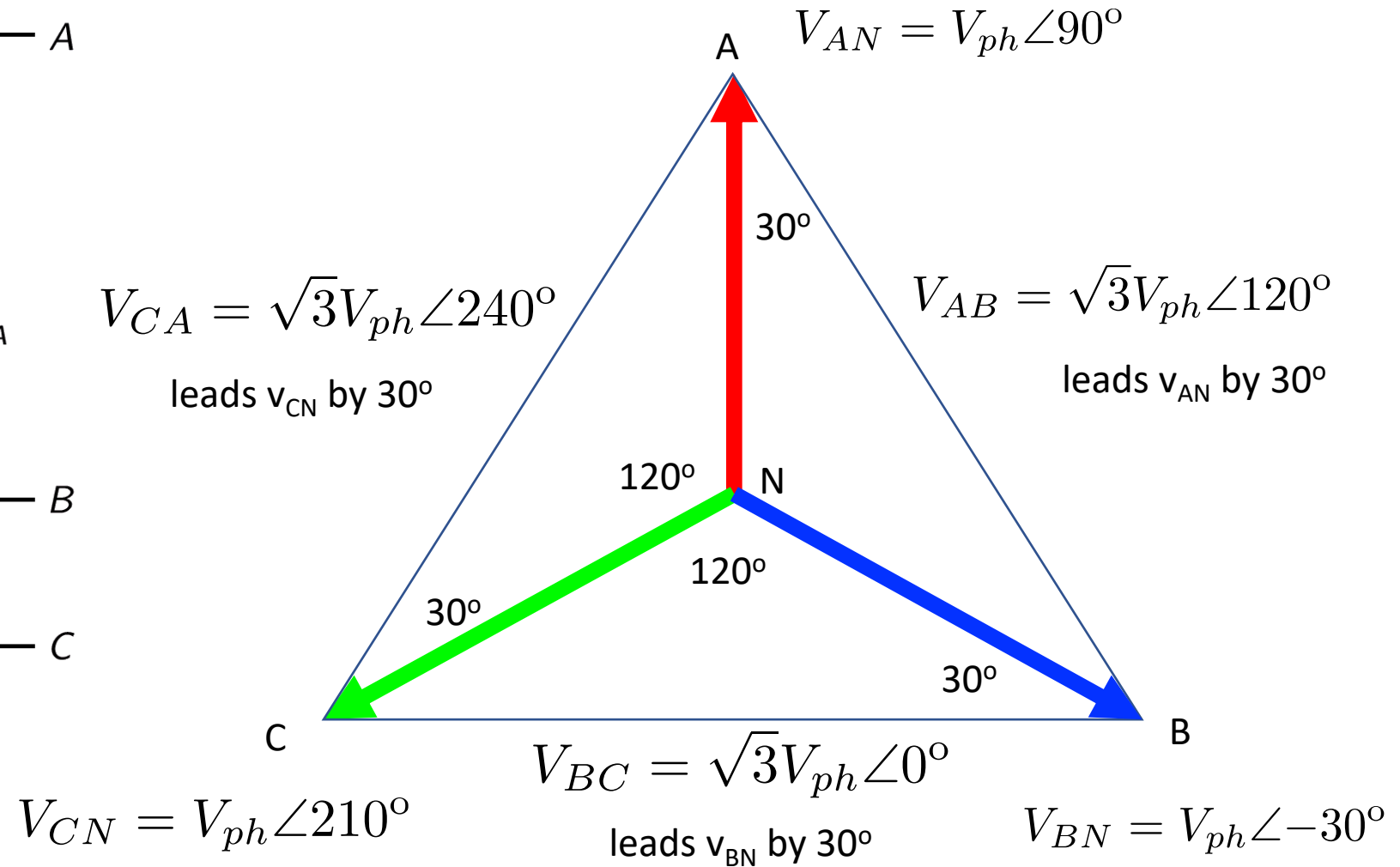
$$\begin{aligned} E_{ab} &= \sqrt{3}E_{an} \angle +30^\circ \\ E_{bc} &= \sqrt{3}E_{bn} \angle +30^\circ \\ E_{ca} &= \sqrt{3}E_{cn} \angle +30^\circ \end{aligned}$$



# Three-phase connections

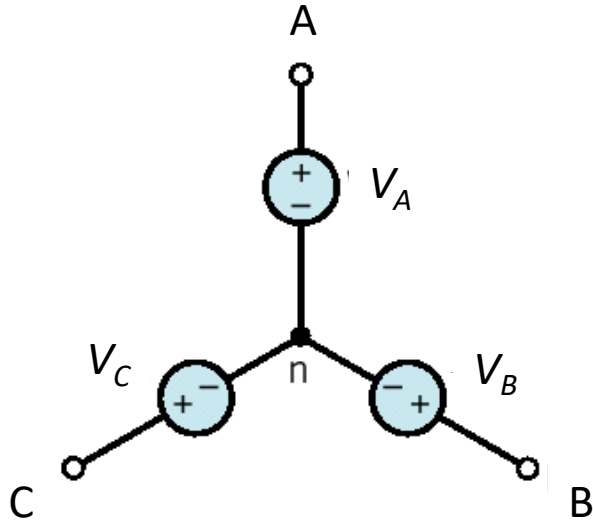


$$V_A = 110 \text{ V}$$

$$V_A = 220 \text{ V}$$

$$V_A = 240 \text{ V}$$

Phase voltage

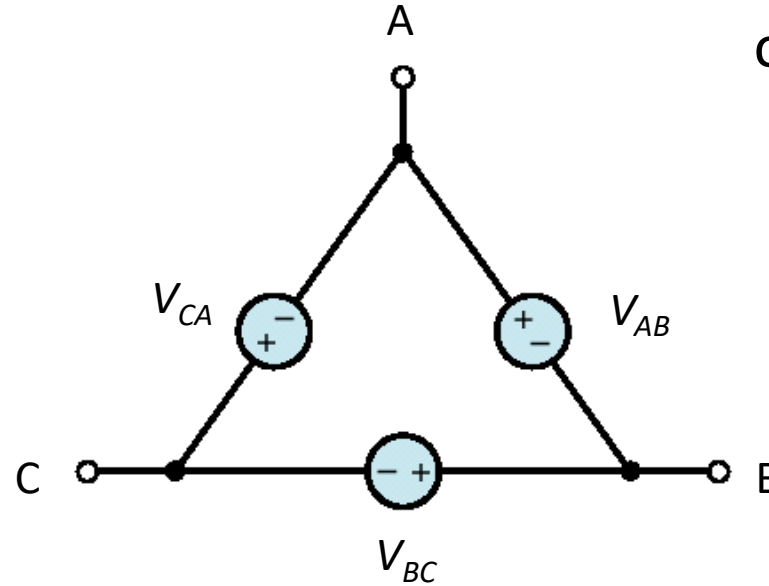

$$V_{AC} = 190 \text{ V}$$

$$V_{AC} = 380 \text{ V}$$

$$V_{AC} = 416 \text{ V}$$


Line voltage

$$V_{\text{line}} = \sqrt{3}V_{\text{phase}}$$


or

$$V_{LL} = \sqrt{3}V_{LN}$$

Delta Connction

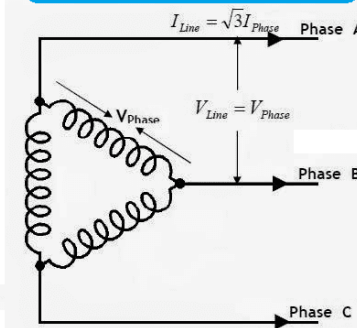

Star Connection

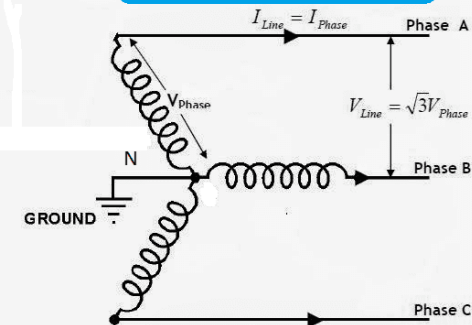


# Three-phase balanced loads

If all loads are equal in a Y or  $\Delta$  circuit, then the three-phase load is BALANCED.

For balanced loads,

$$Z_{\Delta} = 3Z_Y$$

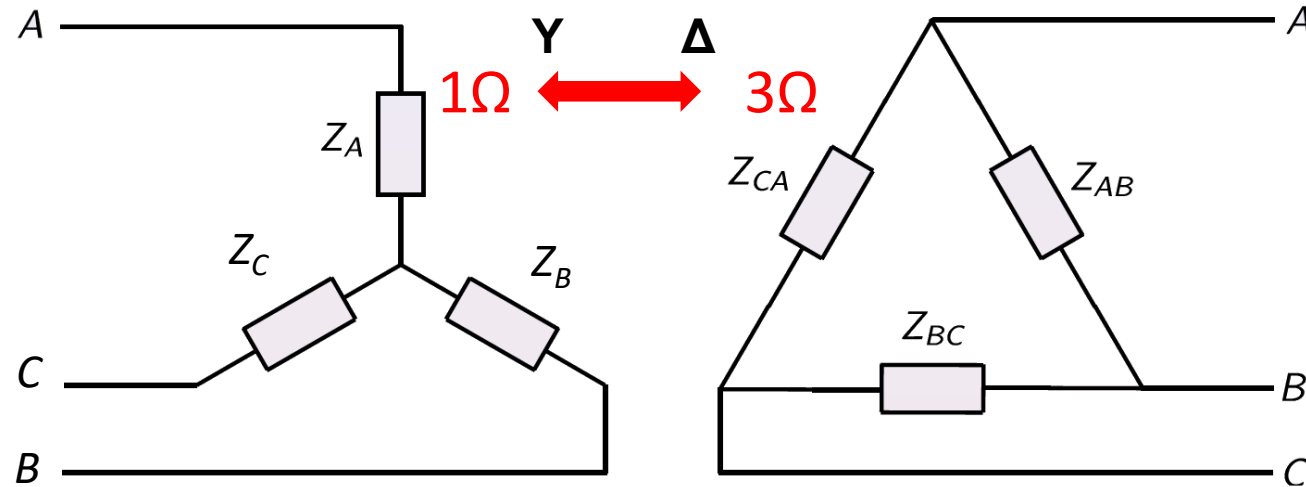

$$Z_A = \frac{Z_{CA}Z_{AB}}{Z_{AB} + Z_{BC} + Z_{CA}}$$

$$Z_B = \frac{Z_{AB}Z_{BC}}{Z_{AB} + Z_{BC} + Z_{CA}}$$


$$Z_C = \frac{Z_{BC}Z_{CA}}{Z_{AB} + Z_{BC} + Z_{CA}}$$

$$Z_{AB} = \frac{Z_A Z_B + Z_B Z_C + Z_C Z_A}{Z_C}$$

$$Z_{BC} = \frac{Z_A Z_B + Z_B Z_C + Z_C Z_A}{Z_A}$$


$$Z_{CA} = \frac{Z_A Z_B + Z_B Z_C + Z_C Z_A}{Z_B}$$

Pi - T transformation

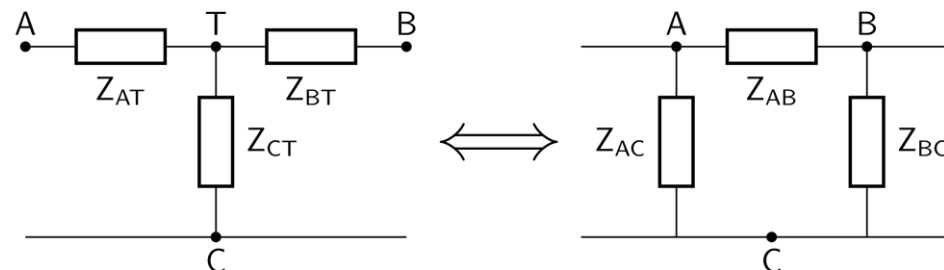

# Proof of Wye (Y) – Delta (Δ) Transformation

Δ – Y derivation

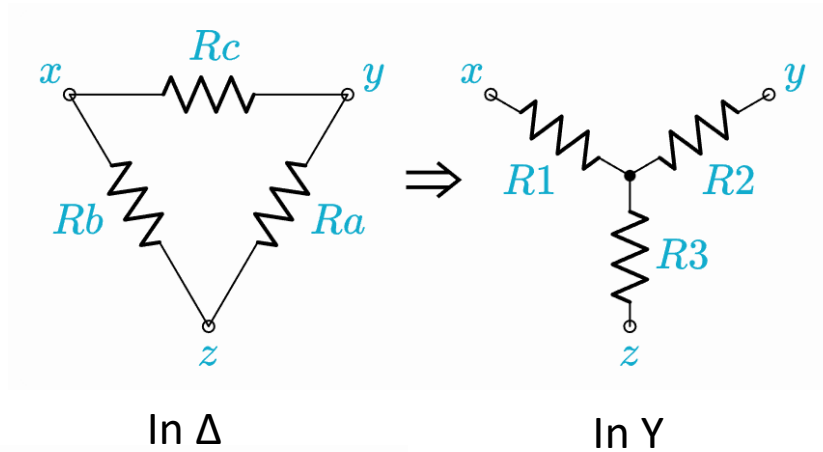

$$R_{xy} = R_c \parallel (R_a + R_b) = \frac{R_c (R_a + R_b)}{R_c + (R_a + R_b)}$$

$$R_{xy} = R_1 + R_2$$

$$R_{xy} : R_1 + R_2 = R_c (R_a + R_b) / (R_a + R_b + R_c)$$

The same for other two sub circuits

$$R_{xy} : R_1 + R_2 = R_c (R_a + R_b) / (R_a + R_b + R_c)$$

$$R_{yz} : R_2 + R_3 = R_a (R_b + R_c) / (R_a + R_b + R_c)$$

$$R_{zx} : R_3 + R_1 = R_b (R_c + R_a) / (R_a + R_b + R_c)$$

$$R_1 = (R_{xy} + R_{zx} - R_{yz}) / 2$$

$$= \frac{R_c(R_a + R_b) + R_b(R_c + R_a) - R_a(R_b + R_c)}{2(R_a + R_b + R_c)}$$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

The same to get R2 and R3.

The Δ to Y transformation is,

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$


$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$



# Proof of Wye (Y) – Delta (Δ) Transformation

Y – Δ derivation

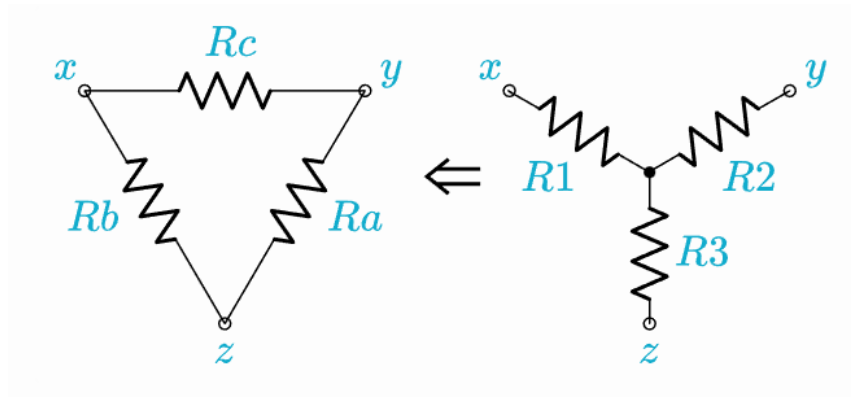

The Y to Δ transformation is,

$$R_a = \frac{R_3 R_2 + R_3 R_1 + R_1 R_2}{R_1}$$

$$R_b = \frac{R_3 R_2 + R_3 R_1 + R_1 R_2}{R_2}$$

$$R_c = \frac{R_3 R_2 + R_3 R_1 + R_1 R_2}{R_3}$$

The Δ to Y transformation is,

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$\frac{R_3}{R_1} = \frac{\frac{R_a R_b}{R_b R_c}}{\frac{R_a + R_b + R_c}{R_b R_c}}$$

$$\frac{R_3}{R_1} = \frac{R_a R_b}{R_b R_c} = \frac{R_a}{R_c}$$

$$R_a = \frac{R_3 R_c}{R_1}$$

Repeat the previous

$$\frac{R_3}{R_2} = \frac{R_a R_b}{R_a R_c} = \frac{R_b}{R_c}$$


$$R_b = \frac{R_3 R_c}{R_2}$$

$$R_2 = \frac{\frac{R_3 R_c}{R_1} R_c}{\frac{R_3 R_c}{R_1} + \frac{R_3 R_c}{R_2} + R_c}$$

$$R_2 = \frac{\frac{R_3 R_c}{R_1}}{\frac{R_3}{R_1} + \frac{R_3}{R_2} + 1}$$

$$R_c = \frac{R_3 R_2 + R_3 R_1 + R_1 R_2}{R_3}$$
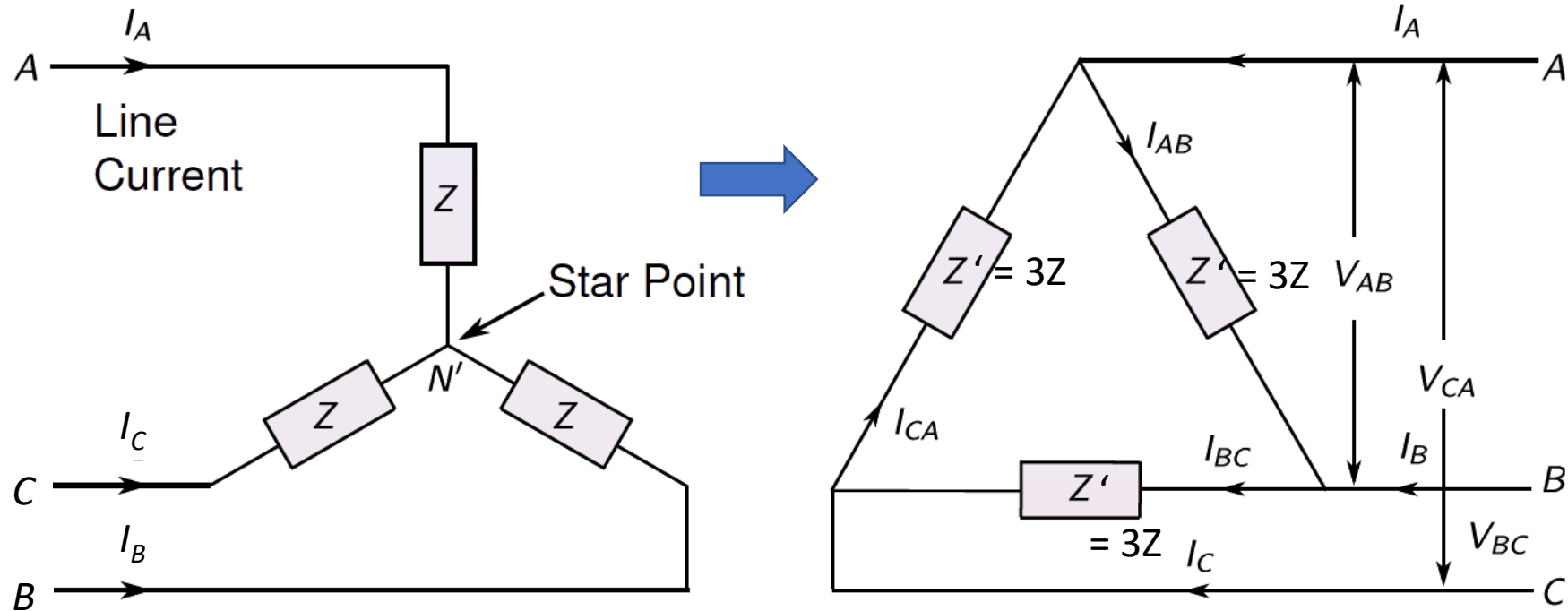
# Line currents – Transformation for Loads




$$I_A = \sqrt{3} I_{AB} \angle -30^\circ$$

$$\text{or } I_{AB} = \frac{I_A}{\sqrt{3}} \angle 30^\circ$$



# Three-phase electricity

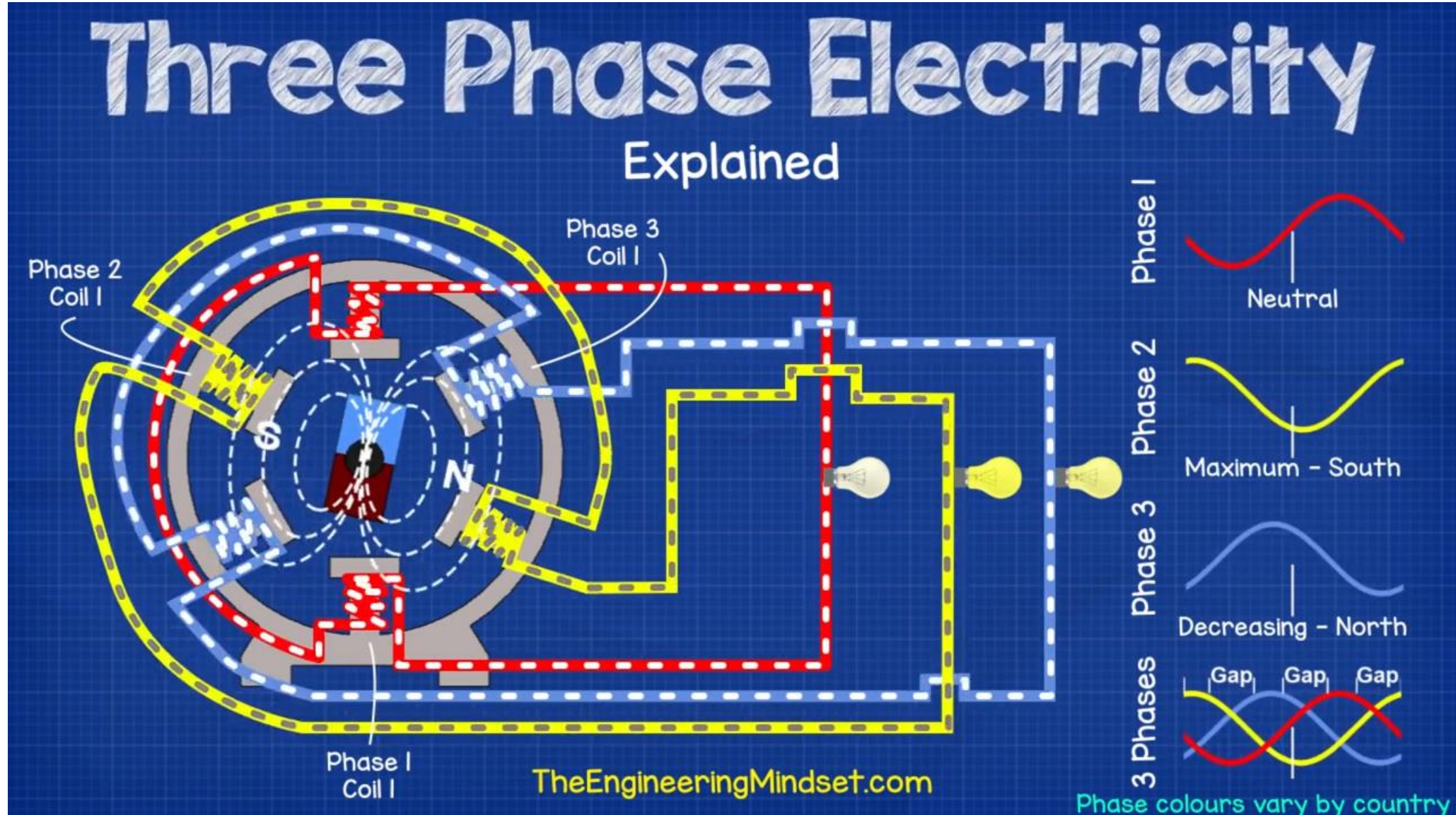


# Y-to-Y circuit

If the circuit is balanced,  $V_{Nn}$  will be 0.

In other words, there will be no returning current from  $N$  to  $n$ .

The neutral cable is thus NOT needed!

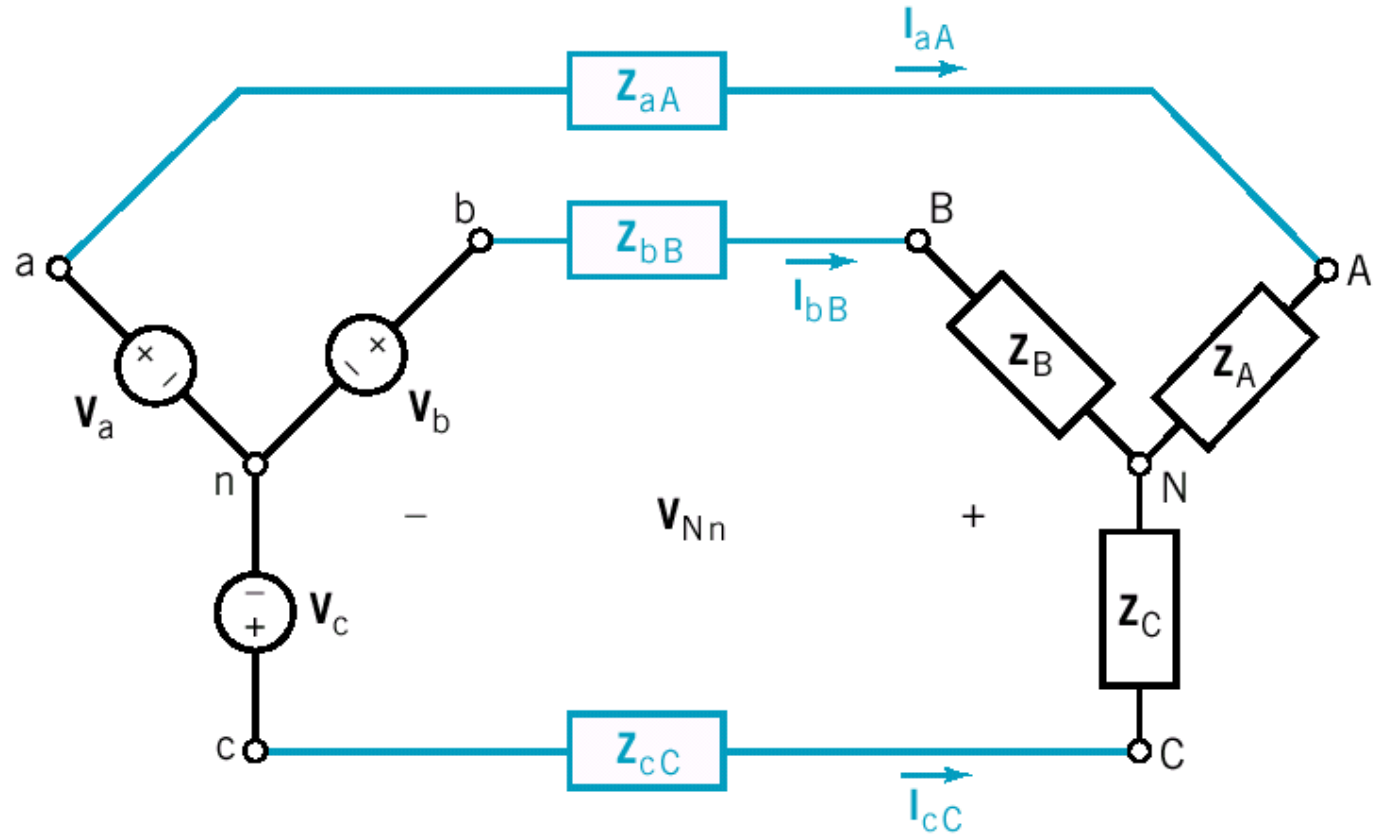

Suppose  $Z_A = Z_B = Z_C = Z \angle \theta$  and  $V_{AN} = V_{ph}$  (voltage in rms)

$$\text{Power in each impedance} = \frac{V_{ph}^2}{Z} \cos \theta$$

$$\text{Total power delivered to load} = \frac{3V_{ph}^2}{Z} \cos \theta$$


# Single-phase equivalent

For a balanced circuit, we know that

- $V_{Nn} = 0$ .
- All line currents are equal and differ by  $120^\circ$ .
- Equal power is dissipated in each load.

So, we can simplify the representation to a single-phase circuit, like considering only one of the phases.

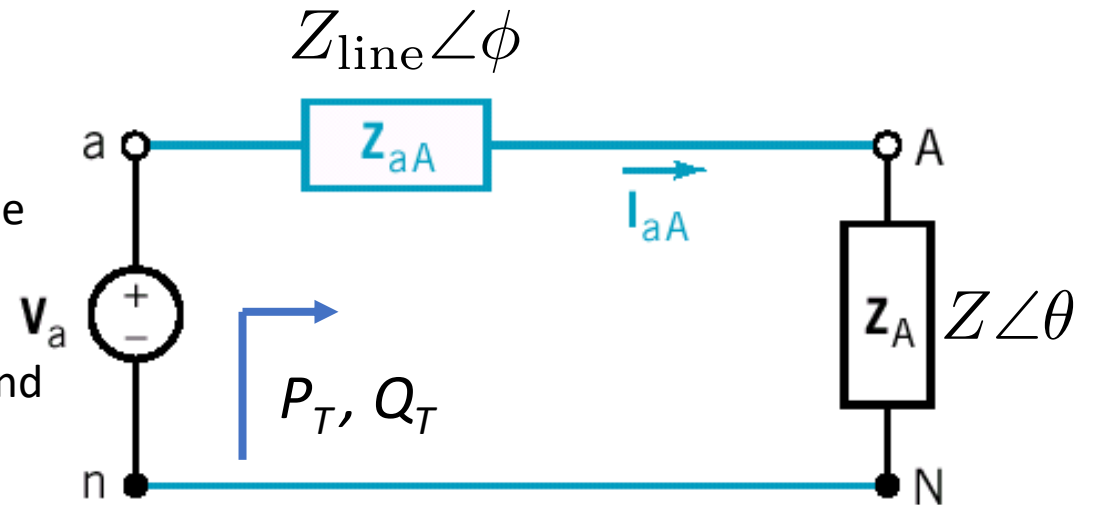Solve the circuit like a single-phase circuit, and then extend all the phase voltages and currents accordingly.



$$Z_T = (Z_{\text{line}} \cos \phi + Z \cos \theta) + j(Z_{\text{line}} \sin \phi + Z \sin \theta)$$

$$|Z_T| = \sqrt{(Z_{\text{line}} \cos \phi + Z \cos \theta)^2 + (Z_{\text{line}} \sin \phi + Z \sin \theta)^2}$$

$$I_{aA} = \frac{V_a}{|Z_T|} \quad (\text{current and voltage in rms})$$

$$P_T = I_{aA}^2 (Z_{\text{line}} \cos \phi + Z \cos \theta)$$

$$Q_T = I_{aA}^2 (Z_{\text{line}} \sin \phi + Z \sin \theta)$$


$$S_T = \sqrt{P_T^2 + Q_T^2}$$

$$\theta_T = \tan^{-1}(Q_T/P_T)$$
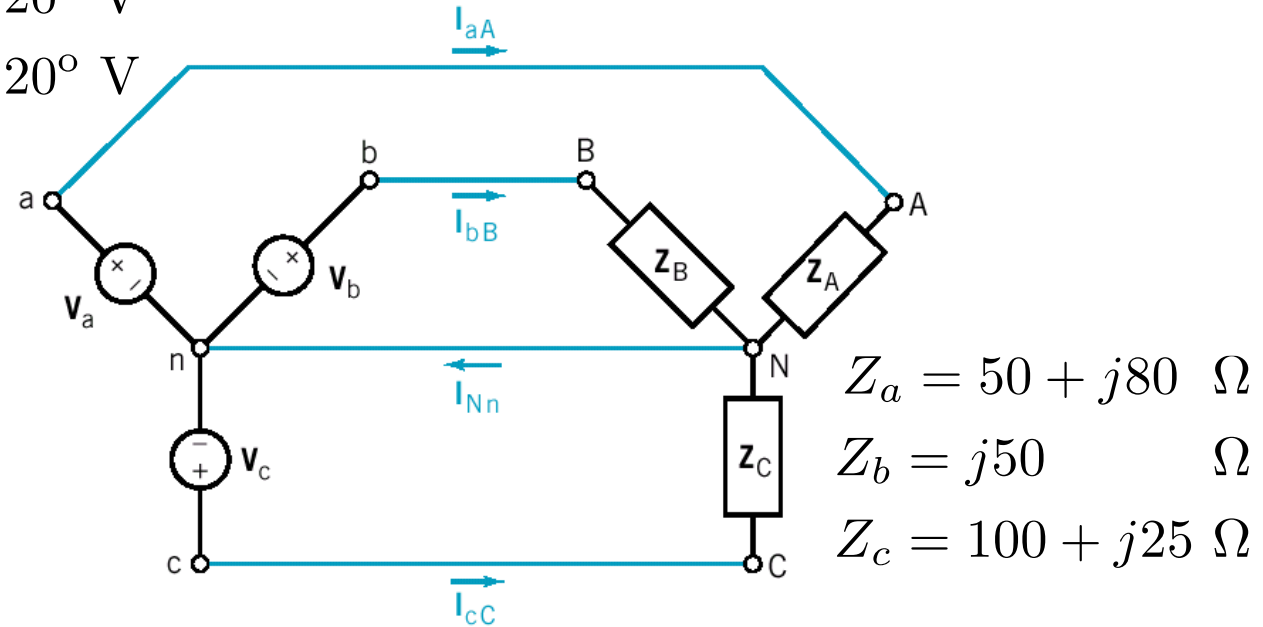
# Unbalanced loads

What is the apparent power delivered to the load by the source?

$$\begin{aligned} V_a &= 110\angle 0^\circ \text{ V} \\ V_b &= 110\angle -120^\circ \text{ V} \\ V_c &= 110\angle +120^\circ \text{ V} \end{aligned} \quad \text{all in rms}$$



$$I_{aA} = \frac{110\angle 0^\circ}{50 + j80} = 1.16\angle -58^\circ \text{ A}$$

$$I_{bB} = \frac{110\angle -120^\circ}{j50} = 2.2\angle 150^\circ \text{ A}$$

$$I_{cC} = \frac{110\angle 120^\circ}{100 + j25} = 1.07\angle 106^\circ \text{ A}$$

$$I_{Nn} = I_{aA} + I_{bB} + I_{cC} = 1.9556\angle 144.2^\circ \text{ A}$$

$$S_A = V_a I_{aA}^* = 68 + j109 \text{ VA}$$

$$S_B = V_b I_{bB}^* = j242 \text{ VA}$$

$$S_C = V_c I_{cC}^* = 114 + j28 \text{ VA}$$


$$S = S_A + S_B + S_C = 182 + j379 \text{ VA}$$

# Example: Balanced- $\Delta$ and-Y loads

A balanced, positive-sequence, Y-connected voltage source with  $E_{ab} = 480 \angle 0^\circ$  volts is applied to a balanced- $\Delta$  load with  $Z_\Delta = 30 \angle 40^\circ \Omega$ . The line impedance between the source and load is  $Z_L = 1 \angle 85^\circ \Omega$  for each phase. Calculate the line currents, the  $\Delta$ -load currents, and the voltages at the load terminals.
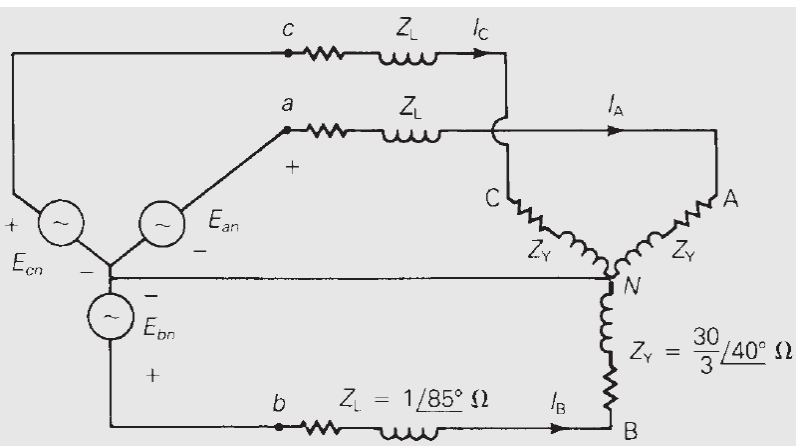
## SOLUTION

First, convert the  $\Delta$  load to an equivalent Y. Then connect the source and Y-load neutrals with a zero-ohm neutral wire. The connection of the neutral wire has no effect on the circuit, since the neutral current  $I_n = 0$  in a balanced system.



$$\begin{aligned}
 I_A &= \frac{E_{an}}{Z_L + Z_Y} = \frac{\frac{480}{\sqrt{3}} \angle -30^\circ}{1 \angle 85^\circ + \frac{30}{3} \angle 40^\circ} \\
 &= \frac{277.1 \angle -30^\circ}{(0.0872 + j0.9962) + (7.660 + j6.428)} \\
 &= \frac{277.1 \angle -30^\circ}{(7.748 + j7.424)} = \frac{277.1 \angle -30^\circ}{10.73 \angle 43.78^\circ} = 25.83 \angle -73.78^\circ \text{ A} \\
 I_B &= 25.83 \angle 166.22^\circ \text{ A} \\
 I_C &= 25.83 \angle 46.22^\circ \text{ A}
 \end{aligned}$$

$$\begin{aligned}
 I_{AB} &= \frac{I_a}{\sqrt{3}} \angle +30^\circ = \frac{25.83}{\sqrt{3}} \angle -73.78^\circ + 30^\circ = 14.91 \angle -43.78^\circ \text{ A} \\
 I_{BC} &= 14.91 \angle -163.78^\circ \text{ A} \\
 I_{CA} &= 14.91 \angle +76.22^\circ \text{ A}
 \end{aligned}$$

The voltages at the load terminals are


$$\begin{aligned}
 E_{AB} &= Z_\Delta I_{AB} = (30 \angle 40^\circ)(14.91 \angle -43.78^\circ) = 447.3 \angle -3.78^\circ \text{ volts} \\
 E_{BC} &= 447.3 \angle -123.78^\circ \\
 E_{CA} &= 447.3 \angle 116.22^\circ \text{ volts}
 \end{aligned}$$



# Instantaneous power (updated slide)



## Balanced three-phase circuits

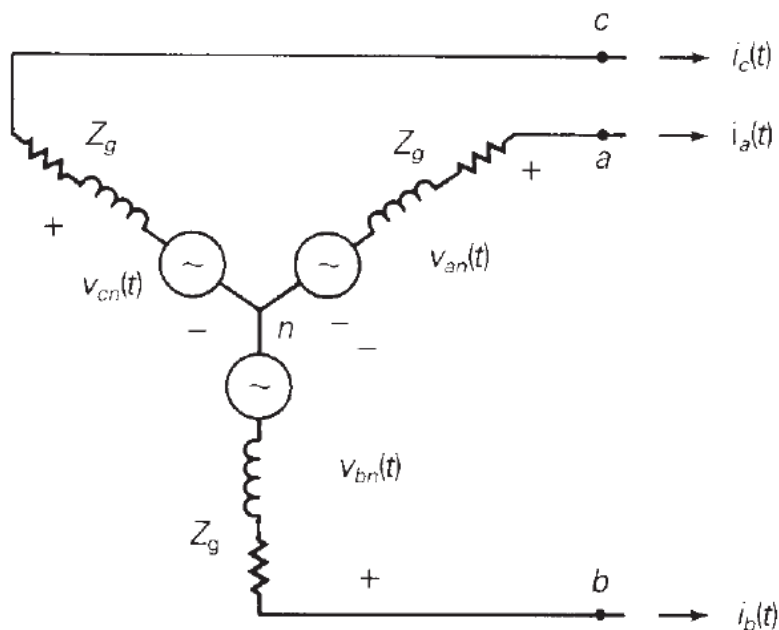

$$\sin^2 \theta = \frac{1 - \cos 2\theta}{2}$$

$$\cos(\alpha - \beta) = \cos \alpha \cos \beta + \sin \alpha \sin \beta$$

$$v_{an}(t) = \sqrt{2}V_{LN} \cos(\omega t + \delta) \quad \text{volts}$$

$$i_a(t) = \sqrt{2}I_L \cos(\omega t + \beta) \quad \text{A}$$


$$\begin{aligned} p_a(t) &= v_{an}(t)i_a(t) \\ &= 2V_{LN}I_L \cos(\omega t + \delta) \cos(\omega t + \beta) \\ &= V_{LN}I_L \cos(\delta - \beta) + V_{LN}I_L \cos(2\omega t + \delta + \beta) \quad \text{W} \end{aligned}$$

$$\begin{aligned} p_b(t) &= 2V_{LN}I_L \cos(\omega t + \delta - 120^\circ) \cos(\omega t + \beta - 120^\circ) \\ &= V_{LN}I_L \cos(\delta - \beta) + V_{LN}I_L \cos(2\omega t + \delta + \beta - 240^\circ) \end{aligned}$$

$$\begin{aligned} p_c(t) &= 2V_{LN}I_L \cos(\omega t + \delta + 120^\circ) \cos(\omega t + \beta + 120^\circ) \\ &= V_{LN}I_L \cos(\delta - \beta) + V_{LN}I_L \cos(2\omega t + \delta + \beta + 240^\circ) \quad \text{W} \end{aligned}$$

$$\begin{aligned} p_{3\phi}(t) &= p_a(t) + p_b(t) + p_c(t) \\ &= 3V_{LN}I_L \cos(\delta - \beta) + V_{LN}I_L [\cos(2\omega t + \delta + \beta) \\ &\quad + \cos(2\omega t + \delta + \beta - 240^\circ) \\ &\quad + \cos(2\omega t + \delta + \beta + 240^\circ)] \quad \text{W} \end{aligned}$$

# (Average) Power (updated slide)

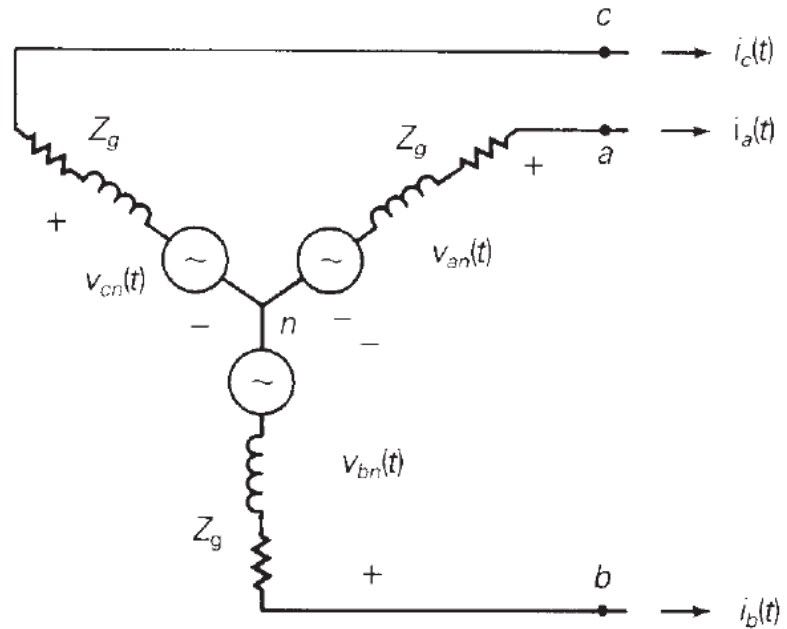

$$P_{3\phi} = 3V_{LN}I_L \cos(\delta - \beta) \quad W$$



$$V_{LN} = V_{LL}/\sqrt{3} \quad \text{and} \quad P_{3\phi} = \sqrt{3}V_{LL}I_L \cos(\delta - \beta) \quad W$$



$$P_{3\phi} = 3V_{LN}I_L \cos \phi$$

$$P_{3\phi} = \sqrt{3}V_{LL}I_L \cos \phi$$




$$\cos \phi$$

$$\begin{aligned} \cos \theta \cos \varphi &= \frac{\cos(\theta - \varphi) + \cos(\theta + \varphi)}{2} \\ \sin \theta \sin \varphi &= \frac{\cos(\theta - \varphi) - \cos(\theta + \varphi)}{2} \end{aligned}$$

V and I in rms values



# Wattmeter

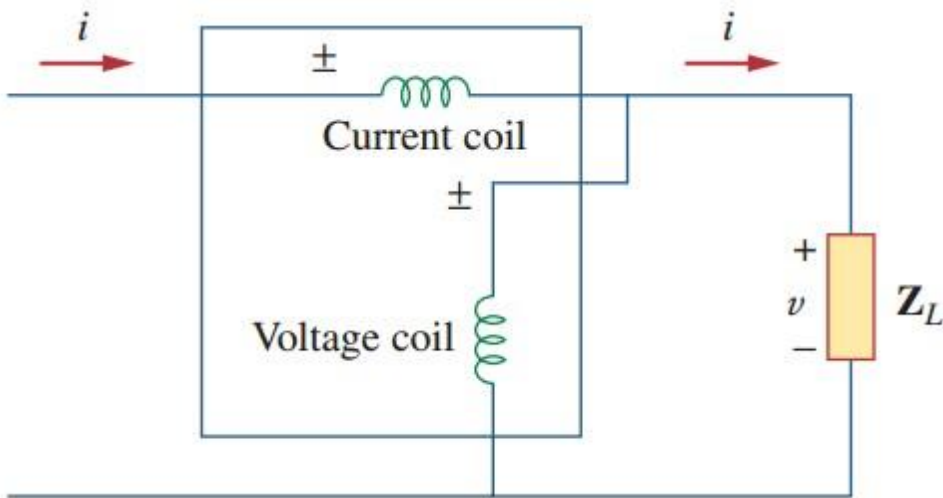

Current coil picks up the current through  
Voltage coil picks up the voltage across  
Meter reading gives the average product.

$$P = P_{\text{average}} = VI \cos \phi$$









where  $\phi$  is the angle between  $V$  and  $I$




# Wattmeter: Current sensing techniques

Measurement methods:

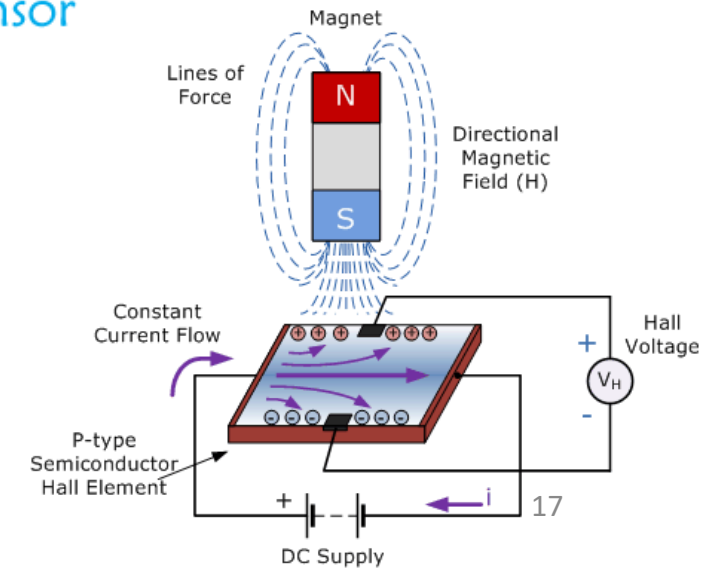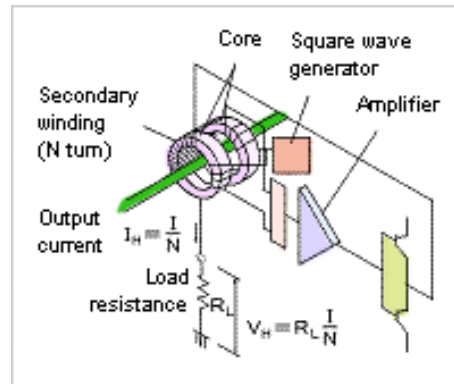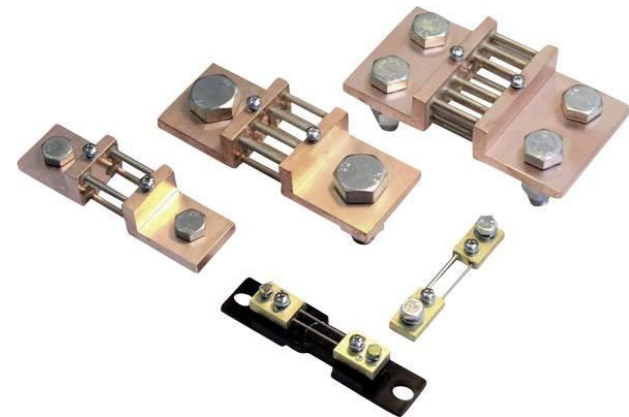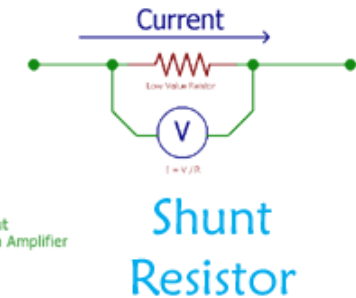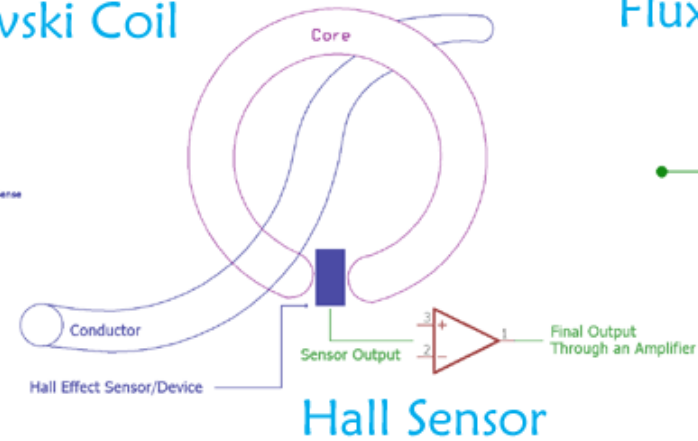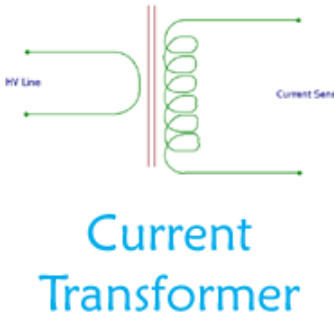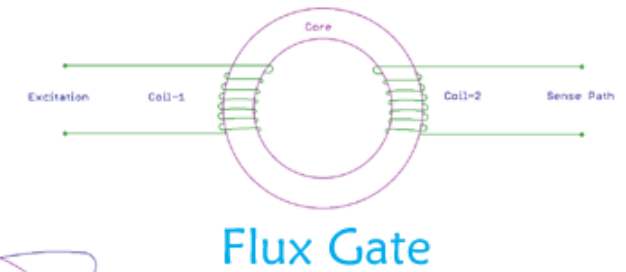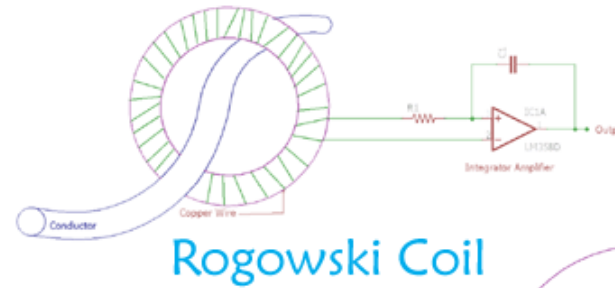1. Resistive (direct)
  - a. Shunt resistors
2. Magnetic (indirect)
  - a. Current transformer
  - b. Rogowski coil
  - c. Hall effect device- hall sensor
3. Transistor (direct)
  - a. RDS(ON)
  - b. Ratio-metric



# Measuring power

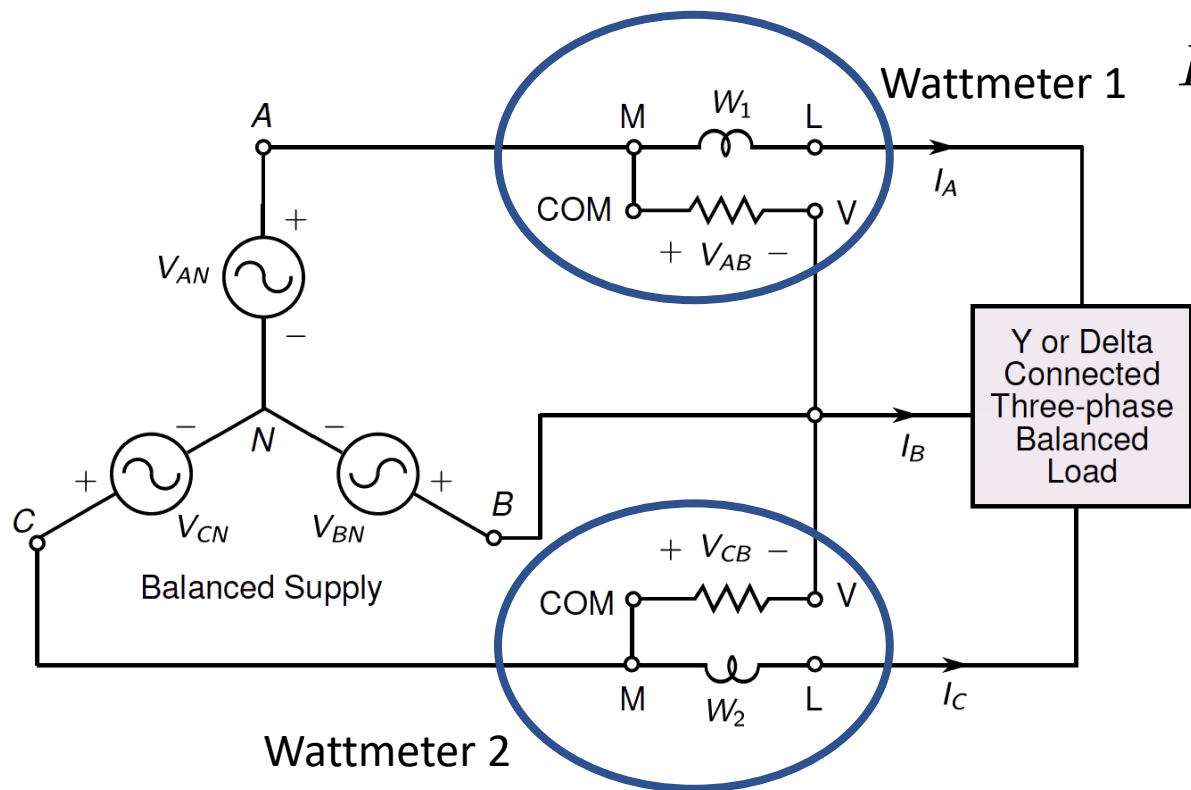


**SUM OF THE READINGS  $W_1$  and  $W_2$  = TOTAL LOAD POWER**


$$P_1 = |V_{AB}| |I_A| \cos(\phi + 30^\circ) = |V| |I| \cos(\phi + 30^\circ)$$

$$P_2 = |V_{BC}| |I_C| \cos(30^\circ - \phi) = |V| |I| \cos(30^\circ - \phi)$$

$$\begin{aligned} P_1 + P_2 &= |V| |I| (\cos(\phi + 30^\circ) + \cos(30^\circ - \phi)) \\ &= 2|V| |I| \cos 30^\circ \cos \phi = \sqrt{3} |V| |I| \cos \phi \end{aligned}$$

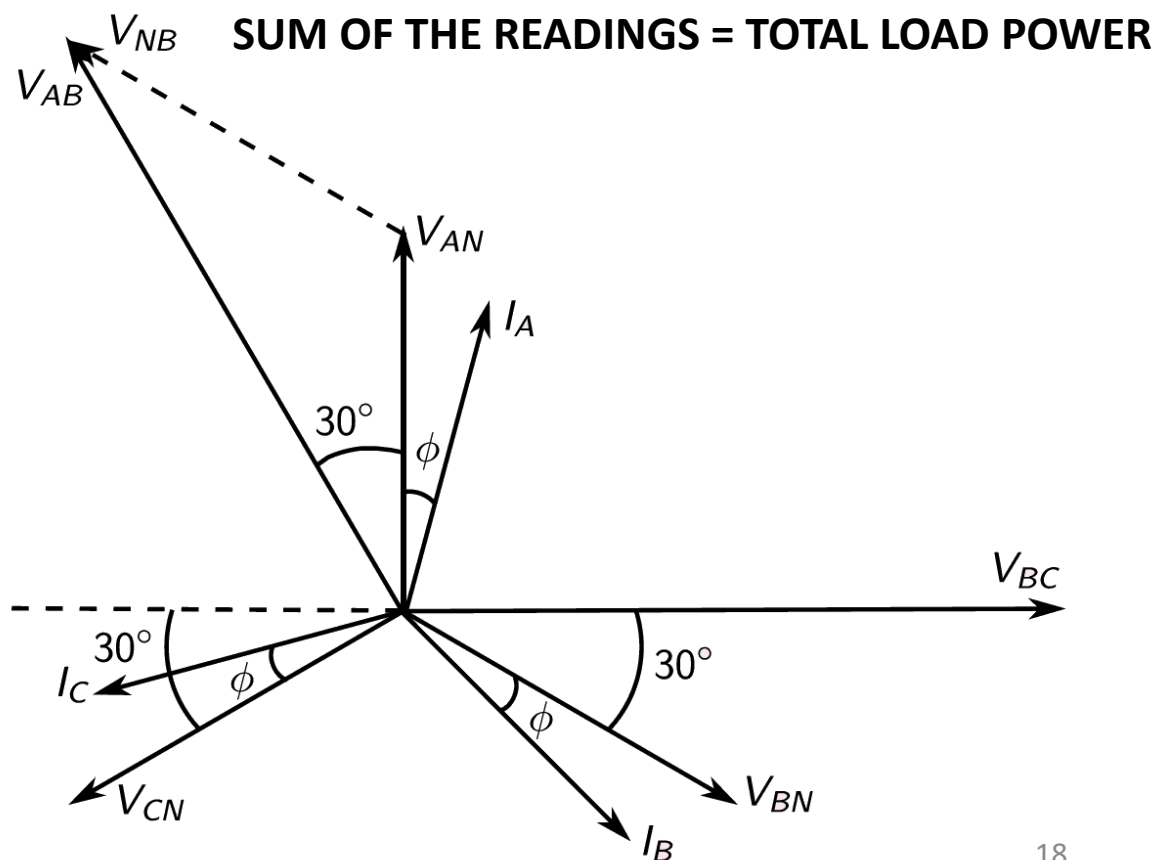

# Impedance angle

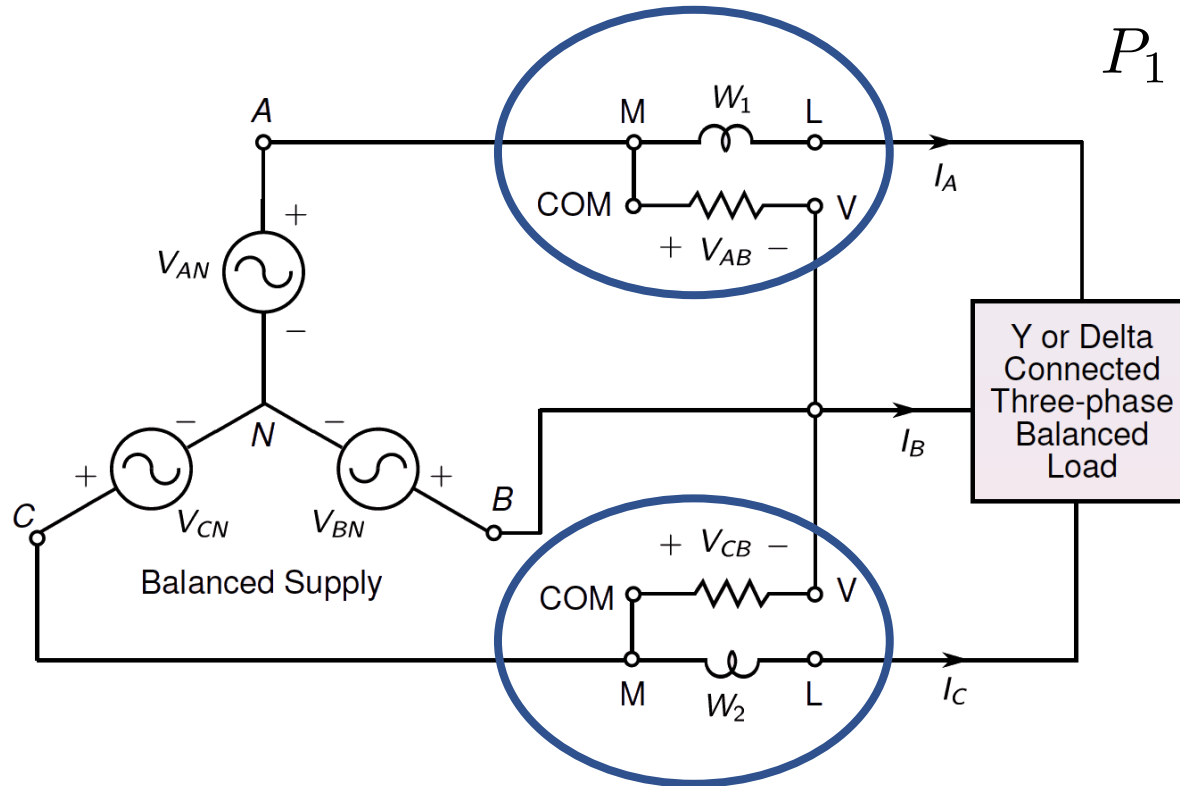

$$P_1 - P_2 = |V||I|(\cos(\phi + 30^\circ) - \cos(30^\circ - \phi))$$

$$= -2|V||I|\sin 30^\circ \sin \phi = -|V||I|\sin \phi$$

$$\frac{P_1 - P_2}{P_1 + P_2} = \frac{-\tan \phi}{\sqrt{3}}$$

$$\tan \phi = -\sqrt{3} \frac{P_1 - P_2}{P_1 + P_2} = \sqrt{3} \frac{P_2 - P_1}{P_1 + P_2}$$

**IMPEDANCE ANGLE CAN ALSO BE FOUND**


$$\cos(\alpha - \beta) = \cos \alpha \cos \beta + \sin \alpha \sin \beta$$

# Three-phase transformer arrangement
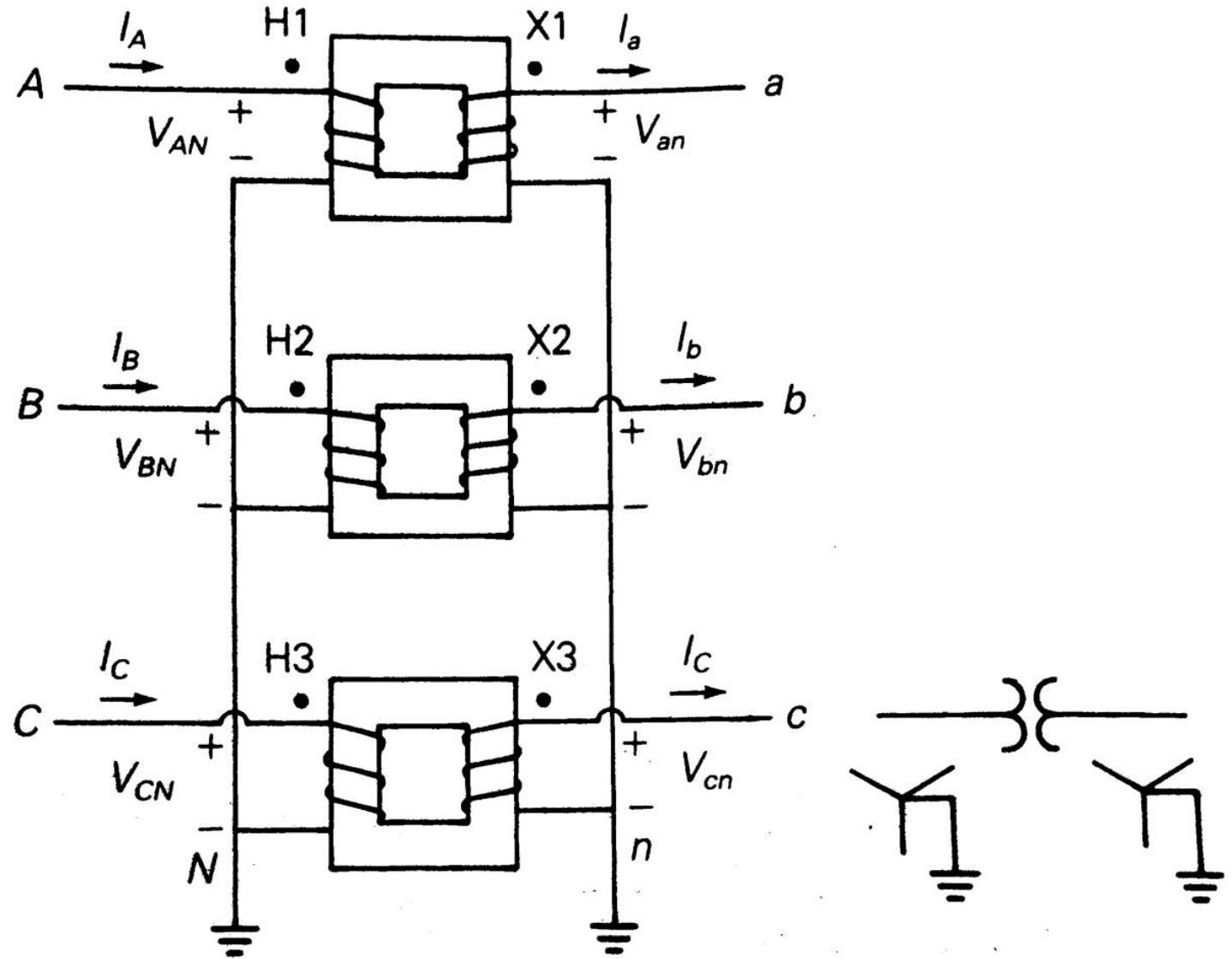
## Y-Y connection

Primary and secondary voltages are in phase

Y-connection provides a neutral line which is good for transmission as it allows unbalanced current to flow out and simplify insulation.



# Three-phase transformer arrangement

## Y-Δ connection

- Y side to N is leading Δ side to n by 30° in this case.
- Δ-connection suppresses third harmonic currents that are generated due to the nonlinear core characteristics (hysteresis) by trapping the harmonic currents in the Δ loop.
- Single transformer:  $\frac{V_{AN}}{V_{ab}} = \frac{N_{H1}}{N_{X1}}$

In single phase equivalent circuit, the Δ side quantities


$$V_{an} = \frac{V_{ab}}{\sqrt{3}} \angle -30^\circ$$

or

$$I_a = \sqrt{3} I_{ab} \angle -30^\circ$$

Thus, we have:  $V_{AN} = \sqrt{3} \frac{N_{H1}}{N_{X1}} V_{an} \angle 30^\circ$

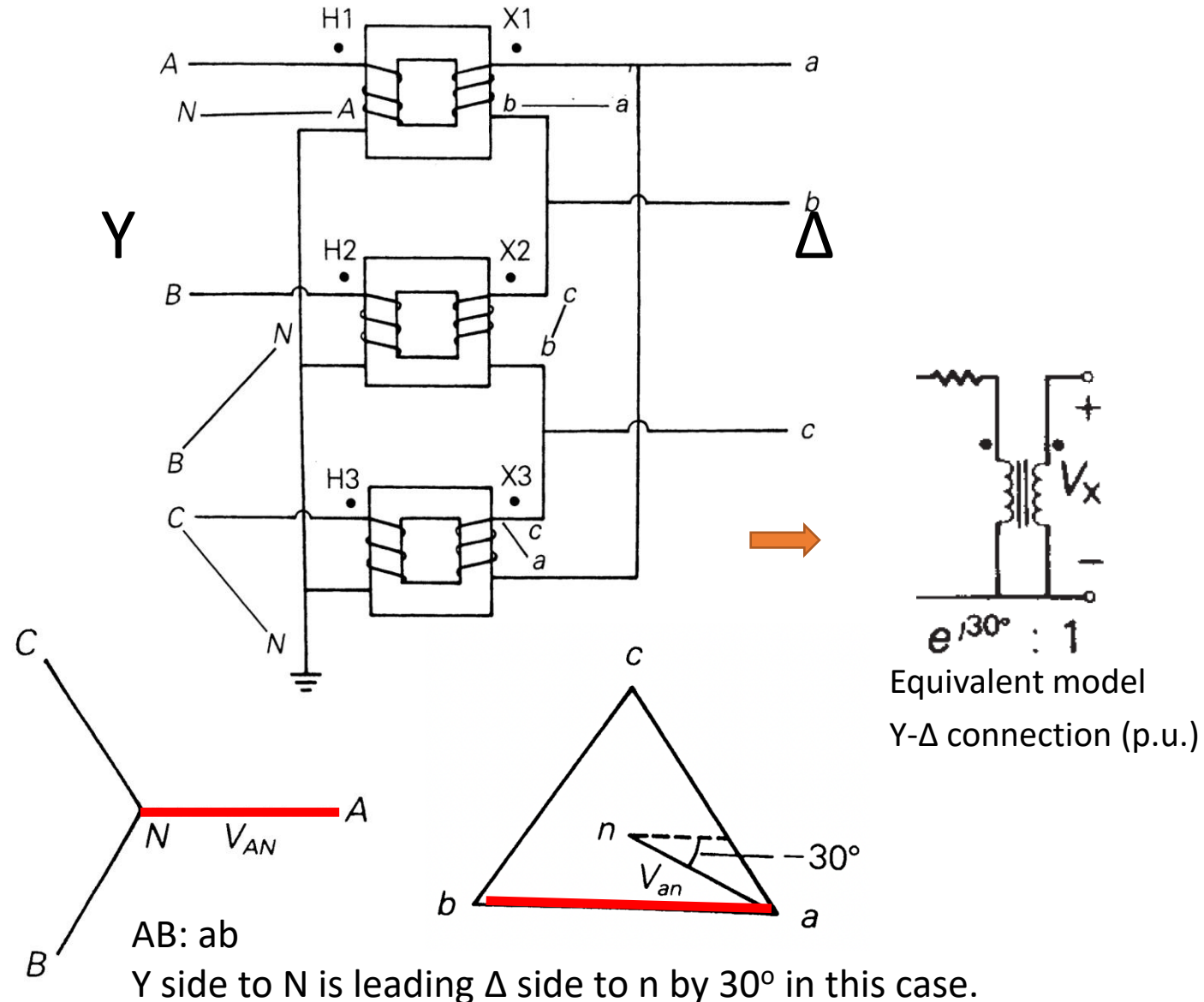For p.u. calculation,  $\sqrt{3} \frac{N_{H1}}{N_{X1}}$  will be eliminated.




# Per unit for three-phase transformer

## Y-Y connection

The following are two conventional rules for selecting base quantities:

- A common  $S_{\text{base}}$  is selected for both the H and X terminals.
- The ratio of the voltage bases  $V_{\text{baseH}}/V_{\text{baseX}}$  is selected to be equal to the ratio of the rated line-to-line voltages  $V_{\text{ratedHLL}}/V_{\text{ratedXLL}}$ .

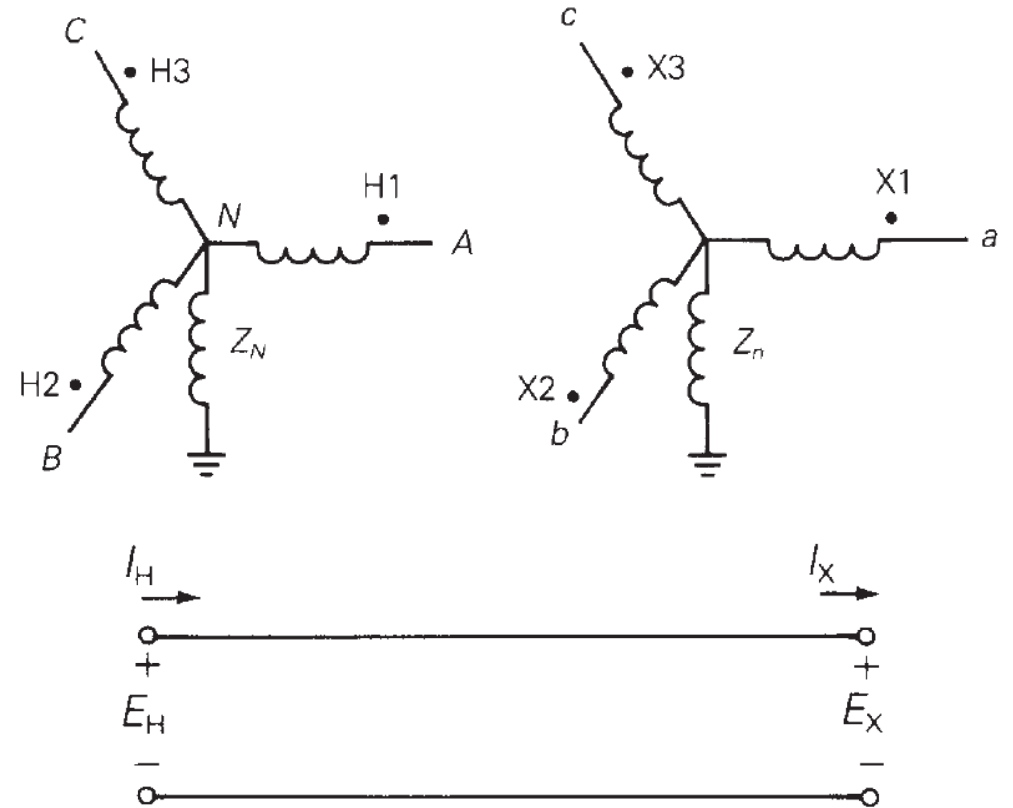For the American standard, the positive-sequence (A-B-C) voltages and currents on the high-voltage side of the Y- $\Delta$  transformer lead the corresponding quantities on the low-voltage side by  $30^\circ$ .





# Example: Voltage calculations

- ❖ Three single-phase two-winding transformers, each rated 400 MVA, 13.8/199.2 kV, with leakage reactance  $X_{eq}=0.10$  per unit, are connected to form a three-phase bank. Winding resistances and exciting current are neglected. The high-voltage windings are connected in Y. A three-phase load operating under balanced positive- sequence conditions on the high-voltage side absorbs 1000 MVA at 0.90 p.f. lagging, with  $V_{AN}=199.2\angle 0^\circ$  kV. Determine the voltage  $V_{an}$  at the low-voltage bus if the low-voltage windings are connected (a) in Y and (b) in  $\Delta$ .

## SOLUTION for (a)

Using the transformer bank ratings as base quantities,

$$S_{base3\phi}=1200 \text{ MVA}, V_{baseHLL}=345 \text{ kV}, \text{ and } I_{baseH}=1200/(345\sqrt{3})=2.008 \text{ kA}.$$

The per-unit load voltage and load current are then

$$V_{AN} = 1.0\angle 0^\circ \text{ per unit}$$

$$I_A = \frac{1000/(345\sqrt{3})}{2.008} \angle -\cos^{-1}0.9 = 0.8333\angle -25.84^\circ \text{ per unit}$$

$$I_a = I_A = 0.8333\angle -25.84^\circ \text{ per unit}$$


$$V_{an} = V_{AN} + (jX_{eq})I_A$$

$$= 1.0\angle 0^\circ + (j0.10)(0.8333\angle -25.84^\circ)$$

$$= 1.0 + 0.08333\angle 64.16^\circ = 1.0363 + j0.0750 = 1.039\angle 4.139^\circ$$

$$= 1.039\angle 4.139^\circ \text{ per unit}$$

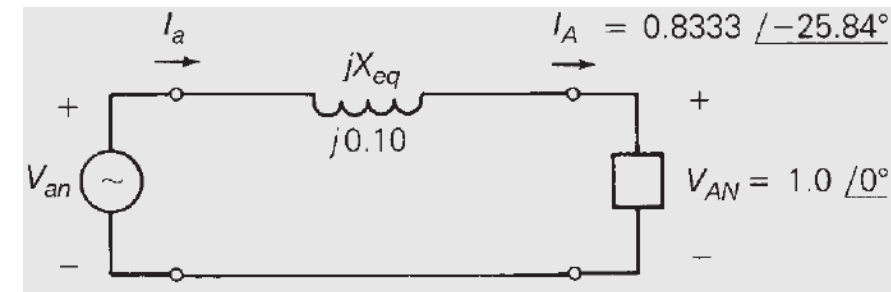Further, since  $V_{baseXLN}=13.8$  kV for the low-voltage Y windings,  $V_{an} = 1.039(13.8) = 14.34$  kV, and



Y connected winding

➔  $V_{an} = 14.34\angle 4.139^\circ \text{ kV}$

# Example: Voltage calculations

- ❖ Three single-phase two-winding transformers, each rated 400 MVA, 13.8/199.2 kV, with leakage reactance  $X_{eq}=0.10$  per unit, are connected to form a three-phase bank. Winding resistances and exciting current are neglected. The high-voltage windings are connected in Y. A three-phase load operating under balanced positive- sequence conditions on the high-voltage side absorbs 1000 MVA at 0.90 p.f. lagging, with  $V_{AN}=199.2\angle 0^\circ$  kV. Determine the voltage  $V_{an}$  at the low-voltage bus if the low-voltage windings are connected (a) in Y and (b) in  $\Delta$ .

## SOLUTION for (b)

\* Y side to N is leading  $\Delta$  side to n by  $30^\circ$  in this case.

$$E_{an} = 1.0\angle -30^\circ \text{ per unit}$$


$$I_a = 0.8333\angle -25.84^\circ - 30^\circ = 0.8333\angle -55.84^\circ \text{ per unit}$$


$$V_{an} = E_{an} + (jX_{eq})I_a = 1.0\angle -30^\circ + (j0.10)(0.8333\angle -55.84^\circ)$$

$$V_{an} = 1.039\angle -25.861^\circ \text{ per unit}$$

Further, since  $V_{baseXLN} = 13.8/\sqrt{3} = 7.967$  kV for the low-voltage  $\Delta$  windings,  
 $V_{an} = (1.039)(7.967) = 8.278$  kV, and
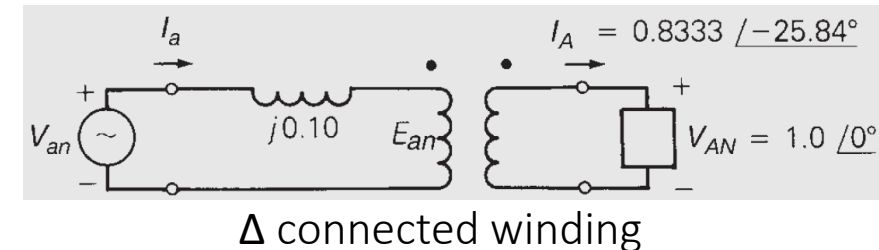
$$V_{an} = 8.278\angle -25.861^\circ \text{ kV}$$





# Summary

- Three-phase voltage source and load
- Y and  $\Delta$  connections
- Phase and line values
- Power in three-phase loads
- Wattmeter and measurements
- $3\phi$  transformer connections