

## EE3123 Tutorial 2 (Solution)

### AC Power Circuits and Components II

Name:

Student No.:

---

#### Q1

An ideal transformer with  $N_1 = 1000$  and  $N_2 = 250$  is connected with an impedance  $Z_{22}$  across winding 2. If  $V_1 = 1000 \angle 0^\circ$  V and  $I_1 = 5 \angle -30^\circ$  A, determine  $V_2$ ,  $I_2$ ,  $Z_2$ , and the impedance  $Z'_2$ , which is the value of  $Z_2$  referred to the primary side of the transformer.

#### Solution

$$\bar{V}_2 = \frac{N_2}{N_1} \bar{V}_1 = \frac{250}{1000} (1000 \angle 0^\circ) = 250 \angle 0^\circ \text{ V} \leftarrow$$

$$\bar{I}_2 = \frac{N_1}{N_2} \bar{I}_1 = \frac{1000}{250} (5 \angle -30^\circ) = 20 \angle -30^\circ \text{ A} \leftarrow$$

$$\bar{Z}_2 = \frac{\bar{V}_2}{\bar{I}_2} = \frac{250 \angle 0^\circ}{20 \angle -30^\circ} = 12.5 \angle 30^\circ \Omega$$

$$\bar{Z}'_2 = Z_2 \left( \frac{N_1}{N_2} \right)^2 = (12.5 \angle 30^\circ) \left( \frac{1000}{250} \right)^2 = 200 \angle 30^\circ \Omega \leftarrow$$


$$\text{Also } \bar{Z}'_2 = \bar{V}_1 / \bar{I}_1 = (1000 \angle 0^\circ) / (5 \angle -30^\circ) = 200 \angle 30^\circ \Omega \leftarrow$$

#### Q2

A single-phase 100-kVA, 2400/240-volt, 60-Hz distribution transformer is used as a step-down transformer. The load, which is connected to the 240-volt secondary winding, absorbs 60 kVA at 0.8 power factor lagging and is at 230 volts. Assuming an ideal transformer, calculate the following:

- (a) primary voltage,
- (b) load impedance,
- (c) load impedance referred to the primary, and
- (d) the real and reactive power supplied to the primary winding.

#### Solution

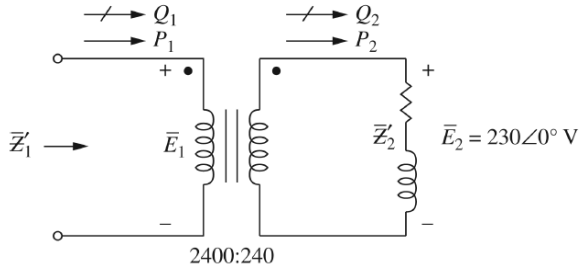

$$(a) \quad E_1 = \frac{N_1}{N_2} E_2 = \frac{2400}{240} (230) = 2300 \text{ V}$$

$$(b) \quad \bar{S}_2 = \bar{E}_2 \bar{I}_2^*; \bar{I}_2 = \left( \frac{\bar{S}_2}{\bar{E}_2} \right)^* = \left[ \frac{60 \times 10^3 \angle \cos^{-1} 0.8}{230 \angle 0^\circ} \right]^* = 260.9 \angle -36.87^\circ$$

$$\bar{Z}_2 = \frac{\bar{E}_2}{\bar{I}_2} = \frac{230 \angle 0^\circ}{260.9 \angle -36.87^\circ} = 0.8817 \angle 36.87^\circ \Omega$$

$$= 0.705 + j.529 \Omega$$

$$(c) \quad \bar{Z}'_1 = \left( \frac{N_1}{N_2} \right)^2 \bar{Z}_2 = 100 \bar{Z}_2 = 88.17 \angle 36.87^\circ \Omega$$

$$(d) \quad P_1 = P_2 = 60(0.8) = 48 \text{ kW}$$

$$Q_1 = Q_2 = 48 \tan(36.87^\circ) = 36 \text{ kVAR}$$

### Q3

A single-phase step-down transformer is rated 13 MVA, 66 kV/11.5 kV. With the 11.5 kV winding short-circuited, rated current flows when the voltage applied to the primary is 5.5 kV. The power input is read as 100 kW. Determine  $R_{eq1}$  and  $X_{eq1}$  in ohms referred to the high-voltage winding.

### Solution

Rated current magnitude on the 66-kV side is given by

$$I_1 = \frac{13,000}{66} = 197.0 \text{ A}$$

$$I_1^2 R_{eq1} = (197.0)^2 R_{eq1} = 100 \times 10^3$$


$$\therefore R_{eq1} = 2.58 \Omega \quad \leftarrow$$

$$\bar{Z}_{eq1} = \frac{5.5 \times 10^3}{197.0} = 27.9 \Omega$$

$$\text{Then } X_{eq1} = \sqrt{\bar{Z}_{eq1}^2 - R_{eq1}^2} = \sqrt{(27.9)^2 - (2.58)^2} = 27.8 \Omega \quad \leftarrow$$
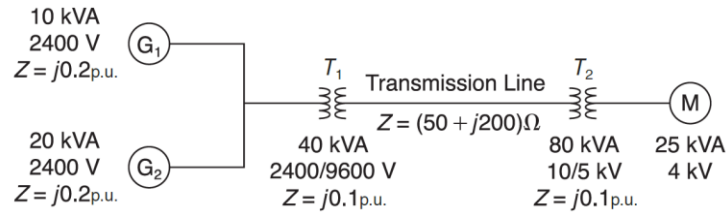
#### Q4

For the system shown below, draw an impedance diagram in per unit by choosing 100 kVA to be the base kVA and 2400 V as the base voltage for the generators.



#### Solution

$$G_1 : \bar{Z} = j0.2 \left( \frac{2400}{2400} \right)^2 \left( \frac{100}{10} \right) = j2 \text{ pu}$$

$$G_2 : \bar{Z} = j0.2 \left( \frac{2400}{2400} \right)^2 \left( \frac{100}{20} \right) = j1 \text{ pu}$$

$$T_1 : \bar{Z} = j0.1 \left( \frac{2400}{2400} \right)^2 \left( \frac{100}{40} \right) = j0.25 \text{ pu}$$

$$T_2 : \bar{Z} = j0.1 \left( \frac{10}{9.6} \right)^2 \left( \frac{100}{80} \right) = j0.136 \text{ pu}$$

$$\text{For the transmission-line zone, base impedance} = \frac{(9600)^2}{100 \times 10^3}$$

$$\therefore \bar{Z}_{LINE} = (50 + j200) \frac{100 \times 10^3}{(9600)^2} = (0.054 + j0.217) \text{ pu}$$

$$M; \text{ kVA} = \frac{25}{100} = 0.25 \text{ pu}; 4 \text{ kV} = \frac{4}{4.8} = 0.833 \text{ pu}$$

The impedance diagram for the system is shown below:

