

EE3123 Tutorial 4 (Solution)

Power System Stability


Name:

Student No.:

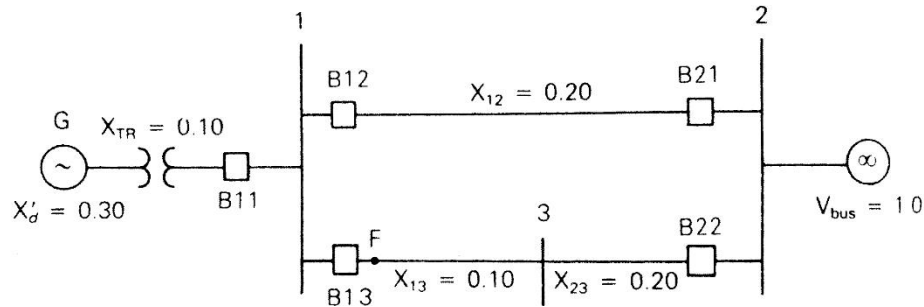
Q1

The synchronous generator below delivers 0.8 per-unit real power at 1.05 per-unit terminal voltage. Determine:

- the reactive power output of the generator;
- the generator internal voltage; and
- an equation for the electrical power delivered by the generator versus power angle δ .



Solution

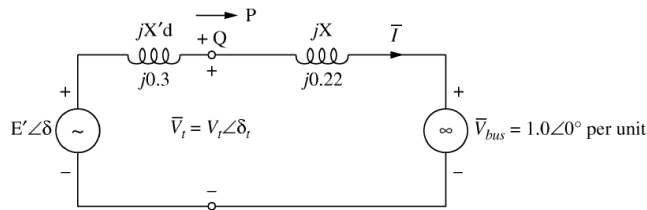

$$(a) \quad P = \frac{V_t V_{bus}}{X} \sin \delta_t \Rightarrow \sin \delta_t = \frac{(P)(X)}{(V_t)(V_{bus})} = \frac{(0.8)(0.22)}{(1.05)(1.0)} = 0.167619$$

$$\delta_t = \sin^{-1}(0.167619) = 9.65^\circ$$

$$\bar{I} = \frac{\bar{V}_t - \bar{V}_{bus}}{jX} = \frac{1.05 \angle 9.65^\circ - 1.0 \angle 0^\circ}{j0.22}$$

$$\bar{I} = \frac{0.03514 + j0.1760}{j0.22} = 0.81579 \angle -11.291^\circ$$

$$\bar{S} = \bar{V}_t \bar{I}^* = (1.05 \angle 9.65^\circ)(0.81579 \angle 11.291^\circ) = 0.85658 \angle 20.941^\circ$$

$$\bar{S} = 0.80 + j0.306 \quad Q = \text{Im} \bar{S} = \underline{0.306} \text{ per unit}$$

$$(b) \quad \bar{E}' = \bar{V}_{bus} + j(X'_d + X)\bar{I} = 1.0 \angle 0^\circ + j(0.3 + 0.22)(0.81579 \angle -11.291^\circ)$$

$$\bar{E}' = 1.0 \angle 0^\circ + 0.4242 \angle 78.709^\circ$$


$$\bar{E}' = 1.160 \angle 21.01^\circ \text{ per unit}$$

$$(c) \quad P = \frac{E' V_{bus}}{(X'_d + X)} \sin \delta = \frac{(1.160)(1.0)}{0.3 + 0.22} \sin \delta$$

$$P = 2.231 \sin \delta \text{ per unit}$$

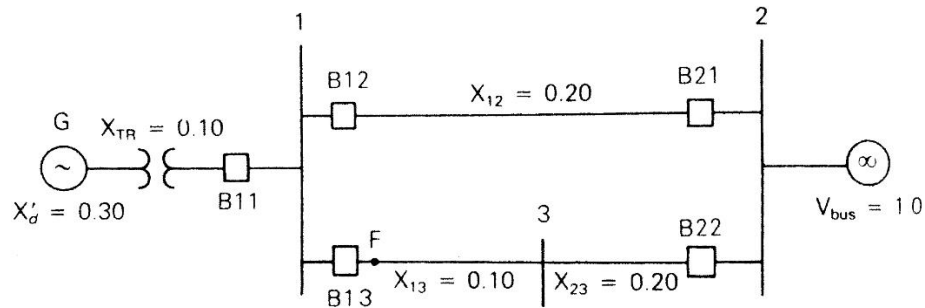
Q2

The generator in Q1 is initially operating in the steady-state condition given in Q1 when a three-phase-to-ground bolted short circuit occurs at bus 3. Determine an equation for the electrical power delivered by the generator versus power angle δ during the fault.




Solution

Circuit during the fault at bus 3:

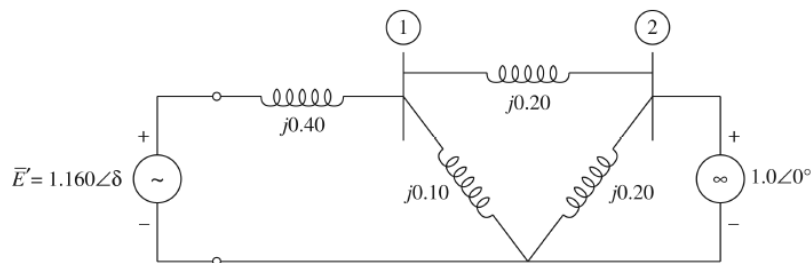

where $\bar{E}' = 1.160 \angle \delta$ is determined

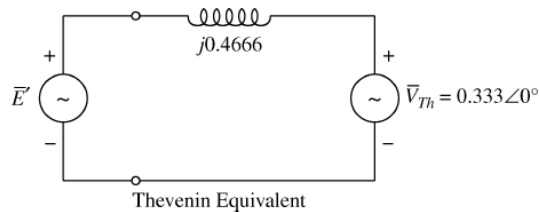
The Thévenin equivalent, as viewed from the generator internal voltage source, is shown here,




$$P = \frac{\bar{E}' V_{Th}}{x_{Th}} \sin \delta = \frac{(1.160)(0.333)}{0.4666} \sin \delta = \underline{\underline{0.8279}} \sin \delta \text{ per unit}$$

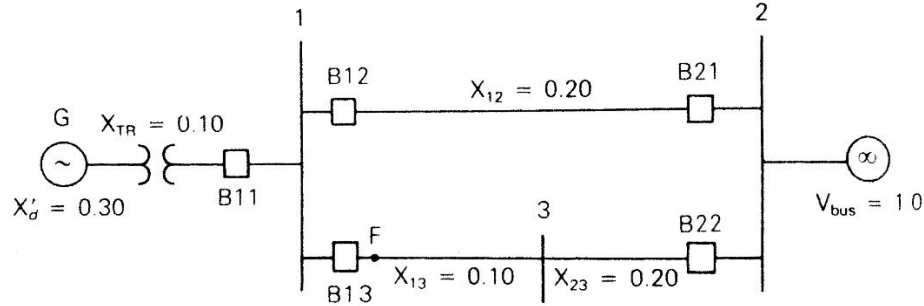Q3


The 60-Hz synchronous generator shown below is initially operating in the steady-state condition: the infinite bus receives 1.0 per unit real power at 0.95 p.f. lagging. When circuit breaker B12 inadvertently opens, use the equal-area criterion to calculate the maximum value of the generator power angle δ . Assume $\omega_{p.u.}(t)=1.0$ in the swing equation.



Solution

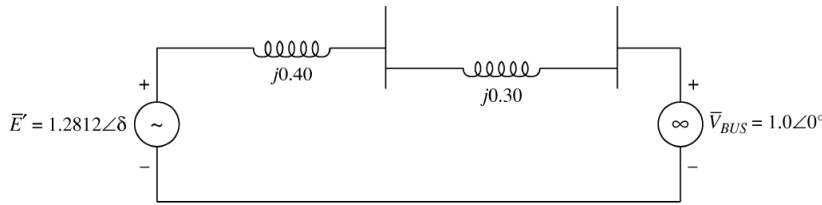
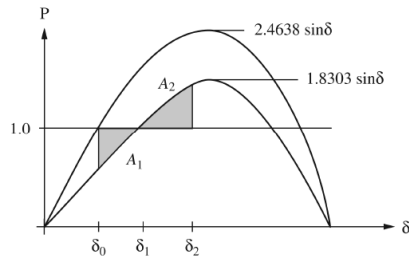
$$P = \frac{E' V_{BUS}}{X_{eq}} \sin \delta = \frac{(1.2812)(1.0)}{0.70} \sin \delta = 1.8303 \sin \delta$$



$$\delta_0 = \sin^{-1} \left(\frac{1}{2.4638} \right) = 0.4179 \text{ rad}$$

$$\delta_1 = \sin^{-1} \left(\frac{1}{1.8303} \right) = 0.5780 \text{ rad}$$

$$A_1 = \int_{\delta_0=0.4179}^{\delta_1=0.5780} (1.0 - 1.8303 \sin \delta) d\delta = \int_{\delta_1=0.5780}^{\delta_2} (1.8303 \sin \delta - 1) d\delta = A_2$$


$$(0.5780 - 0.4179) + 1.8303(\cos 0.5780 - \cos 0.4179) = 1.8303(\cos 0.5780 - \cos \delta_2)$$

$$-(\delta_2 - 0.5780)$$

$$1.8303 \cos \delta_2 + \delta_2 = 2.0907$$

Solving iteratively (Newton-Raphson) $\delta_2 = \underline{\underline{0.7439 \text{ rad}}} = \underline{\underline{42.62^\circ}}$

The 60-Hz synchronous generator shown below is initially operating in the steady-state condition: the infinite bus receives 1.0 per unit real power at 0.95 p.f. lagging. There is a temporary three-phase-to-ground short circuit that occurs at point F. Exact three cycles later, circuit breakers B13 and B22 permanently open to clear the fault. Use the equal-area criterion to determine the maximum value of the power angle δ_2 . (H = 3 pu-s)

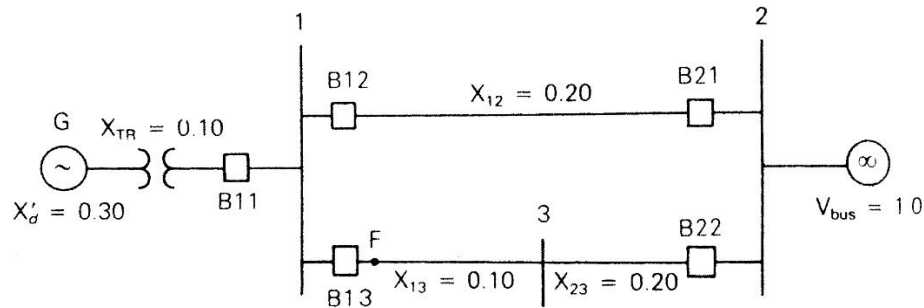

The graph shows Power (P) on the vertical axis and angle (δ) on the horizontal axis. A horizontal line is drawn at $P = 1.0$. Two sine wave curves originate from the origin. The upper curve is labeled $2.4638 \sin \delta$ (prefault). The lower curve is labeled $\frac{(1.2812)}{0.6} \sin \delta = 2.1353 \sin \delta$ (postfault). The area under the prefault curve above the $P = 1.0$ line, between δ_0 and δ_1 , is shaded gray and labeled A_1 . The area under the postfault curve above the $P = 1.0$ line, between δ_1 and δ_2 , is shaded white and labeled A_2 . The x-axis has points δ_0 , δ_1 , and δ_2 marked. The y-axis has a value of 1.0 marked.

$$\delta_1 = 0.4964 \text{ rad}$$

$$A_1 = \int_{\delta_0=0.4179}^{\delta_1=0.4964} 1.0 d\delta = \int_{\delta_1=0.4964}^{\delta_2} (2.1353 \sin \delta - 1.0) d\delta$$

$$(0.4964 - 0.4179) = 2.1353(\cos 0.4964 - \cos \delta_2) - (\delta_2 - 0.4964)$$

$$2.1353 \cos \delta_2 + \delta_2 = 2.2955$$

$$\delta_2(i+1) = \delta_2(i) + [-2.1353 \sin \delta_2(i) + 1]^{-1} [2.2955 - 2.1353 \cos \delta_2(i) - \delta_2(i)]$$

i	0	1	2	3	4
δ_2	0.60	0.925	0.804	0.785	0.7850

4 | Page